

AUSTRALIA'S DYNAMIC ELECTRONICS MONTHLY!

Electronics Today

INTERNATIONAL




\$2.95 NZ\$3.75

JUNE 1986

**PC BOARD SHOPS
NEW WAVE**

FIBRE OPTICS ARRIVE

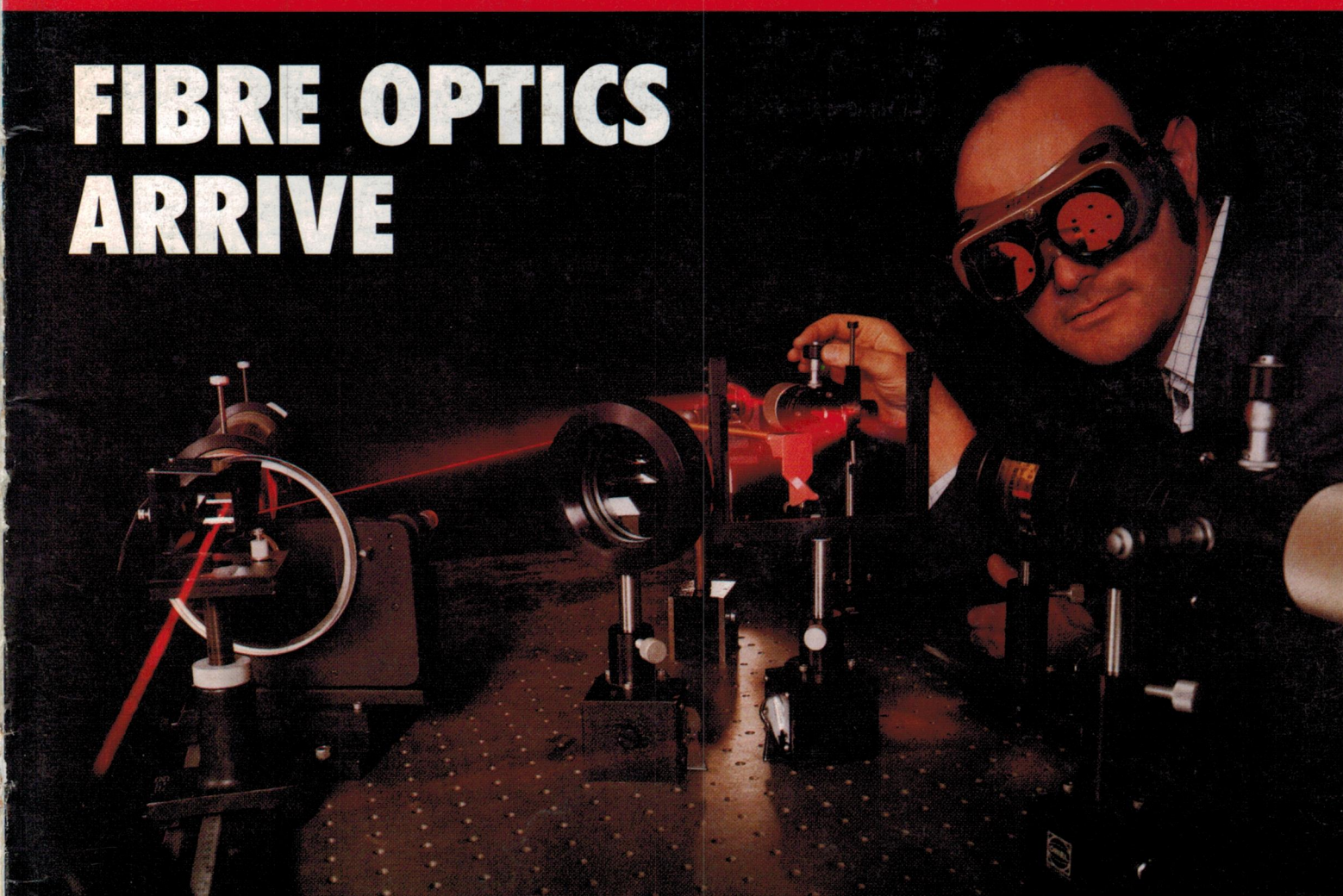


PROJECTS:

**THE INTELLIGENT MODEM
CAR DEMISTER TIMER**

**ELECTROSTATIC HAZARD ALARM
MUSICIAN'S DIGITAL SAMPLER**


Some CAD names come before others

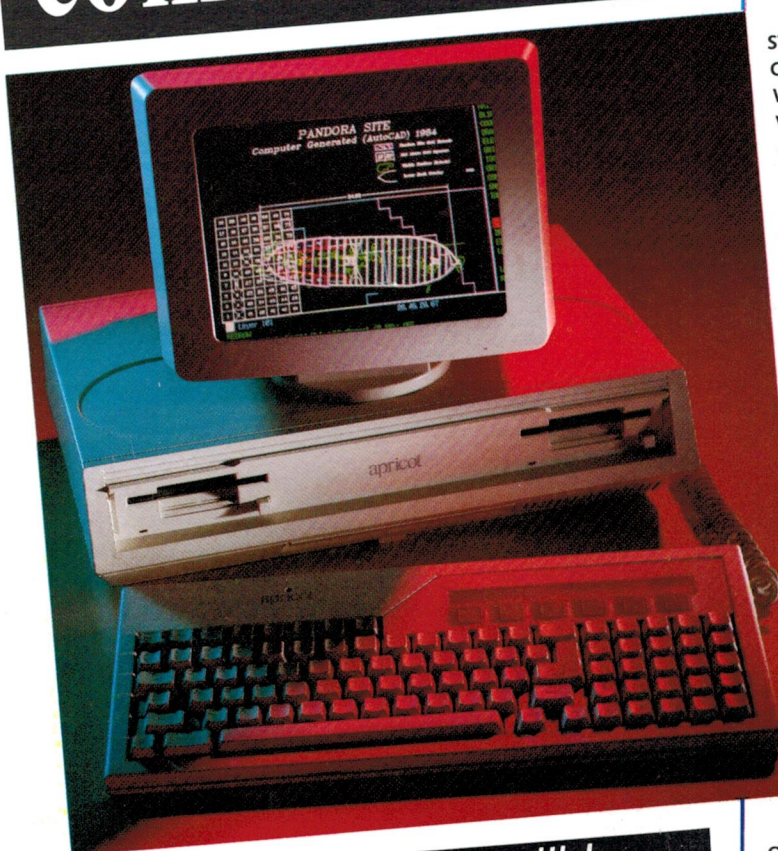

Pandora project, an incredible application in marine technology.



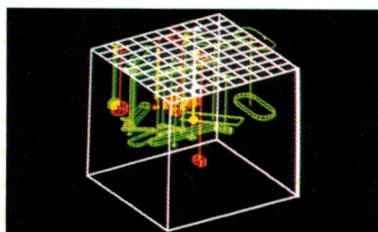Overlay and grid definition in the Pandora application.



Demonstration of AutoCAD's 3D visualization capabilities.

AutoCAD™ is a trademark of Autodesk Int.
apricot is distributed by BARSON COMPUTERS



"Our strategy to make AutoCAD™ the standard in Australia is working and our commitment to this strategy never wavers" say the directors of ENTERCOM, venting the same philosophy and commitment as the president of Autodesk Int. Mr. John Walker.

Upgrades to AutoCAD™ provide new releases like 3D visualization, curve fitting and macro programming capability. AutoCAD™ currently runs on over 31 personal computers, with more being released on a continuing basis. Vertical market applications such as AE/CADD™, are being Australianized for professional architectural applications. CAD/camera™, provides an auto-vectorizing system which converts paper drawings into AutoCAD™ usable and modifiable drawings automatically at approximately 5% of the price of competitive systems. AutoCAD™ to mainframe translators allow the integration of AutoCAD™ with large scale CAD systems including CADAM™, Intergraph™ and Computervision™. AutoCAD™ is available in French, German, Swedish, Italian, Japanese and Spanish.

ENTERCOM believes, as do the authors of AutoCAD™ that by mid-1986, the distinctions being made between mainframe and mini-based CAD systems will disappear.

**The secret is out.
AutoCAD™ is better.**

AutoCAD™ can perform all the functions most people want from a Computer Aided Design/Drafting Package. AutoCAD™ is fast, easy to learn as well as being user-customizable, with the added ability to communicate with other Systems. There is no other CAD package that supports as many peripheral devices, (that is both input and output devices) and there is certainly no other package that is supported by over 150 independent application software interfacers. AutoCAD™ is Number one in Australia and Worldwide — **for all the right reasons.**



AUSTRALIAN DISTRIBUTOR

136 BRIDGE RD., RICHMOND, VICTORIA, 3121, AUSTRALIA
PHONE: (03) 429 9888 TELEX: 30625 ME1400

EDITOR

David Kelly B.Com.

ASSISTANT EDITOR

Jon Fairall B.A.

EDITORIAL STAFF

Mary Rennie B.A.

S. K. Hui B.Sc. (Hons), M.Eng.Sc., MIEEE, MIREE
Neale Hancock B.E.**DRAUGHTING**

David Burrows

ART DIRECTOR

Vicki Jones

ART STAFF

Ray Eirth

ADVERTISING MANAGER

Peter Hayes B.Sc.

ADVERTISING PRODUCTION

Wayne Hanley

READER SERVICES

Pam Todd

ACOUSTICAL CONSULTANTS

Louis Challis and Associates

PUBLISHER

Michael Hannan

MANAGING EDITOR

Leo Simpson

HEAD OFFICE180 Bourke Road, (PO Box 227, Waterloo, NSW
2017)

Alexandria, NSW 2015.

Phone: (02) 693-6666.

Telex: AA74488, FEDPUB.

Federal Facsimile: (02) 693-2842.

ADVERTISING**New South Wales**

Peter Hayes, Mark Lewis (02) 693-6666

Victoria and Tasmania

Virginia Salmon (03) 662-1222

South Australia and Northern Territory

Dane Hansen (08) 212-1212

Queensland

Tracy Tyler (07) 854-1119

Western Australia

Jim Wells (09) 481-3171

New Zealand

John Easton 79-6648 (Auckland)

OFFICES**New South Wales:** The Federal Publishing
Company, 180 Bourke Road, Alexandria, NSW
2015. Phone (02) 693-6666. Telex: AA74488
FEDPUB.**Victoria and Tasmania:** The Federal Publishing
Company, 23rd Floor, 150 Lonsdale Street,
Melbourne, Vic. 3000. Phone: (03) 662-1222.
Telex: AA34340, FEDPUB.**South Australia and Northern Territory:** John
Fairfax & Sons, 101-105 Waymouth Street,
Adelaide, 5000. Phone (08) 212-1212. Telex:
AA82930.**Queensland:** The Federal Publishing Company,
26 Chermiside Street, Newstead, Qld. 4006.
Phone: (07) 854-1119. Telex: AA145520.**Western Australia:** Jim Wells, John Fairfax &
Sons, 454 Murray Street, Perth, WA 6000. Phone:
(09) 321-8217. Telex: AA92635.**New Zealand:** 3rd Floor, Communications House,
12 Heather Street, Parnell, Auckland, PO Box
8770, Symonds St, 37-291 Telex NZ63122. Phone
(09) 396-096.

ELECTRONICS TODAY INTERNATIONAL is
published and distributed monthly by the
Electronics Division of the Federal Publishing
Company Pty Limited, 180 Bourke Road,
Alexandria, NSW 2015 under licence from Double
Bay Newspapers Pty Limited, General Newspapers
Pty Limited and Suburban Publications Pty Limited.
Printed by Hannanprint, Sydney. Distributed by
Gordon and Gotch Limited, Sydney. *Maximum
and recommended Australian retail price only.
Registered by Australia Post, Publication No
NBP0407. ISSN No 0013-5216.

COPYRIGHT © 1985, Double Bay Newspapers Pty
Limited, General Newspapers Pty Limited and
Suburban Publications Pty Limited (trading as
"Eastern Suburbs Newspapers").

CONTENTS

Electronics Today

FEATURES

Optical fibres arrive in the marketplace	12
And it's given a boost to industry	
Inside the board shops	19
Where technology has waved goodbye to the human hand	
Inside your computer	70
Central to the computer are the processor and memory	
Starting electronics	82
Light and electronics	

PROJECTS

ETI-1402: Digital sampler Part 3	42
The sampler making sounds	
ETI-173: Electrostatic hazard detector	46
This project alerts you to dangerous moving electrostatic fields	
ETI-345: Demister timer	54
A simple project to switch off your demister after 10 or 20 minutes	
ETI-684: Intelligent modem Part 4	58
Software protocols, commands and memory	

REVIEWS

Tempting Alpine heights	30
The Alpine 5900 car CD player offers something for the high flyer	
Glittering gold	35
The Tannoy M20 "gold" loudspeakers lure	
Clearing the lab shelves	93
Marconi's 2955 combines a shelf full of test equipment	

OFFERS


Advertisers' index	55
ETI mail order books	76,77
ETI-Schools projects competition	78
Subscriptions offer	90

DEPARTMENTS

News Digest	6	Shoparound	75
Computing News	67	Microbee Column	73
Communications News	96	Commodore Column	74
Idea of the Month	63	Minimart	45
Ideas for Experimenters	64	Dregs	98
Schools News	78		

COVER: Designed by Vicki Jones, photograph courtesy Telecom Photographic Section, Melbourne.

Tektronix new digital oscilloscopes

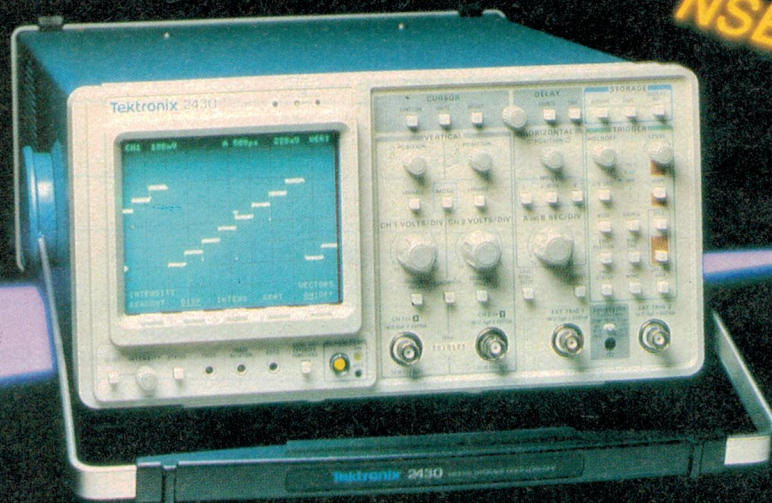

The fastest signal capture and A/D conversion yet.

Tek researchers have again run ahead, anticipating the higher performance levels required for design, trouble shooting, applied research and test and measurement. The new Tek 2430, 150 MHz digital oscilloscope is a breakthrough in price/performance levels.

A 100-megasample/sec sampling rate makes the Tek 2430 spot on for fast conversion and viewing of analogy or digital signals. This is achieved with a new proprietary charge coupled device.

Capturing single shot glitches as narrow as 2ns at any sample rate is now a constant reality with Tektronix new clocked peak detector. The 2430 gives

recording of two high-speed transients, simultaneously.

High wave form update rate allows 40-100 acquisitions per second with the sharp resolution required for digital design and trouble shooting.

Fast control to screen response time cuts user overcompensation in selection or adjustment.

New concept in chassis design reduces cost. While providing better protection for the components this new composite chassis also weighs some 30% less than similar models. To further reduce ownership costs the 2430 incorporates extensive self test/diagnostic and auto calibration features.

A price/performance choice in portables. There's also the new low cost Tek 2230 and 2220 digital models offering storage and non-storage bandwidths of 100MHz and 60MHz.

Call us. We'll move fast to let you experience these new high performance models.

Brisbane 394 1155, **Sydney** 888 7066, **Canberra** 82 3587, **Melbourne** 813 1455, **Adelaide** 223 2811, **Perth** 325 8433.

Tektronix®
COMMITTED TO EXCELLENCE

SERVICES

TECHNICAL INQUIRIES: Technical inquiries by mail must be accompanied by a stamped self-addressed envelope. There is no charge, but we reserve the right to publish the inquiry and the reply in *Electronics Today* or any of its associated publications. We can only answer queries relating to projects and articles as published. We cannot advise on modifications, other than errata or addenda. Difficult questions may take some time to answer.

GENERAL INQUIRIES: For all inquiries about back issues, subscriptions, photocopies of articles, artwork or submitting articles call (02) 693-6666 or write to: ETI Reader Services, 180 Bourke Rd, Alexandria, NSW 2015; (PO Box 227, Waterloo NSW 2017).

CONTRIBUTIONS: Submissions must be accompanied by a stamped, self-addressed envelope. The publisher accepts no responsibility for unsolicited material.

COPYRIGHT: The contents of *Electronics Today International* and associated publications is fully protected by the Commonwealth Copyright Act (1968). Copyright extends to all written material, photographs, drawings, circuit diagrams and printed-circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by bands (for example) constructing one or more items for use in connection with their performances. Commercial organisations should note that no project or part project described in *Electronics Today International* or associated publications may be offered for sale, or sold in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publisher, The Federal Publishing Company, or from the copyright holders.

LIABILITY: Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available, no responsibility is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any component parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.

IT IS INEVITABLE that the issue of the Federal Government breaking up or selling off Telecom will raise its head every few years.

Although the people who work for Telecom believe such an outcome would be a very bad thing, the means to prevent it lies precisely with them.

Don't get me wrong, I am not promoting the privatisation of Telecom. In fact I think those who are asking for changes are asking for something which will do them little if any good.

Virtually all of the demands for a Telecom sale or break-up come because people are dissatisfied with the service or from businesses that incur significant costs in use of their inter capital communications routes.

Telecom still uses revenue from these major routes to subsidise its activities in other areas, particularly services in more remote places. Given the business community's belief that this is costing them a lot of money it is little wonder it wants to have communications costs reduced. But it is here that I think the business community is misguided.

Because the great bulk of Telecom traffic is between the capitals the elimination of cross subsidies may not reduce its cost by very much at all.

Also the very nature of the telecommunications business is changing. There are three main cost components involved in carrying a communications signal, based on distance, bandwidth and the time taken to transmit the signal.

As technology crams more signals into the one cable duct, and with satellites, the distance element and hence the need for cross subsidies is becoming less and less important.

The other area of discontent and potentially the most damaging for Telecom is the quality of service. If enough people are dissatisfied, Telecom's position will be at risk even if no other organisation could do its job any better, and then Telecom employees might be affected.

Telecom suffers from the same management ills that affect all large organisations, public or private. The bigger they become the more management loses touch with its customers.

It also becomes easier for staff to lose touch and become less interested in serving the people who provide the organisation's revenue, its customers.

In my experience most people who work for Telecom are enthusiastic about Telecom and its customers. Yet there are a few, hopefully only a small few, who at best are lethargic and at worst actively discourage any enthusiasm from their colleagues.

Most Telecom people and people who work for similarly large organisations know the sort of person I mean. They are usually the major source of frustration and even anger of fellow workers and customers.

Telecom is no different from any other large private or public organisation in that in the long run the organisation's future is entirely in the hands of its staff and management.


I don't know whether Telecom would be better run by private industry — I'm sure no one else does either.

But there is one thing I am absolutely sure about. If Telecom people want a future that they will have some control over they must provide a service that is unerringly a pleasure for its business and domestic customers to use.

If they don't make some changes about the people who are holding the organisation back they will get some change they really don't want.

SUBSCRIBERS SHOULD NOTE that they can receive a free ETI publication with this issue. Because of packaging problems it has not been included. Subscribers who want the publication should write to ETI June Offer, PO Box 227, Waterloo NSW 2017.

David Kelly
Editor

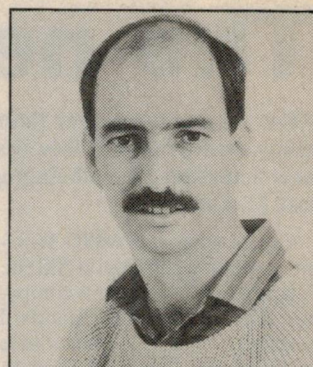

NEXT MONTH

COMPUTER AIDED DESIGN

Why has it taken so long to introduce CAD in Australia? Perhaps it's because the advantages of computer aided design are not always obvious; perhaps it's endemic conservatism. We evaluate CAD in the light of its applications.

VZ200 UPDATE

A welcome project which among other things provides for more memory and a new keyboard.

MODEM NEWS

The full details! No kidding...

CASSETTE TAPE REVIEW

The audio review next month focuses on cassette tape. Louis Challis tests all the major brands of Type II chrome tape for their audio characteristics as well as durability and packaging. The result is a ranking with consideration to price and quality indispensable to anyone who values their recordings.

The new 'Bee

After a gestation longer than an elephant's and with twice as many rumours, Microbee Systems announced the launch of its new computer, the all singing, all dancing Gamma at PC '86 last March.

Centre stage is a 68000 16/32-bit processor running at 8MHz. A couple of Z80s keep it company. This controls a standard megabyte of RAM, expandable to four megs internally and to eight megs in total. It uses a 3.5 inch, double sided microfloppy for mass storage.

The graphics system will run high speed 720 x 350 pixels. A palette system allows 16 colours to be selected from a total of 4096.

The Gamma runs on CP/M 68K and Unix operating systems. In addition an optional card carries an 80186 co-processor so that it can run MS-DOS. Finally, it is compatible with CP/M80 8-bit software developed for previous 'Bees.

A break with the past is a separate low profiled, 92-pad keyboard. It has tilting feet to allow the operator to orientate the keyboard at a comfortable angle. The keyboard was designed in-house by Microbee to suit the Gamma and other modern computers.

According to Microbee Publicity Manager, Jim Rowe, the first production run of 'Bees has been given to software producers to write software for the machine. A release date has not yet been decided on but is likely to be later this year. Price is likely to be \$2500 or so, cheaper than its main competitor, the Commodore Amiga.



NASA shuttles plans

According to NASA publicity, the space agency intends ferrying the orbiter Columbia to Vandenberg Air Force Base in July "to support site validation testing". Vandenberg is the new shuttle base controlled by the US military.

However, suspicion is growing that the US Air Force intends to use Columbia to loft a new spy

satellite even before the enquiry into the Challenger disaster reports to Congress. Currently the US has only one operational spy satellite, a KH11. It was to be replaced this year with a KH12, but this plan was put into limbo after the Challenger disaster because the satellite is too heavy to be carried by any other available rocket.

A plan to use a final back-up KH11 as an interim replacement ended in disaster when the Titan rocket carrying it exploded seconds after launch. This leaves the US with three options: either build a new KH11, wait for shuttle clearance, or do without space spying.

It appears that Air Force officials are now ready to force the

issue of shuttle clearance. New booster rockets have already been designed that do without the O rings responsible for the Challenger crash, and pressure will mount to launch on a "try it and see" basis. The names of the crew members have yet to be announced.

WA traineeships

The WA Deputy Premier and Minister for Technology, Mal Bryce, and the Federal Minister for Employment and Industrial Relations, Ralph Willis, recently launched a program to train 100 teenagers in information and data processing.

The traineeships are part of the Commonwealth and State Government's commitment to improve the vocational training opportunities for young people

making the transition from school to work.

The program will provide on and off the job training. Trainees will be placed in a wide range of State Government departments while the Federal Government will meet the cost of the trainees attending TAFE colleges within the metropolitan area.

In addressing the trainees, Mr Bryce said suitably qualified

young people in the information technology field were in considerable demand.

"Almost every major office across the public and private sectors is opting for partial or complete office automation. There is a common belief that advances in information technology may be taking away jobs — the very opposite is the case.


"We very much need newly-qualified young people and this

program is the first in WA to recognise this need in such a comprehensive way," Mr Bryce said.

The traineeships have been organised by the WA Department of Computing and Information Technology, with the assistance of the WA Department of Employment and Training.

IF YOU BUY THIS SEIKOSHA BP5420AI BUSINESS PRINTER

\$3500 incl. tax

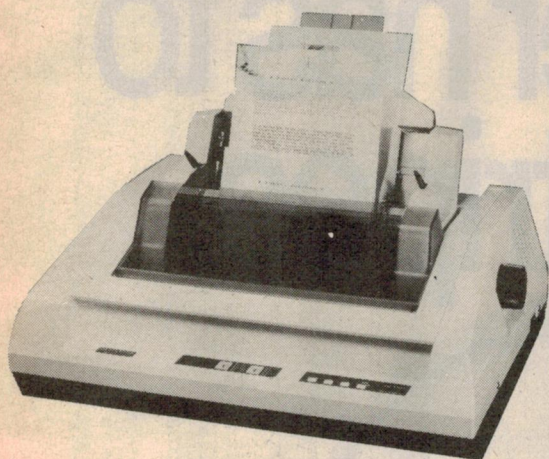


Features

- Two modes selectable, Standard mode (based on EPSON® FX) IBM® mode (IBM® PC compatible).
- Throughout-150 lines/minute at 132 chars./line.
- 420 cps (Draft mode) 104 cps (High quality Elite) print speed, with reduced noise level.
- A variety of print character sets including Pica, Elite, Proportional Condensed, Elongated, Italic, Super/Subscripts, Italic Super/Subscripts.
- A variety of functions including underlining, bold-printing double-strike and software-selectable line pitch specification.
- .18 K-byte communication buffer which allows the reception of data during printing.
- Two built-in interfaces (Centronics Parallel, RS-232C Serial).

THEN YOU GET THIS SEIKO WRIST TERMINAL FREE

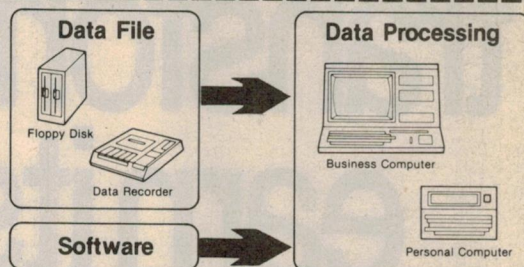Offer valid until September 5, 1986. Available only at participating dealers. Phone your local AWA office listed below for your nearest dealer.



For further information:


NAME.....

COMPANY.....

ADDRESS.....


- ☐ WRIST TERMINAL OFFER
☐ OTHER PRINTERS

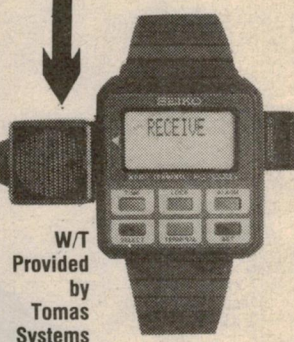Send to: P.O. 96,
NORTH RYDE,
OR PHONE YOUR LOCAL
AWA OFFICE




W/T
Provided
by
Tomas
Systems

SOME OTHER SEIKOSHA PRODUCTS:

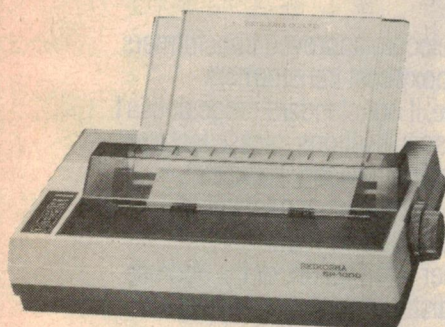

Features of SP-1000


- 100 cps (Draft mode), 20 cps (Near Letter Quality) print speed, with reduced noise level.
- Pin-feed or friction-feed • Automatic paper loading function.
- Right, left margin set function.
- A variety of functions including: Underline, Bold print, Double Striking.
- A variety of print character sets including: Pica, Elite, Proportional, Elongated, Condensed, Italics, Super/Subscripts, and Italic Super/Subscripts.

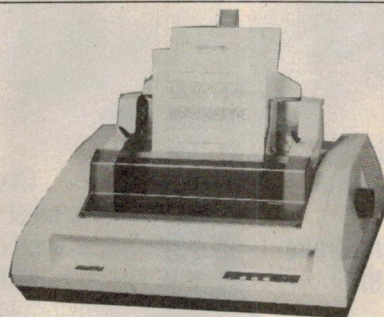

Features of BP5200

- 206 cps (Draft model) 103 cps (Correspondence mode) print speed, with reduced noise level.
- A variety of print character sets including Pica, Elite, Proportional, Elongated, Italic, Super/Subscripts, Italic Super/Subscripts.
- A variety of functions including underlining, bold-printing, double-strike, software-selectable line pitch specification.
- 4K byte communication buffer.
- Pin-feed and friction-feed both available.
- Paper width up to 15.5 inches.
- BP52201 — Centronics parallel with IBM character.
- BP5200A — 2 standard Interfaces (parallel and serial, 4K byte buffer expandable to 20K byte).

NEW RELEASE

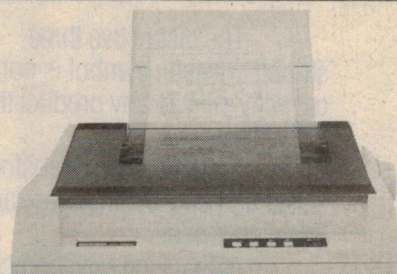

Features of MP-1300AI

- High speed printing (300 cps draft) with lowest noise.
- Superb NLQ printing.
- Variety of characters and graphics.
- IBM® mode and EPSON® mode.
- Built-in Parallel and Serial interfaces.
- Automatic paper loading and ejection.
- Download character setting. (Up to 256 characters.)
- Front panel margin setting.
- Built-in 10 K buffer. (7 K when download characters.)
- Rear and bottom paper loading.
- Optional Automatic Cut Sheet Feeder #MP-13009.
- Easy-to-handle optional 7-colour printing kit, MP COLOR KIT 10. #MP-13005.




**Proud sponsors of the
Sydney Hobart Yacht Race**

Amalgamated Wireless (Australasia) Limited
(Incorporated in New South Wales)

Sydney (02) 887-7111 Melbourne (03) 560-4533 Brisbane (07) 369-9053
Adelaide (08) 297-5887 Perth (09) 321-9334 Canberra (062) 73-1802

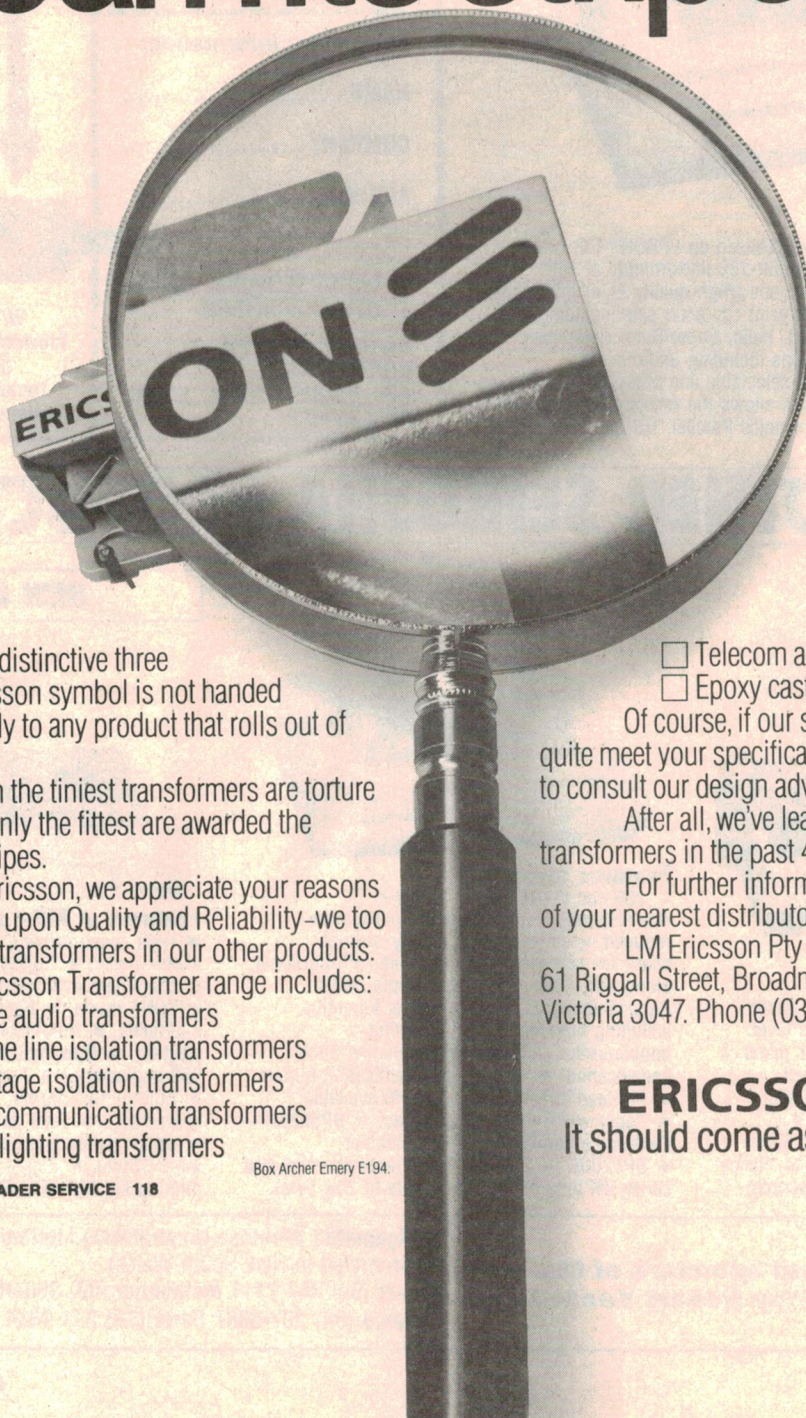Even our tiniest transformer has to earn its stripes.



The distinctive three striped Ericsson symbol is not handed out willy-nilly to any product that rolls out of the factory.

Even the tiniest transformers are torture tested and only the fittest are awarded the Ericsson stripes.

At Ericsson, we appreciate your reasons for insisting upon Quality and Reliability—we too employ our transformers in our other products.

The Ericsson Transformer range includes:

- ☐ Miniature audio transformers
- ☐ Telephone line isolation transformers
- ☐ High voltage isolation transformers
- ☐ General communication transformers
- ☐ Runway lighting transformers

- ☐ Telecom approved transformers
- ☐ Epoxy cast transformers

Of course, if our standard range doesn't quite meet your specifications, please feel free to consult our design advisory service.

After all, we've learned a lot about transformers in the past 45 years.

For further information, or the address of your nearest distributor, please contact
LM Ericsson Pty Ltd,
61 Riggall Street, Broadmeadows,
Victoria 3047. Phone (03) 309 2244.

ERICSSON 
It should come as no surprise.

Optical fibre plant in Victoria

A new plant to make optical fibre cable opened in the Melbourne suburb of Noble Park last April.

The company which built the plant at a cost of \$20m is Optical Waveguides Australia, a consortium of Metal Manufactures, Australia's major manufacturer of cable and other conductors for power and communications, together with AWA, and Corning Glass Works of the USA.

The plant's initial capacity is predicted to be 100,000 fibre kilometres per annum. Its location was selected to be well removed from possible sources of industrial contamination and from major sources of ground vibration such as railways and heavy vehicular traffic.

Central to the operation are the fibre drawing facilities which

are installed in a three storey draw tower. The structure, which sits on an independent foundation of 250 tonnes of concrete, has been tuned to dampen any vibrations which may impair the high quality of the fibre produced.

The plant is expected to have a significant export capacity and to add to Australia's trade in high technology products.

Austral Standard Cable, major supplier of optical fibre cable to Telecom and other industrial users will utilise optical fibre cable manufactured at Noble Park for the Telecom link between Melbourne and Sydney when the new plant comes on stream. Overall, this project will use some 30,000 fibre kilometres of optical fibre.

IF YOUR NEEDS ARE QUALITY ELECTRONIC ASSEMBLY TRY US

Intertronics assembly offers very **COMPETITIVE** pricing on assembly and manufacture due to our **LOW OVERHEAD** costs, labor saving semi-automated equipment, and **COMPUTERISED** management information systems. Intertronics also provides **100% QUALITY INSPECTION**, thus assuring customers of perfect assemblies, everytime.

INTERTRONICS

Provides customers with:

- ★ circuit board assembly
- ★ wire harness assembly
- ★ flow and hand soldering
- ★ mechanical assembly
- ★ automatic wire cutting and stripping
- ★ wire termination and related services

INTERTRONICS

Unit C1, 23-25 Windsor Rd, Northmead
(02) 683-5959

BRIEFS

Australia's largest electronics show

The 1986 Perth Electronics Show will run from July 30 to August 3 at the Claremont Showgrounds in Perth. Exhibitions of audio equipment, computers and peripherals, electronic business equipment, home appliances and photographic tools are what you can expect to see. For further information and details of special travel and accommodation arrangements, contact Chris Gulland on (09)382-3122.

SMPTE conference

The second international conference of the Society of Motion Picture and Television Engineers is to be held from June 24 to 27 at the Sydney Showground. Papers and discussion will cover such topics as film and laboratory technology, television technology, sound in film, television and radio, video and film production. There will also be a comprehensive equipment and services exhibition to complement.

Enquiries about exhibition hours, programme and costs should be directed to SMPTE, PO Box 88, Willoughby, NSW 2068. (02)692-7222.

New pcb holder from Scope

Scope Laboratories has a new tilt and turn circuit board work holder in its Panavise range. The new Model 333 rotates and locks in 45 increments and at four angles. It is adjustable to 200mm in height and comes with a heavy cast iron base with bench mounting holes as an option, and with spring mounted arms for quick load facility. It's yours for \$97. Scope is at 3 Walton St, Airport West, Vic 3042. (03)338-1566.

Promoting Oz electronics in Asia

Scientific and professional equipment trade promotions are to be held later this year in Kuala Lumpur and Bangkok by Aus-trade, the government's successor to the Department of Trade. The South East Asian region has been identified as a priority market by the Australian scientific and professional equipment industry, according to a Trade Department study.

Second chance for failed wafers


A plant which recovers wafers which have been rejected because of faults or errors in manufacture is operating in Riddings in the English midlands. The process used at the plant chemically removes all device structures from the wafer front face and etches out any diffused impurities from the back and edges. The front face is then polished and cleaned.

NOTES & ERRATA


Project 170, Precision CRO calibrator, Feb '85: In order to make the attenuators conform to the front panel artwork, use the following resistor values: R=220R, R18=330R, R22=22R, R23=33R, R29=220R, R30=330R, R34=22R, R35=33R.

The little electric store (Sept '85): The caption of Figure 1 should read: 'The elliptical path of an electron around the nucleus in an electric field'. Figure 2 was placed on the page, rotated through 90°. Alternatively, read 'horizontal' for 'vertical' and 'vertical' for 'horizontal' in the caption.

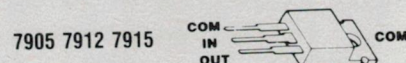1986 ETI reference section, Jan '86 & Starting Electronics 13, April '86: The pin connection package illustrated for the 7900 series regulators is incorrectly labelled. The correct package is reproduced below.



Lamborghini style...

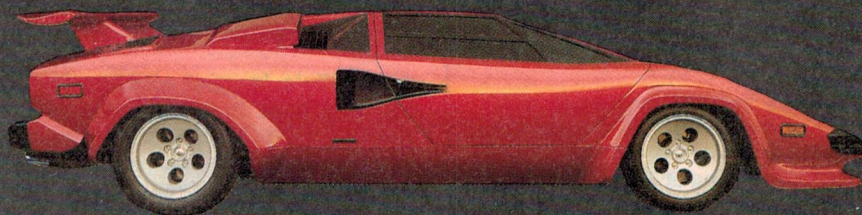

...Alpine performance



ACTUAL SIZE



When it comes to sound "on the move", Alpine technology gives you the choice... cassette or disc. Either way, your music will sound as good on the road as it does in the home.

Model 7273E Cassette Radio. Highlighting: Preset scan tuning • Up/Down seek tuning • Auto metal capability • Dolby* B & C • Tape blank skip • Bi-level • Auto dimmer lighting • Recommended retail price **\$950**

Model 5900 Compact Disc Player. Highlighting: Stabilized mechanism for precision performance • Key off pause • Repeat one or all tracks • Music sensor • Full logic I.C. control • Compatible with Alpine Bi-level cassette radios • Recommended retail price **\$1546**

* Dolby is the registered trademark of Dolby Corporation (USA).



ETI READER SERVICE 154

Another fine product from Anitech a division of the ANI Corporation (Inc. in NSW)


ALPINE

car audio systems

Prices subject to change without notice.

ANI/6242

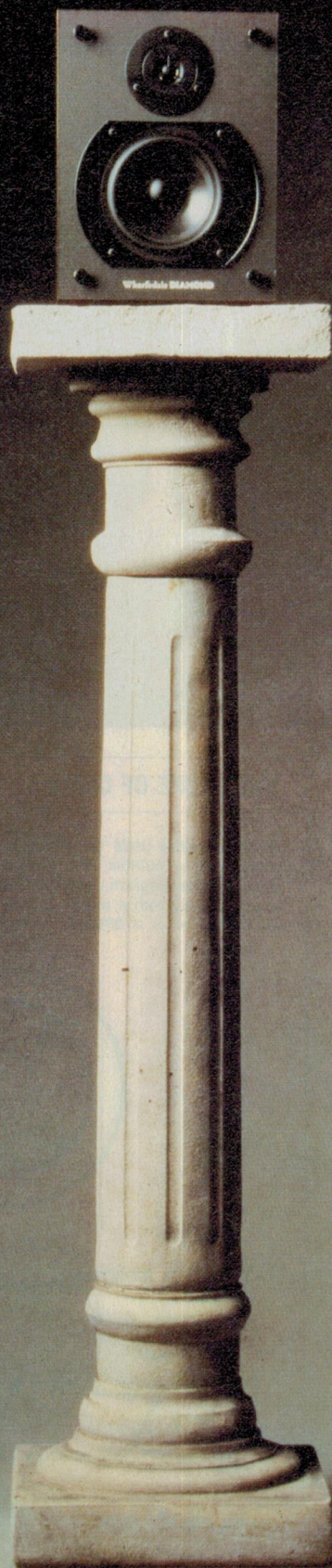The critics have put it on a pedestal.
(But it sounds better on a speaker stand.)




Wharfedale
DIAMOND II

wharfedale/2

Distributed by:
N.Z. MARKETING PTY. LTD.
Phone (02) 938 4077

ETI READER SERVICE 155

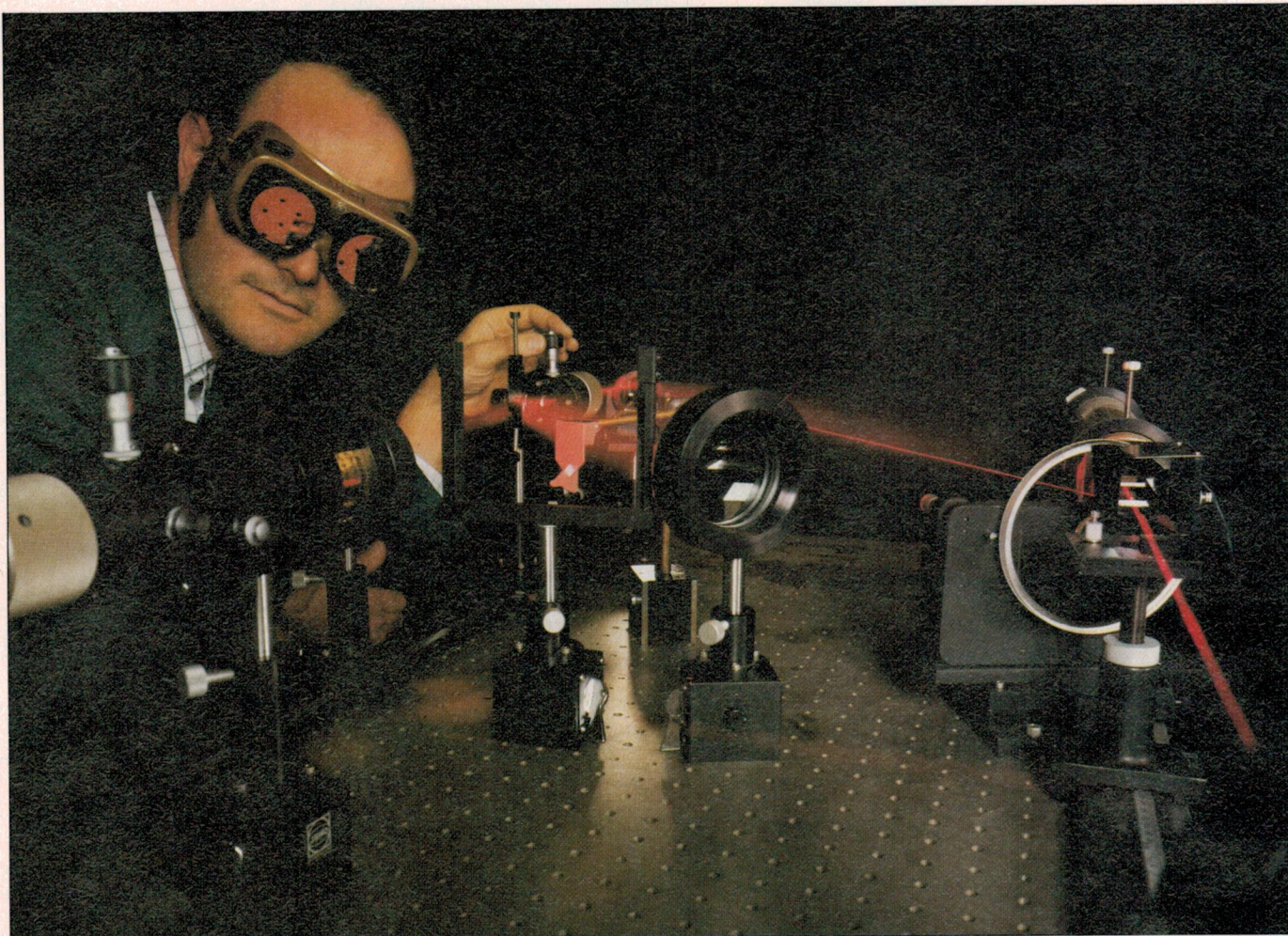

DIFFERENT TYPES OF FIBRE

Fibre consists of a central core surrounded by a cladding. Light propagates down the core. Unless it is launched into the fibre precisely along the axis of the cable, sooner or later it will hit the edge of the core. When it does so, it will be refracted by an amount depending on the difference between the refractive indices of the core and the cladding, and also by the angle at which it hits the interface.

The idea of an optical fibre is that it is possible to arrange things so that the light is always refracted back into the core. If this is done, the light ray will be guided down the fibre for any distance.

Fibres can be divided up depending on how they treat the interface between core and cladding. Single or monomode fibre consists of a very narrow core, of the order of a micron across. Only one ray of light can propagate, hence the name, but its frequency is very high.



Multimode fibre, on the other hand, has a much bigger core, which supports many different routes through the fibre. The frequency has to be lower than with single mode, because of the phase errors in the multipath cable.

Clearly, both cables have advantages. Monomode is good at bandwidth and distance, and so is used by all communications authorities. Multimode has a bigger core, and is therefore handled a lot more easily. It is also cheaper to manufacture. It tends to be used where bandwidth and distance are not problems.

STRUCTURE OF CABLE

A typical cable used in communications work consists of a number of individual fibres. As shown in the diagram, individual fibres are laid in grooves cut into a plastic central core. Right at the centre is a strength member which is

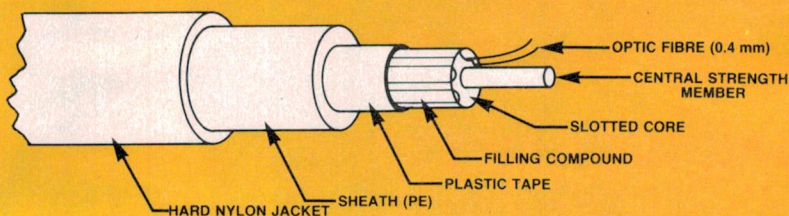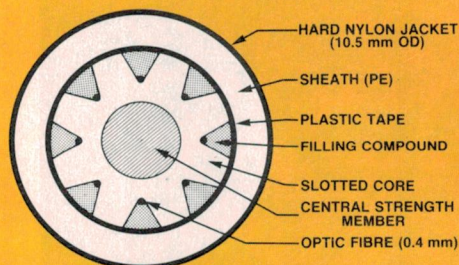supposed to take any strain imposed on the cable during storage or laying. Wrapping around the outside prevents the ingress of moisture.



OPTICAL FIBRES ARRIVE IN THE MARKETPLACE

Optical fibre cables are catching on — though not at the speed of light! Still things are happening fast enough to make one sit up and take note. And Australia can't be accused of lagging behind, as Telecom plans and other companies' uses indicate.

Jon Fairall

AT LONG LAST optical fibre has finally arrived. Between Sydney and Melbourne, giant Telecom tractors are plowing four kilometres into the ground every day. OTC is busy planning its first undersea fibre cable to New Zealand. All over the country, mining and industrial companies are using fibre to control pipelines and conveyor belts. And in the cities, buildings are being wired and rewired to carry light. Everywhere, companies are springing up offering modems, connectors and test gear, service and advice, in fact, all the bits and pieces that go to make up a practical communications network.

The electro-optics industry is expanding at a rate of about 100% per annum, and expansion is predicted to continue at this rate for at least the next few years. Optical fibres have arrived. According to John Wise, of Integral Fibre Systems, a 'tidal wave' of optical fibres is hitting our shores, and today we are only seeing the first swell.

Optical fibres have been around for a long time. The seminal paper on the topic was delivered by Hopkins and Kapay back in 1954. Even further back, Sir Isaac Newton is supposed to have remarked in passing that a beam of light could get 'stuck' in a column of water if the geometry of the situation was correctly arranged.

During the late 50s and 60s scientists and engineers worked on developing the basic parameters of light communications. By the mid 70s, the first experimental routes were being installed, often in third world countries without any existing telecommunications infrastructure. For instance, since about 1980, Brazil has connected all its main cities by fibre.

Today, worldwide, fibre is the glamour connector. In Europe, most of the capital cities have internal fibre routes, and many cities will soon be connected together. In the US, after a slow start, current plans call for a six fold increase in the capability of the network.

In Australia the CSIRO first started playing around with fibre in 1971, and AWA set up a pilot plant to produce fibre on an experimental basis shortly after. Since then the pace of the development has slowly increased and today Australia has a commitment to optical fibre unparalleled in the world.

Bits and pieces


As fibre optics moves out of the lab into the market place it has spawned peripherals that do all the jobs necessary to turn the medium into a viable transmission network. To make it work, users need transmitters

and receivers, devices to quantify the transmission characteristics of the line, connectors and so on.

Transmitters: In practical optical systems these are usually LEDs or lasers. The LEDs are designed to have a high degree of spectral purity, ie, to emit most of their energy in as small a band of frequencies as possible. This makes it possible to tailor the glass in the fibre to the frequency. The ultimate device in this respect, of course, is the laser, which emits a very small range of frequencies.

Receivers: Usually some form of photodiode. Photons fall on to semiconductor material and produce hole electron pairs, and so a voltage. Even greater sensitivity can be produced with an avalanche photodiode, in which the reverse voltage is increased until internal gain takes place due to electron avalanche multiplication.

For the most part, the consumer doesn't buy these devices across the counter. It seems that the most common package for sale is a plastic pack called a transmitter or receiver, consisting usually of pins for electrical connection and a fibre optic 'tail' for optical connection. The package contains the transducer, whatever other electronic interface circuitry is required, and the optical interface that leads into the fibre. ►

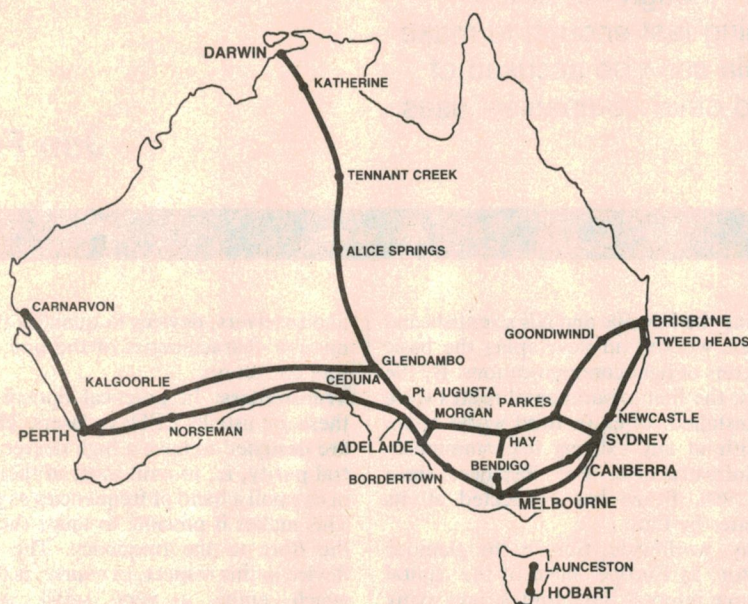

Telecom's proposed optical fibre system.
Top: The cable laying D9 tractor at work.

Test gear: Fundamental to the use of optical fibre is the optical time domain reflectometer. The OTDR maps the way in which light intensity decays in a cable by looking at back-scatter in the cable. It is the OTDR that tells you if signal levels are correct, measures losses across joints and gain in amplifiers.

Another important instrument is the optical power meter. This is connected into the end of the fibre and reveals the incident power level. Usually the machine is calibrated in dB in the conventional way. There is often a filtering provision, to allow the

user to specify the wavelength being received.

Splicers: Joining fibre entails special problems. Firstly, the fibre is extremely small and must be connected with an accuracy approaching a micron. At the same time, special techniques have to be developed to make one bit of glass stick to another. The former problem is being solved with the aid of micromanipulators that allow very precise positioning, usually with the aid of a microscope. The answer to the second problem turned out to be very simple. Heat it and it melts. During a demonstration run


for me by Dr Bob Ayre at Telecom's research laboratories in Melbourne, I saw heat welds being created with losses of less than 0.1 dB.

Connectors: Connectors also need to be positioned with considerable accuracy, although here the acceptable losses are much higher, of the order of a dB or so. In general, connectors are attached to a fibre optic 'tail' in the factory, and joined to the existing cable in the field. Connectors are available from most of the companies that produce or supply conventional connectors. They are even available in Belling Lee and BNC type cases. Some manufacturers are beginning manufacture of large assemblies with multi fibre connectors. Amphenol, for instance, has just released a range of connectors having up to eight cables at once, with a claimed loss of less than a dB. It is also possible to buy do it yourself kits for joining the fibre to the connector. These have higher losses than the factory ones and take time to do, but are often a good temporary solution when one is needed.

Manufacturing

Until this year, the only Australian made fibre was that from AWA. Overseas interests benefitted mostly from the growing use of optical fibres in this country, especially NEC, which won some notable Telecom contracts. In 1985 the AWA pilot plant closed down, pending a reorganisation of the manufacturing industry.

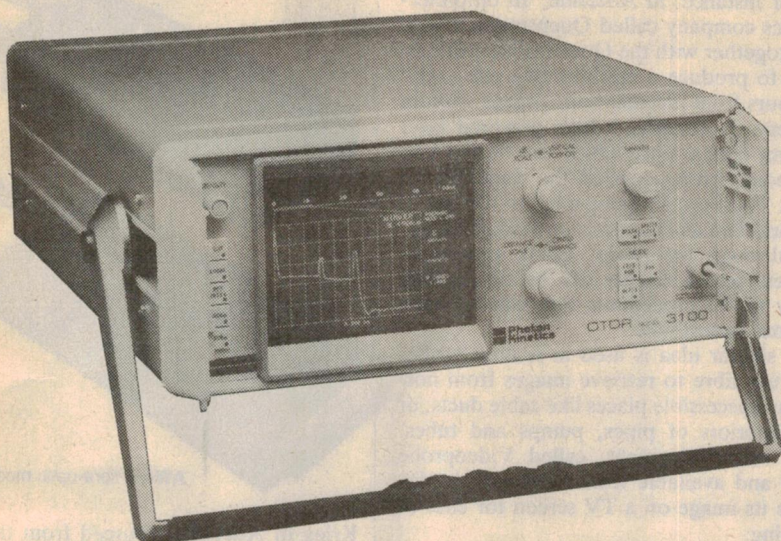Now two large conglomerates have set up in Melbourne to produce fibre for the Australian market. One of these is Optical Waveguides of Australia, a conglomerate consisting of Corning Glass, Metal Manufacturers and AWA. The other company is Optrix Australia, consisting of Dunlop,



Important test gear: the optical time domain reflectometer.

Sumitomo and Pirelli Ericsson. Between the two of them they should provide more than sufficient manufacturing capacity for Australia.

The break up of the suppliers into two conglomerates reflects events overseas, where the Japanese Sumitomo and the American Corning Glass have emerged as the two giants of the market. It also reflects local conditions, where the current marketplace for coaxial cables is dominated by Pirelli Ericsson and Austral Standard Cable, itself part owned by Metal Manufacturers.

Telecom

The biggest user of optical fibre in Australia is Telecom. A glance at the map gives the picture. By 1988 the first route to Melbourne will be finished, as will the Katherine to Darwin section. By the end of the decade, all the capital cities will be connected, and by the end of the century, connected again to provide a doubling of capacity.

This isn't Telecom's first foray into optical fibre. Field trials were conducted at the research labs in Clayton in the late 70s, and the first working route was installed between Darlington Road and Sydney University's computer centre in 1981. Since then, a number of junction routes have been laid between busy inner city exchanges in Sydney, Melbourne and Brisbane.

With the success of these field trials, the confidence of engineers has increased to the point where, in 1982, a decision was made to lay the first really long fibre link, the 975 km route between Sydney and Melbourne. At the same time, fibres are now being considered on all the shorter hauls, to the extent that Telecom is moving to phase

out the laying of copper coaxial cables completely.

The Sydney to Melbourne bearer is something of a show piece for Telecom at its best. It's the phone commission's contribution to the 1988 bicentennial. Ground was broken on the project in Canberra in July 1985, and it is expected to be finished mid 1987.

Engineers are planning on laying four kilometres a day to meet their schedule. The secret of success is a couple of customised D9 tractors, one equipped with a giant spike on the back, the other with a roll of fibre up the front. The spike opens up a slit in the earth as it is pulled forward while the cable-carrying tractor comes behind, dropping cable as it goes.

One of the most difficult problems with laying an optical fibre cable is checking that the cable is not under tension. If it is, micro-cracks in the cable open up over time so that the cable gradually fails. This is avoided in the cable-carrying D9 by having the cable drum mounted on a motor driven shaft. Cable tension is sensed by a lever and the drum drive speeded up or slowed down appropriately.

When the fibre link is completed, it will extend the number of telephone channels to 92,000, versus the 9000 that exist today. Critics of the optical fibre project have contended that this represents a tremendous excess in supply, which might have implications for cost, and thus the profitability of the organisation. However, experience with the introduction of other services suggests that demand quickly increases to fill the extra capacity.

In this case it is suggested that most of the excess supply will be taken up by business users wishing to link computers in Sydney

and Melbourne. Certainly, the prices will be designed to attract new custom. People in the industry do not forecast a price drop; merely that Telecom long distance charges will rise more slowly than the CPI.

OTC

In the international arena the development of optical fibre technology is also having an effect on route planning. After a twenty year dalliance with satellites, the international routes are once again going under the sea. The first major submarine fibre is the trans Atlantic TAT 8, which will be up and running by 1988. Australia will be linked to New Zealand by 1991 and carry on to North America by 1993. The trans Tasman link is likely to consist of six fibre cable operating at 280 Mbs with repeaters every 150 km.

To support its increasing involvement in optical fibres, OTC has set up a research and development division specifically to look into undersea operations. Some of the topics under investigation include laser/fibre combinations at 1550 nm, and the effect of various components in a communications system. This latter project involves a computer model of a bearer, and allows engineers to evaluate the effect of changing individual components on the entire system.

One of the more interesting concepts under investigation is the idea of submarine branching units, which make it possible to join several cables together on the sea bottom. Up to now, all submarine cables have been point-to-point systems. The suggestion is that it should be possible to create branching units and insert them into the cable on the sea bottom. Although the first one has been deployed experimentally in TAT 8, its most obvious application would be in the Pacific Ocean, which has a large number of widely separated population centres around its periphery.

Design questions

So the question is: why is all this work going on, especially when one considers the amount of money being spent on radio systems and satellites at the same time. The answer, of course, is the simplest one of all: it's cheaper.

At first sight it seems incredible that it can be cheaper to plow in a cable right across the country than send the signal up by satellite, or between a few microwave stations. However, as Merve Lette, chief engineer on the Sydney-Melbourne route points out, we are not talking about a few repeater stations, but a large number, and each and every one of them needs power, access roads and so on, all of which cost money.

In satellite systems, the cost of the satellite itself, plus the launch expense and insur-

ance, are also massive constraints. Further, the economics of satellites are made worse by their short lifespan. The first generation of Aussat satellites, not yet completely installed, will begin to expire about 1991. In fact, Aussat has already set up a working party to begin studying the next generation.

None of these costs is going to get better as time passes. However the price of optical fibre is still going down as technology and techniques improve. Telecom's cable laying methods are also becoming more streamlined, with a combination of big tractors and small working parties providing a very cost effective solution.

Another consideration is that, in both cases, satellites and microwave, a comparison must be made on the basis of equivalent information transfer ability. The small 30 fibre cable currently being installed will have half its fibres running 140 Mbits and half running 565, leading to a total of 10,575 Mbits. In the near future this could be increased to 1.6 Gbits per fibre, leading to a total of 48×10^9 Gbits every second, or the equivalent of about 300,000 telephone circuits. Practical microwaves or satellite systems could not approach within orders of magnitude of this figure.

It hardly needs to be said that implementing such a system in copper would need a ridiculous amount of material.

None of this particularly concerns Wayne Knowland, who is heading the Aussat team specifying the next generation of Australian satellites. He sees a communications regime during the 1990s in which the various components of the communications system provide only the services they are good at.

For instance, point-to-point transmission will almost always be done via optical fibre. The exception might be routes where the terrain is so difficult that microwave radio is a better bet. Services into remote areas, and broadcast services from one transmitter to many receivers will almost always be carried by satellite. This implies that many of the broadband applications of Aussat, studio-to-studio TV for instance, or Sydney-Melbourne computer traffic, will run on fibre, while telephone and broadcast traffic into remote areas will go on the satellite.

Other users

The telecommunications organisations are the spectacular users of fibres, and according to some studies, soak up to 80% of all investment dollars in the country, but they are not by any means the only ones, or even the most important when considered in terms of their effect on employment or research. Other companies concerned with smaller applications are beginning to employ many people, and a large amount of engineering expertise is going into some of them.

For instance, in Adelaide, an opto-electronics company called Quentronics is getting together with the Queen Elizabeth hospital to produce a machine that can excise tumours from internal body organs without surgery. It employs a high powered laser and an optical fibre which can be fed into the body through one of the standard orifices. The fibre is then guided to the site of the problem and the excision made by burning through the tissue. Using such techniques, major surgery can be turned into fairly trivial procedures that can be done without anaesthetic.

A similar idea is used in remote probes that use fibre to retrieve images from normally inaccessible places like cable ducts, or the interiors of pipes, pumps and tubes. One such instrument, called Videoprobe 2000 and available from Panametrics, displays its image on a TV screen for ease of viewing.


In Queensland the railways are using optical fibres to run down the side of 1190 km of electrified tracks to provide communications. Previous attempts to provide a communications network have been thwarted by interference from the electrical supplies to the locomotives.

In Sydney, Integral Fibre Systems has been developing a tidy little business finding optical fibre solutions to complex communications problems. Generally, fibre is used in circumstances where its peculiar mixture of characteristics can be taken advantage of. Electrically noisy environments are a natural, so are environments where there are earthing problems. Common applications are for controlling remote motors on conveyor belts in mines, or remote monitoring of programmable logic controllers.

Another increasingly common trend is in providing secure communications routes. Since fibre emits no electromagnetic radiation it cannot be tapped without physically intercepting the cable. Major banks in Australia have been looking at fibre for precisely that reason. Likewise fibre communications cannot be jammed by electronic means, a fact that has not escaped the notice of military aircraft makers. Latest generation aeroplanes routinely use fibres to control the flight surfaces.

For computer users, many companies are now putting together optical modems. A common pattern is to power the modem from an RS232 interface, send the serial information down a fibre and then reconstruct it back to RS232 standard at the other end. This forms a very cost effective solution where the computers are widely separated. It is also used where the small physical size of the fibre is an advantage when compared to an equivalent copper cable. This happens in heavily populated city buildings where duct space is often at a premium.

A typical system is being sold by Mayer

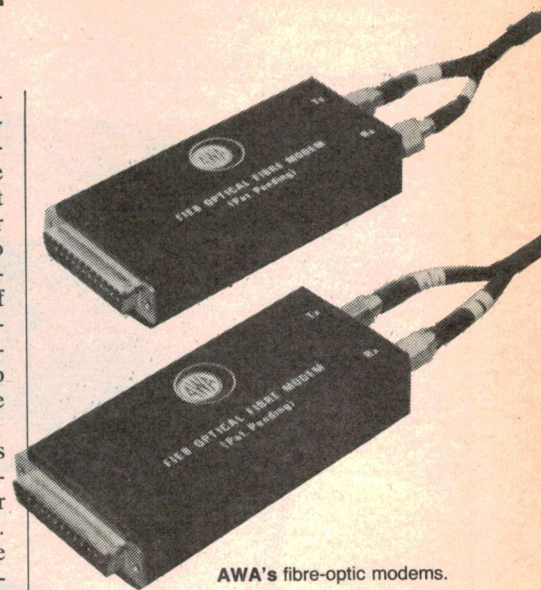

AWA's fibre-optic modems.

Krieg in Adelaide, sourced from the German company Hirschmann. It implements a perfectly standard Ethernet LAN in optical fibre. Without doubt it is more expensive than a copper system, but it allows the system to be spread over a very large geographical distance. If a standard Ethernet system extends over 500 m it requires repeaters. This is extended to 5 km with fibre. Also, annoying problems with ground loops and electronic interference are taken care of.

Future

The future for optical fibre looks extremely bright. Costs continue to drop, both for the manufacturing associated with the cable itself, and for the techniques associated with it. Applications engineers are exploring new ways of using fibres in a variety of settings. Medical uses are possibly the most exciting. One imagines fibre in the future making the surgeon's knife close to redundant.


At the same time, advances in transmission technology will increase its capacity by orders of magnitude without any noticeable increase in complexity. Other things being equal, this should make it even more economically attractive.

Another trend worthy of consideration is the move to light speed information processing. The field of optical integration, in which light is treated just like electrical current and ANDed, ORed and NOTed in physically tiny integrated circuits opens up all sorts of applications which will further boost the importance of light as a communications medium.

In fact, it is probably not putting the case too strongly to say that optics represents the next stage of the electronics revolution. In this context it is a cause for concern that so little thought is being given to it by educators. Like it or not, we are all going to be seeing more of electro-optics in the future. ●

INDEXING P.C.B. HOLDER

LOCKS IN 32 POSITIONS

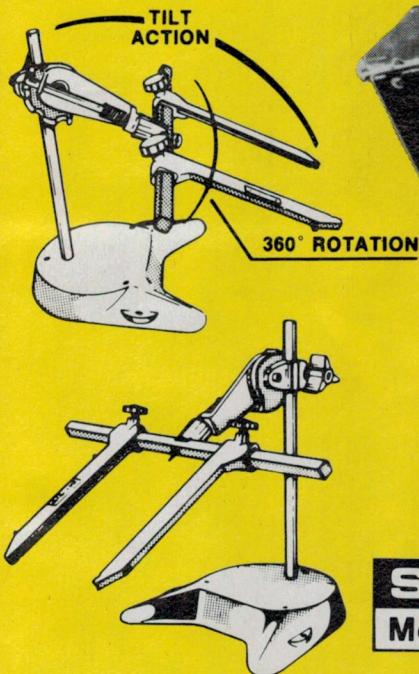

SCOPE
Model 333



TILT AND TURN ACTION – The New Panavise Model 333 rotates the P.C.B. and locks in any of 8 positions in 45° increments. It also Tilts and Locks at 4 angles – 0° (vertical) 45°, 90°, 120° and offers 200mm of vertical adjustment to the work height.

This design is for medium volume production of P.C. Boards and complements the Model 315 P.C.B. Holder which is more suited to the service and repair workshop.

HEAVY BASE – Heavy cast iron base is dedicated to this Model and provides excellent stability and has three mounting holes which permits permanent attachment to a work bench.

QUICK RELEASE ARMS – Spring loaded arms hold boards securely, and provide rapid loading and removal of similar sized P.C.B.'s.

Cross bars are available to 750 (30") for working on large boards or multiple board work, using extra sets of arms.

N.S.W.

CLC Agencies (02) 750 4005
A E Baker & Co Pty Ltd (02) 621 0044 AA26788
J Boomer & Co Pty Ltd (069) 21 4644
Geo Brown (02) 519 5855
Sheridan (02) 699 6912
Martin De Launay Pty Ltd (02) 267 1055 AA26679
David Reid (02) 267 1385

S.A.

AJF Electrical (08) 269 1244
Gerard & Goodman Pty Ltd (08) 223 2222 AA88983

QLD

L E Boughen (07) 369 1277
ECQ (07) 376 5677
Fred Hoe (07) 277 4311
Delsound (07) 229 6155
Dunlop IBC (07) 392 0011 AA41561
St Lucia Electronics (07) 52 7466 AA42883
Magraths (07) 832 3944
Dudley Marshall (07) 779 3855

W.A.

Atkins Carlyle Ltd (09) 321 0101 AA93750
Pro Spec (09) 362 5001

VIC.

Aust School of Electronics (03) 523 5622
Ballarat Electronics Supplies (053) 31 1947 AA37435
Ellistronics Pty Ltd (03) 561 5844 (03) 602 3282
Radio Parts Group (03) 329 7888 (03) 211 8122
Teleparts Investments Pty. Ltd. (052) 21 7085
McGraths Electronics (03) 347 1122 AA31001
R D Irving (03) 489 8131
Electrotool (03) 848 1045
Mektronics (03) 690 2650

TAS.

GHE Electronics (002) 34 2233 (003) 31 6533




SCOPE

BOX 63 NIDDRIE,
VIC. 3042
TEL: (03) 338 1566
TLX: AA38318

FOR A FREE CATALOGUE SEND YOUR NAME AND ADDRESS TO: FREEPOST No.2, SCOPE LABORATORIES P.O. BOX 63, NIDDRIE, VICTORIA, 3042 AUSTRALIA
No Stamp Required

ETI READER SERVICE 156

JMS 194

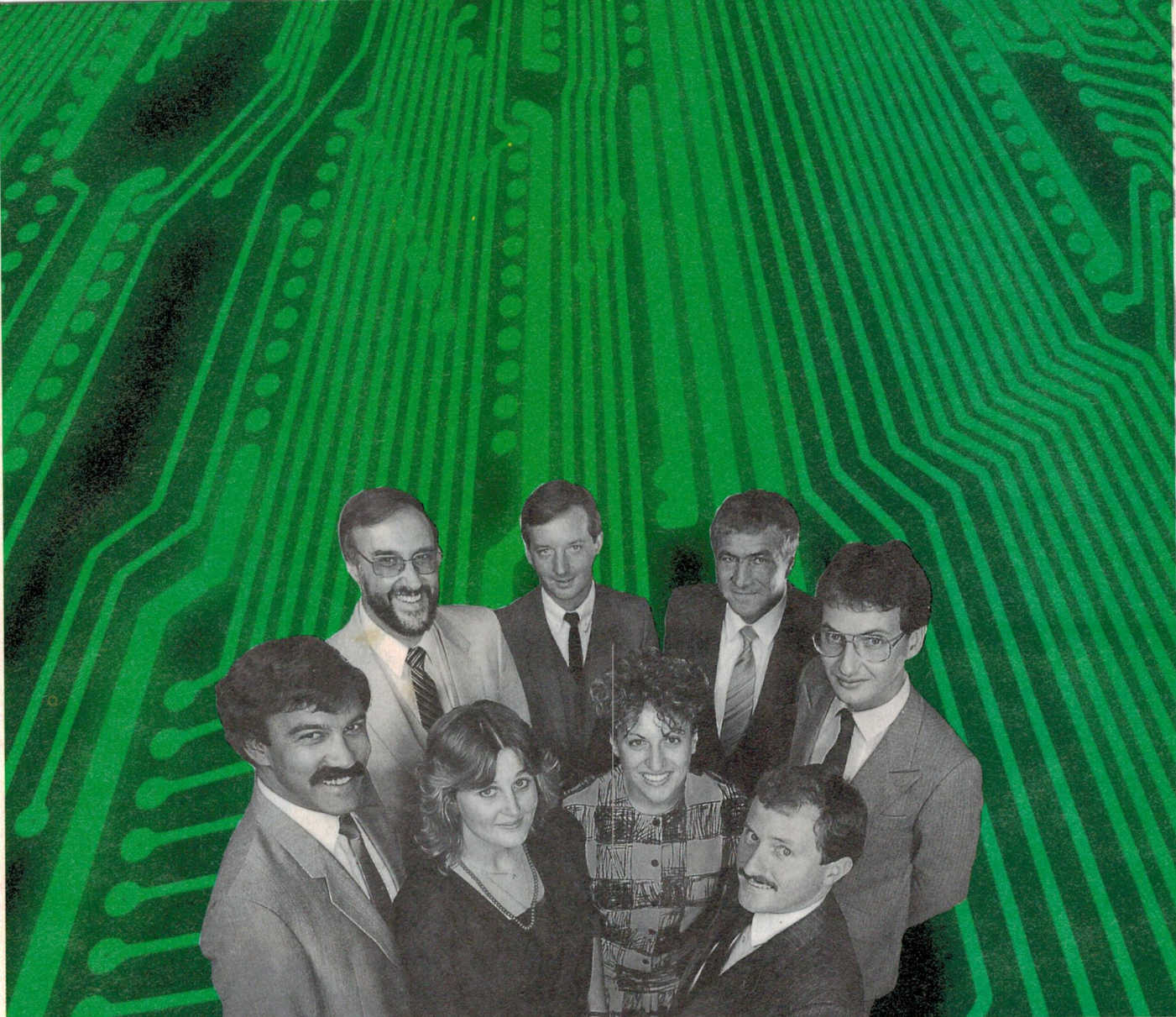


UNITED NOTIONS.

At Printronics, innovative teamwork has always been the key to our technological leadership in printed circuit boards.

Now this has acquired an international aspect because we have added highly qualified personnel from major overseas PCB production centres to our team of skilled scientists and technicians.

Whatever *your* notions about your PCB needs we'd like you to unite with us at the outset of your project. We've truly a world of experience to offer and can put you on the right track to solve problems and minimise costs at the planning stage.

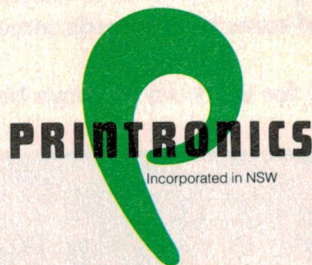Our range includes single-sided to multilayer boards, in reflowed solder or dry film solder mask with black oxide finishes. Fine line technology can be incorporated in your design and you can specify UL, MIL and ASA.



Yes, I would like to receive the latest information on your new developments in PCB's and how they will benefit my business.

NAME _____
 POSITION _____
 COMPANY _____
 ADDRESS _____

 POSTCODE _____
 TEL No. _____

ETI READER SERVICE 157

SYDNEY (02) 816 5066 POB 389, Ryde, NSW 2112 Telex 22965 FAX 817 5687

MELBOURNE (03) 720 3433 17 Scoresby Rd., Bayswater, Vic. 3153 Telex 35102



INSIDE THE BOARD SHOPS

Like everything else, printed circuit board manufacture marches forward, dragged by the demands of the industry it serves, lured by advances in its own techniques.

Jon Fairall

SLOWLY, MORE SLOWLY than many would have liked and most would have predicted, the future is catching up with electronic manufacturing in Australia. A whole swag of techniques and equipment is now lurching into place on assembly lines. In factories big and small, the dirt and the fumes and the noise are being replaced by computers and automatic machines. In the electronics industry at least, the day of the process worker is drawing to a close.

At the centre of the changes is the circuit board. Its manufacture used to be the seamy side of the industry, a hot house of bad smells and funny rashes for the careless. That's all going. Also changing is the way manufacturers put components into the boards. It used to be a job prized by migrant women, (the 'girls' in factory managers' lexicon). Now the machines beat fingers no matter how deft, and they don't make mistakes. Even the type of circuit boards are

changing, as surface mounting comes into view. Finally, the technician who used to sit at the end of the line testing everything is disappearing; replaced by automatic test gear.

Economics

Why? As with all social processes the answer is a complex amalgum of political, economic and technological answers. Manufac-

P.C.B. FILMWORK

Photoplotting, Photo Mask Generation.
Quest or Gerber output from
your C.A.D. system.

Large range of images available.
Accept data on many floppy disk formats
1/2-inch mag tape or paper tape.

Photographic reductions, duplication,
colour separation, pad
pattern duplication and solder mask
expansion. Ground plane
reversal and insertion.

**LARGEST INDEPENDENT PHOTOTOOL
SOURCE IN AUSTRALIA**

PRECISION GRAPHICS PTY. LTD.
Unit 15, 31 Waterloo Road,
North Ryde 2113
Telephone (02) 887-2648

ETI READER SERVICE 158



TENNYSON GRAPHICS

**Tennyson Graphics can do your photoplotting
with the speed of light.**

Tennyson Graphics are Australia's only
company with state of the art laser photoplotting
and computer graphics.

So we can photoplot artwork masters of your
printed circuit boards with higher speed, higher
resolution and higher accuracy than anywhere else
in the country.

You can even choose your own non standard
apertures on our Scitex Response 280 System. It can
also do step-and-repeat and nesting up to 1000 mm
x 1850 mm.


And of course we can accept data on tape or
floppy disk in industry standard Gerber format.

Tennyson Graphics will be happy to give you the
full story if you phone on (03) 579 0424.

TENNYSON GRAPHICS
A DIVISION OF REPROCART PTY LTD
993 NORTH ROAD
MURRUMBEENA VIC 3163
TELEPHONE (03) 579 0424
TELEX 34457

ETI READER SERVICE 159

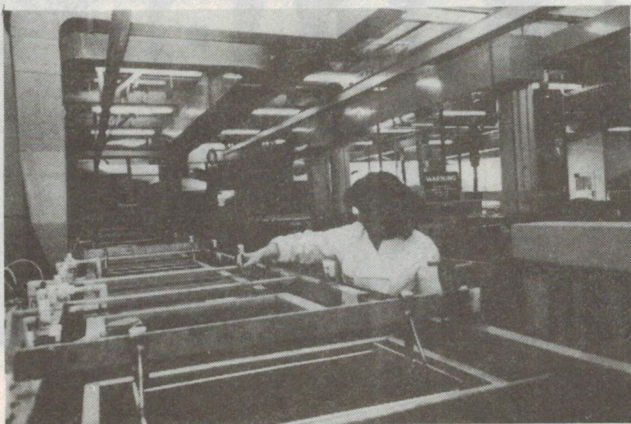P.C.B. ELECTROPLATING PLANTS FOR INDUSTRY



**ELECTROLESS COPPER AND ELECTROLYTIC
COPPER/TIN LEAD LINES DESIGNED AND
INSTALLED BY THE EVERSHARP ENGINEERING
GROUP FOR S.T.C. PTY. LTD. SYDNEY.**

The Eversharp engineering Group have collectively over 60
years experience in specialist automatic electroplating plant
engineering. We offer a comprehensive design and
installation service for all industrial engineering plant
requirements in conjunction with sequential processors
and programmable logic controllers.

We combine engineering service as a 'TURNKEY'
operation or act as management consultants to design and
supervise construction or a combination of both to
customer requirement.

BENEFIT OF THESE FEATURES

- ★ Modular construction, maximum flexibility with
provision for changes and self-installation.
- ★ Conversion compatibility for conversion of existing
manual lines, easily extended for increased output. All
work handling and location independent of process
tanks.
- ★ Reduce unit costs and improve quality. Automatic sys-
tems are more accurate and efficient.
- ★ Reduce effluent problems. Accurate control of drainage
and rinsing reduces 'carry over' of chemicals and
environmental problems.

**EVERSHARP
ENGINEERING
GROUP PTY. LTD.**

110A Victoria Road, Drummoyne, NSW 2047
Telephone (02) 819-7442/6080 (03) 543-2022
Telex AA70842 ERNEX — EVSP

ETI READER SERVICE 160

turing industry in this country has been through hard times. Since the Whitlam government lifted the tariff barriers in the mid 70s it's been out of fashion. Perhaps the nadir was reached when Barry Jones, Labor's mercurial Science Minister, published his influential *Sleepers Awake*, in which he argued that the future of Australia lay not in manufacturing, but in service industries.


The wheel turns. The current economic wisdom is increasingly that the future belongs indeed to manufacturing. Not in the old way though. Not hidden behind trade barriers, not relying on 20 year old processes, but efficient, lean and hungry: competitive with anyone in the world. Interestingly, Jones and Trade, Industry and Commerce Minister Button have been two of the strongest converts to the new economic religion.

Daily we see the steady debunking of the twin pillars of the Australian economic system: mining and farming. In the early 80s the mining boom went bust; today good hearted ladies in the cities are making up food parcels to send out to farmers who can't make enough to pay their own food bill. It's rather reminiscent of the days when Australians, with infinite condescension, sent food parcels to Britain. It's a far cry from the days when the farmers carted swill to the pigs in the boot of a Mercedes Benz.

New techniques

So the new saviour is sophisticated manufacturing. Not salt of the earth stuff, grubbing around in the bowels of Dante's inferno, but computer aided, clean room, anti-static, high quality, very clever manufacturing. New technologies are making it possible to make fundamental changes to both the structure and the competitiveness of Australian electronic manufacturing.

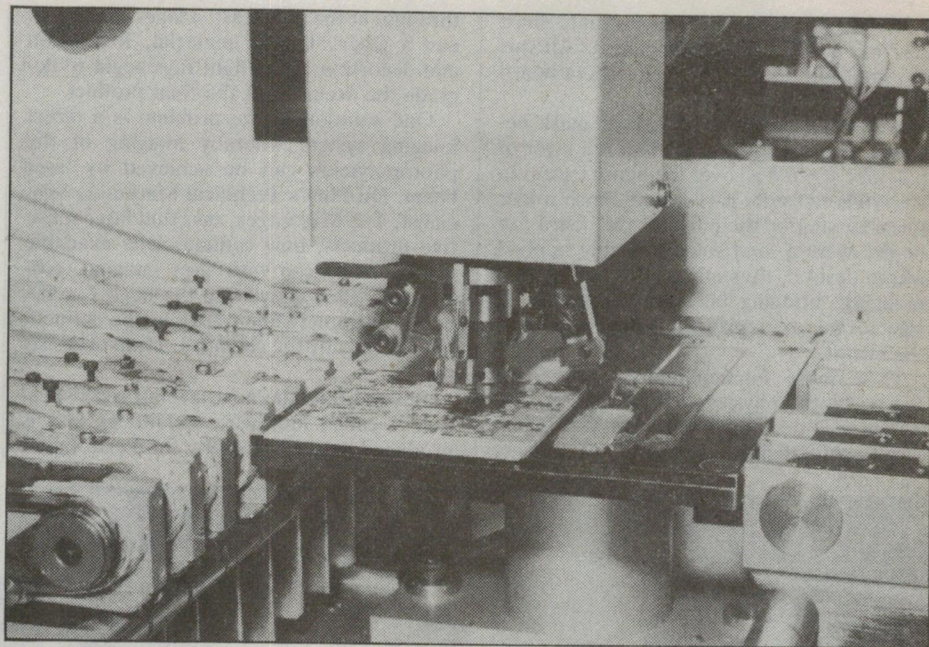From the beginning to the end of the manufacturing process, processor-based equipment is aiding workers and adding to the value of the final product. At the front end, computer aided design equipment is helping workers to design boards (a follow up article next month will look at computer aided design in some detail). The output from CAD machines is used to control



A pick 'n place machine used for surface mounting components (courtesy Philips).

other machines further down the line in a way that can make it possible to build a complete board almost without human intervention.


For instance, numerically controlled drilling machines are now almost standard equipment in board shops around the country. They have one or more drill heads controlled on two axes by computer-guided stepper motors. The computer divides the board up into a grid with 0.1 inch centres, then positions the head over any intersection on the grid with an accuracy measured in tens of thousandths of an inch.

Meanwhile, increasing board packing density (the number of components per square centimetre) is prompting designers to demand narrower tracks. Narrow tracks can be laid more easily between pins, making it possible to route them more efficiently. At the same time, the components themselves are needing less and less current to perform their functions. As a result, the current carrying capacity of the tracks (proportional to their cross sectional area) is less critical.

Until fairly recently, track sizes varied between a millimetre and perhaps 0.5mm, using screen printing techniques. Today, sophisticated shops are using dry film techniques, in which the board to be etched is laminated to a layer of organic polymer which acts as a resist. According to Michael Brinsden, Managing Director of Printronics, a Sydney based board shop, these techniques allow track widths of 0.18mm. This allows two tracks between pins routinely, and three with special care.


To go beyond this level of precision, however, is very difficult. According to the Du Pont company, which makes many of the photographic polymers used in imaging circuit boards, the practical limit of photographic techniques is about 0.1mm. Most manufacturers would be less optimistic.

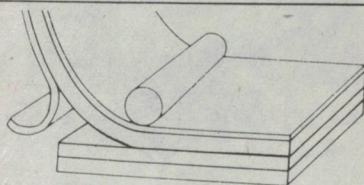Problems start to manifest themselves in the material used and the manufacturing environment. For a start, the board material itself must be built to a fine degree of tolerance. A 0.25mm hole in the copper, for instance, is insignificant at millimetre technology but will cut narrow tracks. Cleanli-




The resist is applied by heat and pressure to the clean substrate surface.

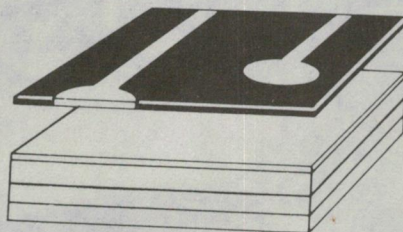The dry film process. (Courtesy Du Pont.)



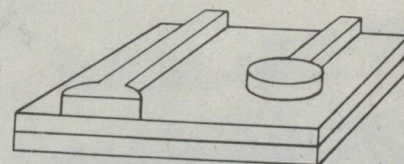It is polymerised under the clear area of the photo-tool.



During development unexposed resist is washed away leaving the required image.

FEATURE

ness becomes extremely important, since dust mites will destroy the board. All this has implications for the economics of board production.

Another factor is that a solder mask becomes essential. A solder mask is a layer of polymer applied all over the board except in areas where solder is required. Since solder does not stick to the polymer the board can be pre-wetted, and solder reliably applied where desired, thus eliminating, or at least reducing, bridging between the tracks. It also serves as a protective layer for fine trackwork.

Even more fundamental problems are caused by the physics of the situation. For instance, in the imaging process, it is necessary to shine light on to the board, passing

through, at the very least, a layer of artwork and a layer of resist material. Refraction and distortion of the light rays begin to degrade the accuracy of the final product.

One solution to the problem is a direct imaging system whereby imaging of the photopolymers can be achieved by laser beam. Du Pont's Technical Marketing Specialist, Ted Messenger, says that laser sensitive products, now commercially available can be interfaced with laser imaging technologies, thus alleviating the need for artwork. Extremely fine tracks can be defined, limited only by the chemical action of resists and so on.


Beyond this, the next level of sophistication is called multiwire technology and is produced under licence by the Perth based

Circuit Technology. Multiwire involves burying fine threads of copper in the molten epoxy of the board during the curing process. It has obvious problems in terms of flexibility of use, but it does have the tremendous advantage of allowing extremely high board density.

The other way to achieve great density is through multilayer boards. Current state of the art is probably at Morris Productions in Sydney, where 14-layer boards for the FA-18 radar are being produced under an offset agreement for Hughes Aircraft.

Stuffing

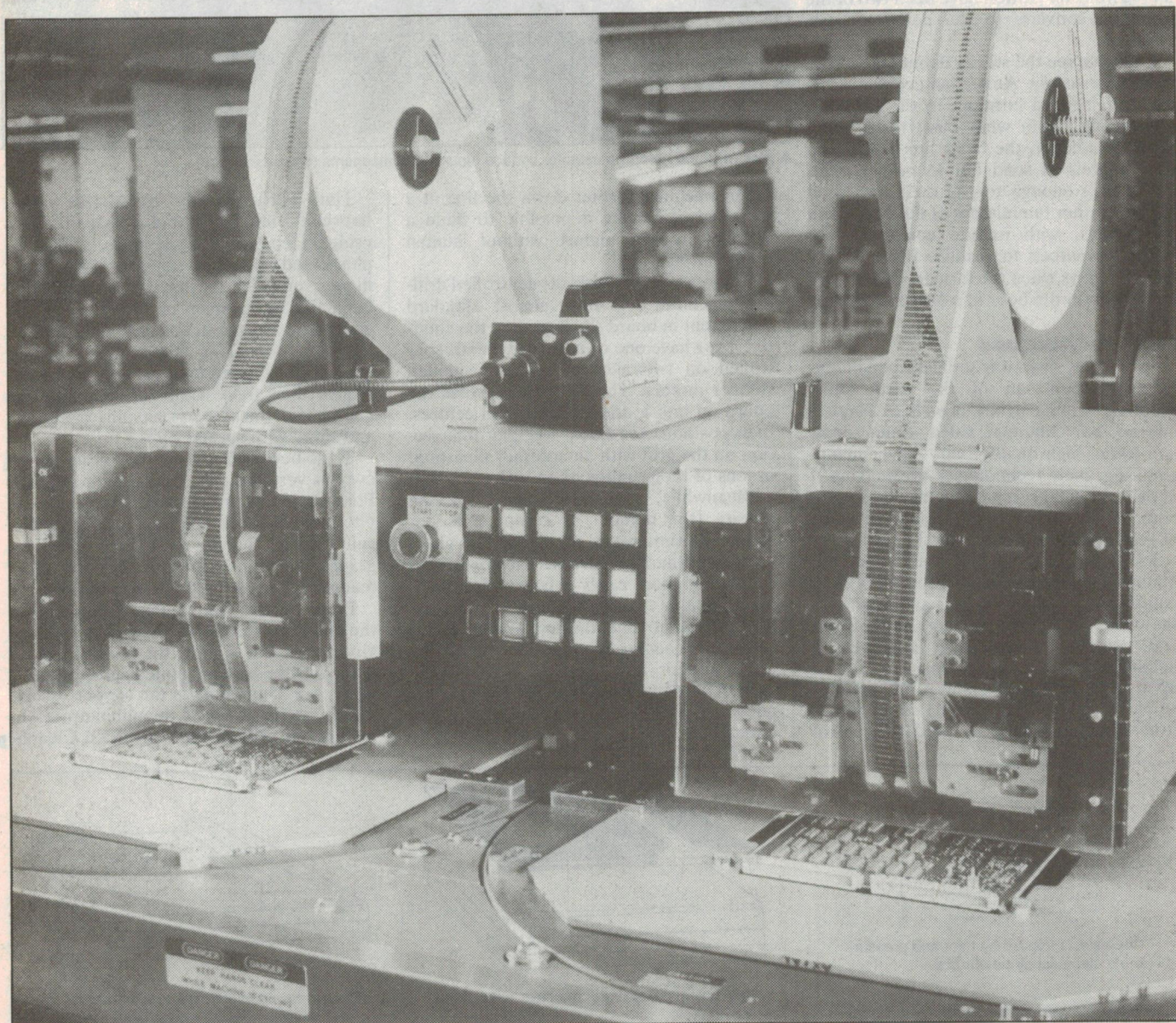Probably nowhere are changes occurring at a greater rate than in the board stuffing part of the industry. Here automation is



A computer controlled automatic insertion machine for axial lead components (courtesy STC).

taking the sweat out of virtually every process in the shop. At centre stage are the automatic insertion machines, most notably from Dynapert, a US manufacturer.

Insertion machines for boards come in three types: axial, radial and DIP, depending on the type of component to be assembled. Axial components require a machine to bend the leads so they are parallel to each other. They need a different type of machine from radial components. DIP insertion is usually done using a vacuum to lift the chip and place it in the correct position.

It goes without saying that all these machines must work to a remarkable degree of accuracy. This is provided in the first place by computer control. Usually, the same program as that used to control the drilling machine is used in the insertion machine as well.

There are large numbers of these machines already in service in Australia. Indeed, most board shops seem to have made some concession to this level of technology. However, even before it is fully in place, it is being overtaken by surface mounting.

Surface mounting

Surface mounted devices (SMDs) do not have leads. Instead they are glued to a circuit board and then pins are soldered to the tracks. The process of mounting the boards has to be done automatically by so called 'pick 'n place' machines because of the extremely small size of the components and the difficulty of identifying them.

There are a number of advantages to surface mounting: small board size, and thus improved economic and electrical characteristics for instance. Also, all SMDs can be mounted by one machine, thus reducing the capital costs involved in setting up shop.

This saving can be considerable. While Dynapert sells inserters of one type or another for upwards of \$100,000, the same company sells pick 'n place machines for \$55,000. Since three inserters are needed to fully automate a line, the real saving is considerable.

However, manufacturers are only slowly coming to the party. Mark Riley of Penn Central, which sells Dynapert machines in Australia, sees the problem lying with many manufacturers questioning whether the possible market in Australia justifies the capital outlay. Says Michael Brinsden of Printronics: "We must be careful of climbing on to a technical bandwagon," and points to the high price of surface mount components compounded by supply problems.

Others attribute the slow start of SMDs to simple conservatism rather than any rational consideration of the economics of the situation. Colin Casey of Royston Engineering says "the full impact of SM technology is still two years away". This reflects the situation in the US where it is still drag-

Ian J. Truscott's

ELECTRONIC WORLD MORE & MORE

People are discovering us each week. Both the home enthusiast through to the small manufacturer.

★ ★ ★

COMPONENTS • TOOLS • KITS

In any quantity, buy one, or one thousand, we're happy to oblige

SCHOOLS • CLUBS ETC.

Inquire about our bulk discount deals

Save yourself a trip to the city - come to

**30 LACEY STREET
CROYDON**

OR PHONE

**(03) 723 3860/
723 3094**

Mail orders welcome.

ETI READER SERVICE 161

**P
a
n
e
l
p
r
i
n
t**

High Quality screen printing of

instrument panels,
chassis and
lexan labels.

Fast prototype single and double-sided printed circuit boards.

PHONE: 725-0444

**Panelprint P/L
34 Taylors Road
Croydon, Vic. 3136**

ETI READER SERVICE 160

IN-HOUSE PCB Equipment Materials

UV MATERIALS

3M Scotchcal Photosensitive

		Pack Price	
8007	Reversal film	\$35.40	\$47.60
8005	Black/Aluminium	\$64.95	\$74.75
8011	Red/White	\$58.50	\$67.30
8013	Black/Yellow	\$58.50	\$67.30
8015	Black/White	\$58.50	\$67.30
8016	Blue/White	\$58.50	\$67.30
8018	Green/White	\$58.50	\$67.30

AUSTRALIA'S LARGEST STOCKISTS

UV PROCESSING EQUIPMENT

KALEX LIGHT BOX

- Autoreset Timer
- 2 Level Exposure
- Timing Light
- Instant Light Up
- Safety Micro Switch
- Exposure to 22in x 11in

\$499.00 + ST

KALEX "PORTU-VEE"

- UV Light Box
- Fully Portable
- Exposure to 10in x 6in

\$175.00 + ST

PCB PROCESSING

KALEX ETCH TANK

- Two Compartment
- Heater
- Recirculation
(by Magnetic Pump)
- Two Level Rack
- Lid

\$595.00 + ST

RISTON 3400 PCB MATERIAL

SIZE INCHES	SINGLE SIDED	DOUBLE SIDED
36 x 24	\$67.50	\$82.50
24 x 18	\$33.75	\$41.25
18 x 12	\$17.00	\$22.00
12 x 12	\$11.50	\$14.00
12 x 6	\$6.00	\$7.50

All prices plus sales tax if applicable.

KALEX 40 Wallis Ave.,
East Ivanhoe 3079
(03) 497 3422
497 3034
Telex AA 37678

9.30 a.m. - 4.30 p.m.
Monday-Friday



ELECTRONIC COMPONENTS & ACCESSORIES
• SPECIALIST SCHOOL SUPPLIERS

ETI READER SERVICE 162

FEATURE

ging its heels. He argues that supply and cost will take care of themselves as demand in Japan continues to increase.

One rather interesting variation on this theme is offered by the German company Schlup, represented here by Meltec, which offers a semi-automatic facility. The dispensing of glue and components is done under operator control. According to Meltec's Ian Mathieson, this saves considerably on initial capital costs, and makes it possible to change rapidly from one board to another.

There is another reason for hesitancy by some manufacturers, and that is the impermanency of the SMD technology. Many see SMD as a transitional technology on the way to a further level of integration called chip-on-board. With chip-on-board, the silicon substrate is actually bonded directly to the board itself, connections are made with gold-thread, and the whole unit covered in protective plastic. This type of technique is already tried and proven in hybrid manufacture, however, the economics of automatic insertion technology will have to improve considerably before it becomes viable in most areas.

Soldering



Accompanying the move to automatic insertion is a parallel move to more efficient and economical soldering techniques. Irrespective of technique, all soldering machines on the market, and there are many, come as a 'black box' in which you put the boards in one end, and they come out the other end with components correctly soldered.

The first and still the most common technique is wave soldering. In this system the board is pulled over a bath of solder by a conveyor belt. In the centre of the bath is a wave, created by pumping solder up from the bottom of the bath. The solder in the wave washes over the bottom of the board and sticks the components down.

Over the years an enormous amount of research has gone into examining the exact geometry and number of waves in the bath, with a view to increasing the reliability of the joints and reducing bridging problems. The latest development from Hollis in the US is the hot air knife. This directs a blast of hot air at the bottom of the board as it emerges from the wave, hopefully blowing away any solder that might form icicles or bridges.


Typically, computerisation is also at work on the solder wave machine, controlling all the important parameters in the process, such as the solder temperature, flow rate, board speed and so on. The beauty of this process is that it is now possible to guarantee a consistent result right through the job.

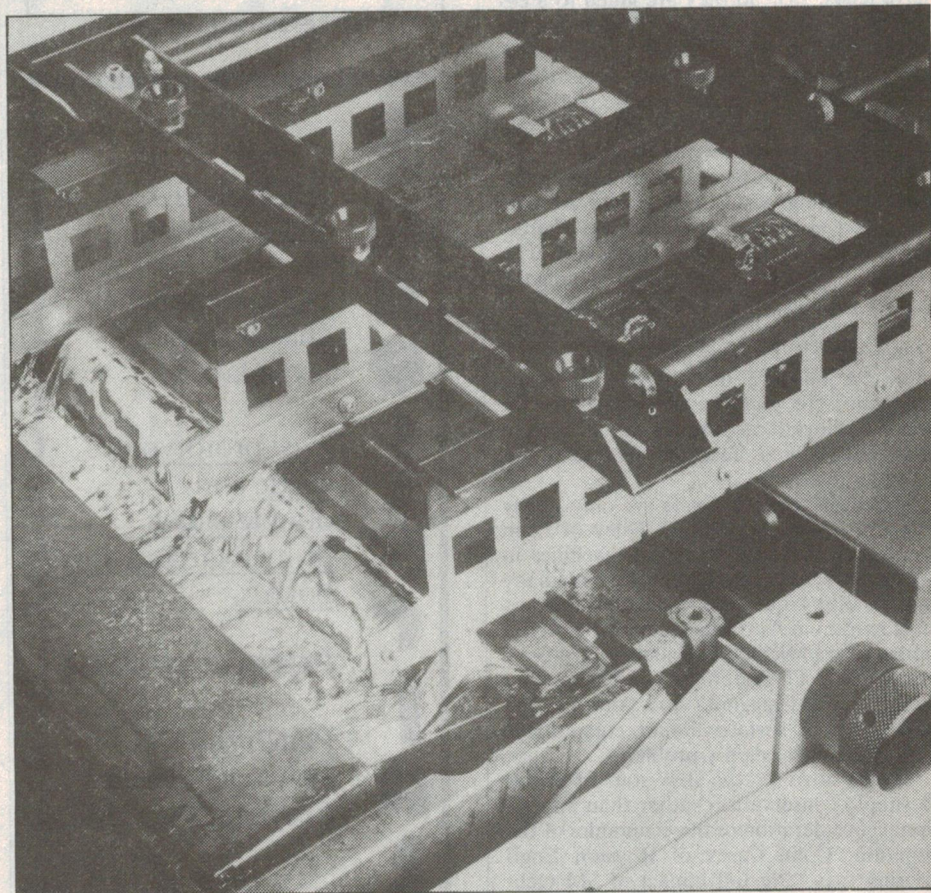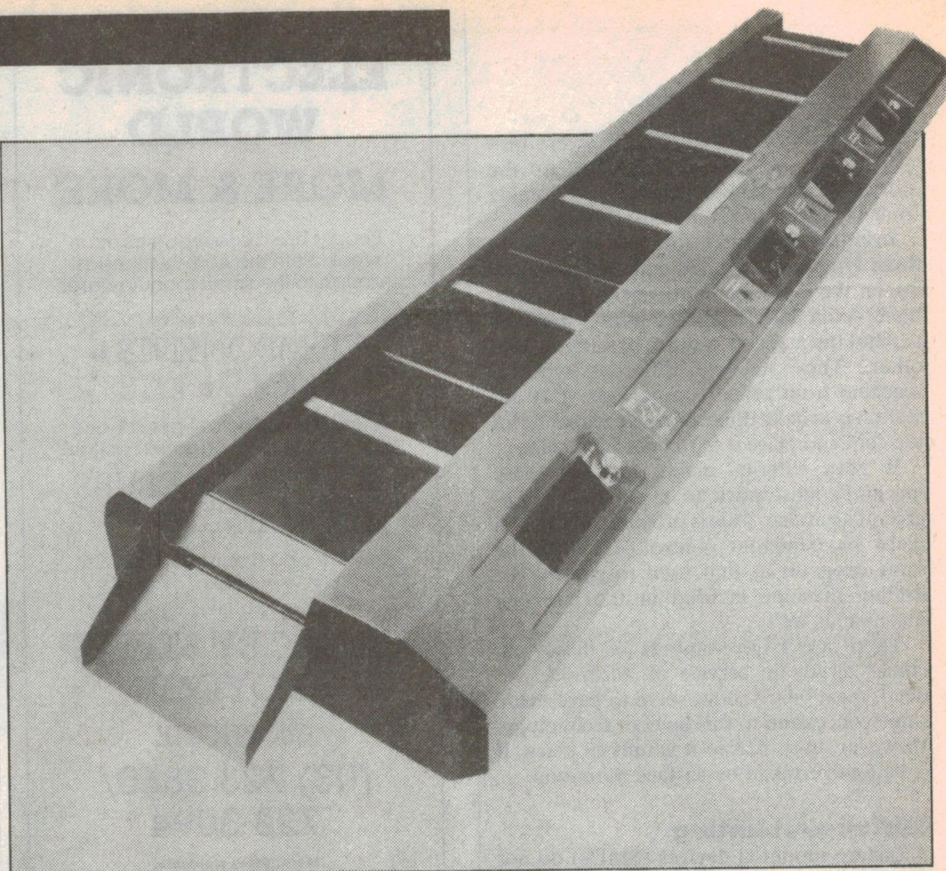But now the solder wave type machine is under threat. The new challenger is reflow



Wave soldering. A board carrier finishes its run over the wave of solder. **Above:** The alternative to wave soldering is the belt reflow machine.

SURFACE MOUNT SOLDERING PROBLEMS SOLVED

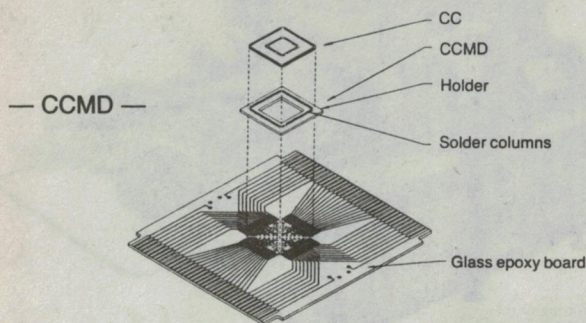

CHIP CARRIER MOUNTING DEVICE

Leaders in materials' science technology, Raychem now offers a unique system for users of leadless-chip carriers who wish to utilise low-cost epoxy resin glass boards...

- Dissolvable Connector
- Simple Installation
- 1000 g survivability — MIL-STD-202

Raychem also continues to offer a whole range of circuit board accessories including:

- Automated Solder/Sleeve Systems
- PTC Current Limiters
- Heat Shrinkable Products
- Computerised Marking Systems
- Zero Insertion Force Connection Systems

... and much more...

For details contact Frank FitzGerald, Electronics Manager,

Raychem (Australia) Pty. Ltd.

14 Pike Street, Rydalmere 2116 Telephone (02) 684-1055

ETI READER SERVICE 163



PRINTED BOARD
DESIGN

CAD BUREAU SINCE 1981


SURFACE MOUNT

FINE LINE

MULTI-LAYER

DOUBLE SIDED

SINGLE SIDED

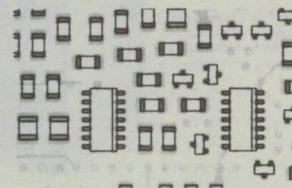

WE CAN PROVIDE ALL THE
ABOVE ON OUR CAD SYSTEM

ELECTRI-BOARD DESIGNS P/L

PCB DESIGN SINCE 1972


15/31 WATERLOO ROAD, 02-888 6925

NORTH RYDE NSW 2113. 02-888 3929

ETI READER SERVICE 165

MENTRON

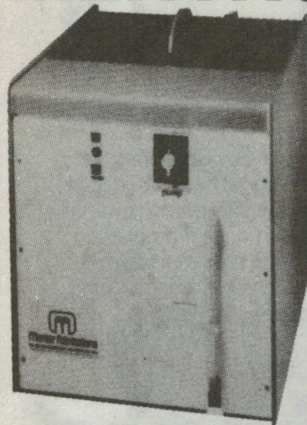Machinery for the
development and
processing of Small
Run, Sensitive Coating P.C.B.'s




Mentron spray developer 300 N.S.D. Designed to spray-develop photo sensitive coatings requiring alkali based chemistry including Du Pont Riston* 3000 series. The unit features a sturdy magnetic drive pump that feeds four spray nozzles in each side manifold. Sprays are controlled by a timer.

*Du Pont registered trademark.

MACHINERY AVAILABLE IN TWO SIZES WITH CAPACITY FOR 300mm AND 450mm P.C.B.'s. **ALSO AVAILABLE** ★ EXPOSURE BOXES ★ SPRAY RINSE ★ SPRAY ETCH ★ AGITATION ETCH ★ STRIPPING MODULE ★ TINNING TANK. **EQUIPMENT TO SUIT ALL LEVELS OF P.C.B. MANUFACTURE, INDUSTRY AND EDUCATIONAL ENQUIRIES WELCOME.**

KEMPROOF INDUSTRIES PTY. LTD.
14 Inman Rd., Dee Why, N.S.W. 2099
Phone (02) 982-4311. Telex 22005

ETI READER SERVICE 164

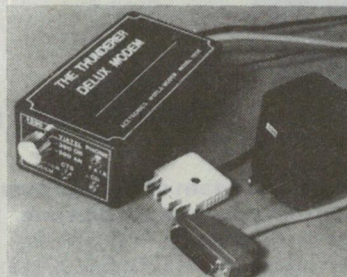

THE THUNDERER MODEM

"The mini-sized modem with a maxi punch"

Why mess around with 300 baud babies? This has everything you will need for a lot less than similar modems.

Just look at the features!

Viatel system at the flick of a switch. • 75/1200 (Equalized), • 1200/75 (Equalized), • 1200 HD (Half Duplex), • 300 Baud — Answer, • 300 Baud — Originate, • Switched Bell System, • Simple connection, • Full instructions, • Small size, • Everything supplied and thundering to go!!!


We're so confident of the quality of our product we are offering a 2 year guarantee, free of labour and part costs. **Introductory offer this month only \$195.00**

usual price **\$230.00 P&P \$9.00**


RS 232 to PIO Converter. Convert RS 232 Port to a Centronics port. No external power required. Accepts 300 to 4800 board rates. RS 232 lead and plug wired in and Centronics lead wired in. Fully assembled **\$55.00. \$4.00 P&P.**

Enquiries: **ACETRONICS PCBs**
112 Robertson Rd, Bass Hill
2197. (02) 645 1241.


ETI READER SERVICE 166

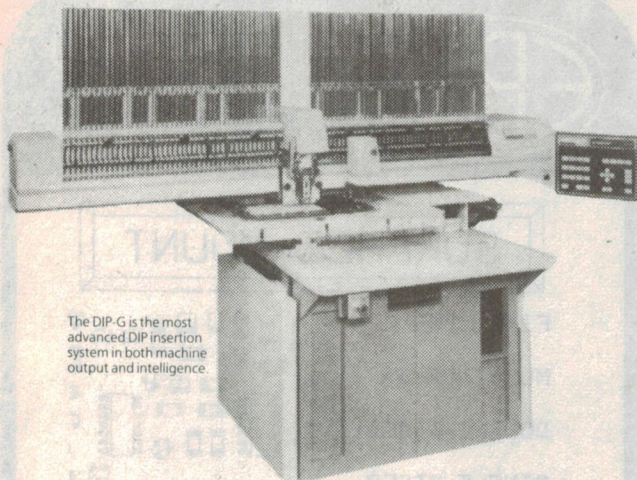

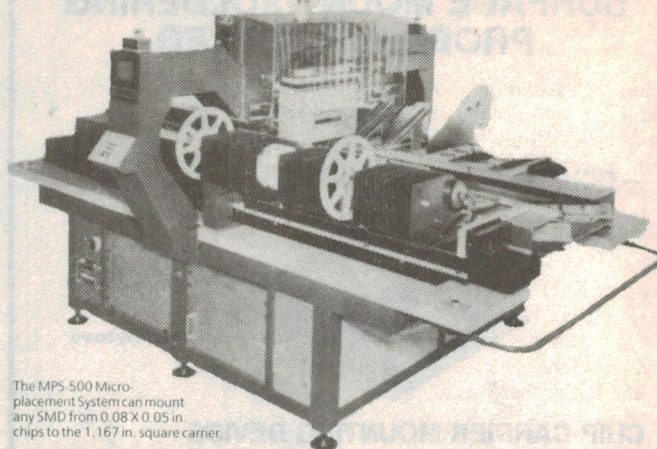
The DIP-G is the most advanced DIP insertion system in both machine output and intelligence.



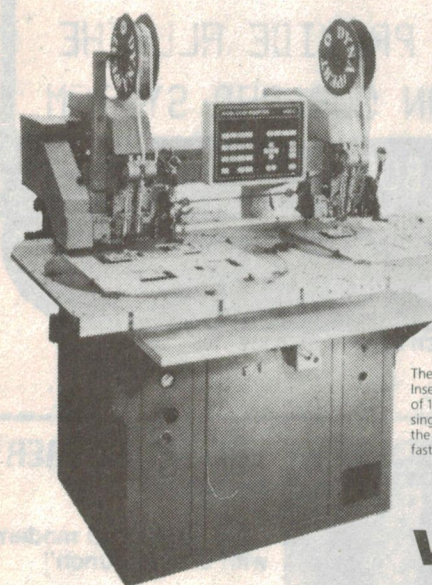The MPS-500 Micro-placement System can mount any SMD from 0.08 x 0.05 in. chips to the 1.167 in. square carrier.



The VCD-F Axial Lead Inserter has a cycle rate of 16,000 pph for a single head, 32,000 for the dual head model, the fastest in the industry.

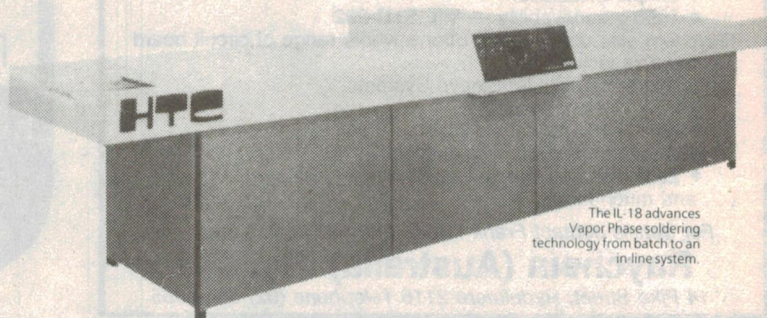

The IL-18 advances Vapor Phase soldering technology from batch to an in-line system.

Four reliable teammates with great competitive spirit

Dynapert has put together a team of field-proven assembly machines to join your production line.


Designed as stand-alone units, all Dynapert's PC Board automated assembly machines show great production yields. Using individual control, each of the Dynapert assembly machines is capable of independent operation at a high throughput level. What's more, Dynapert has designed in-circuit verifiers and other testers that keep production rates high while reducing both the time and expense of PC Board rework.

Statistics: The VCD-F has the fastest axial lead insertion cycle in the industry. The DIP-G is the proven work-horse of the DIP inserters. For surface mounting, the MPS-500 microplacement system handles the widest range of SMDs. And the IL-18

employs the most reliable Vapor Phase soldering technology available anywhere today.

As a team, the Dynapert assembly machines can significantly improve the total throughput of your PC Board production. Editing, diagnostic and high level management information retrieval functions can now become an integral part of your production line. Dynapert supplies today what others promise tomorrow.

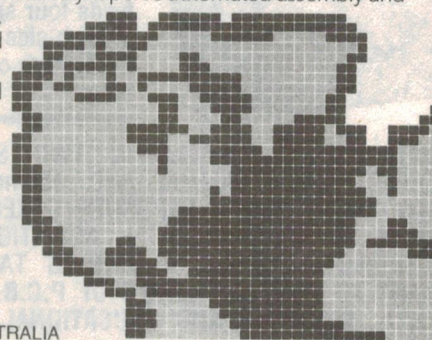To find out more about Dynapert's automated assembly and soldering machines, both entry-level and full production models, write or call Dynapert.



DYNAPERT

EMHART



Penn Central (Australia) Pty. Ltd.

56 SILVERWATER RD,
AUBURN, NSW 2144, AUSTRALIA
PHONE: 648-1661
TELEX: AA72906
FAX: 647-2260

11 RUSHDALE STREET,
KNOXFIELD, VIC 3180, AUSTRALIA
PHONE: 763-8333
TELEX: AA39588

soldering. Although it's been around since the late 60s, reflow is now starting to make an impact, if only because of the introduction of computer control and SMD techniques at more or less the same time.

In a reflow system, the solder is first added to the board, usually in the form of a paste. Often this is part of the original etching process. However it's done, when all the components have been loaded, the assembly is heated, the solder melts (reflows), and components are joined to the tracks.

The major controversy is over the method of heating. Vapour phase and infrared appear to be front runners at the moment, with claimed advantages of reliability and lack of thermal shock. In the vapour phase system the board is plunged into a hot but inert gas. In infrared systems, heating is achieved by exposing the board to infrared radiation.

Hedinair is an English company with extensive experience in both technologies. It claims advantages of tremendous flexibility for the vapour phase system, since all the important set-up parameters of the soldering station are virtually independent of the devices to be soldered. Double-sided, SM or plated-through technologies can all be handled at the same time.

Infrared, on the other hand, is vitally affected by the size and shape of the components on the board, since one component can easily shadow another one. However, infrared is very accurately controllable, so this may not be as much of an operational problem as it sounds. Its advantage is size. Fully professional units will sit on a bench top, or can be integrated into an assembly machine.

Testing

At the testing stage, computers have made massive inroads to the production scene. There are two types, both produced with varying degrees of intelligence and thus user friendliness: static and dynamic testers. A static tester injects a potential on to certain pins and measures current into the others. It's very useful for testing the efficiency of the soldering process and the integrity of tracks and so on. In fact, static testing is often carried out by the board manufacturer to ensure the quality of its product before it's soldered.

However, for testing boards full of components its use is rather limited. For in-circuit testing, especially when complex ICs are involved, the best testers are dynamic. They input a signal similar to those that will be experienced in actual operation and watch the outputs.

Most modern systems have learning functions. These will look at a known good board and learn the expected results. The operator must then go through and specify tolerances but once that is done, the



At STC components are checked against the specification documents (courtesy STC).

machine will reject any board that does not measure up.

One of the largest problem areas is the actual physical connection of the test equipment to the board. Usually, the board is tested using a 'bed of nails'. This consists of a stand of vertical pins, each spring loaded and located in line with every pad on the board. The board is then sucked down by a vacuum on to the bed, and appropriate measurements taken.

The problem is that in some manufacturing plants the probability of a fault developing in the mechanical connection between the bed and the pads is at least as great as an actual problem on the board. In an attempt to solve this, provision is made in the design of the board for pads that are specifically tailored to the needs of the nails and the test routine. But according to Bruce Stephens, Director of Manufacturing at STC, even this has not been completely successful and there is a move towards testing via purpose built circuits on the board, or via edge connectors.

A typical modern piece of automatic test equipment (ATE) is being developed by Tony Richardson of Binary Engineering in Sydney. It's a rack mounted device containing a central processing unit. On one side the board is connected into the ATE via a bed of nails or edge connector, or indeed any arbitrary connection device, and on the other side a set of test instruments: signal generators, counters, oscilloscopes and whatever, connected via standard control buses. This set-up allows the user to define with absolute freedom whatever tests s/he requires, and to make any sort of measurement. At the moment Richardson is work-

ing on learning software for his device, which he hopes will sell for about \$30,000.

Quality control

The implications of all this for quality control are major. In the big companies: STC, Ericsson and AWA, there has been a long and on-going procedure for checking the quality of product going out the door. In the past it tended to be a one stop arrangement. When the product was finished, it was inspected. If it failed, it was sent to a technician who fixed it by hand. It was an overhead on the whole manufacturing process born of necessity.

The existence of cheap, computerised test facilities has made it possible to check at much lower levels within the factory.

At STC for instance, they have done away with the whole idea of the assembly line and instead introduced cells in which a small number of workers carry out a sizable proportion of the manufacturing task. It's an arrangement that not only alleviates the boredom of assembly line work, but it also makes it possible to check the work as it's done. This means that product coming out of a given cell is theoretically always perfect, thus preventing any wasted effort further down the line.

At small companies which includes the majority of board stuffers, the same idea of checking as soon as practical has also taken off. At General Power Tools in Penrith NSW, Fred Morris has divided his factory into sections such that each product batch is tested at every stage of manufacture before it goes any further. There are extra problems in an operation like his though, because of the small size of individual runs.

Imports

Nevertheless, the overheads involved in quality control seem to be welcomed by most manufacturers. This is not as paradoxical as it seems because it allows the local manufacturers to compete with the sweatshops of Asia on their own terms.

For a long time local shops have sat and watched engineers fly their designs out to Hong Kong or Singapore, secure in the belief that both price and reliability was better in Asia than here. For the first time, they have a means of fighting back. Automation means quality control as a matter of course.

The cost of labour, once the albatross around our necks, is becoming irrelevant.

Not that we are having it all our own way. In many respects the Asians are a moving target, at least in price terms. Prices for board and assembly have been driven down by excess capacity following the downturn in the US market. But it's not a situation that is likely to continue.

What will continue is the reliability and quality of the local product, and hopefully an even more competitive pricing structure. ●



**IN 1986 A MAJOR
PRINTED CIRCUIT
BOARD
MANUFACTURER
WILL MOVE
AHEAD OF THEIR
COMPETITION BY
IMPROVING
PRODUCT
QUALITY,
BOOSTING
PRODUCTIVITY
AND DELIVERING
ON TIME ...**


★ TEKPRO ★

*For your immediate P.C.B. requirements call the
TEKPRO TECHNICAL SALES office in your area.*

TEKPRO, part of the TEKNIS LIMITED Group
Philips Crescent, Hendon,
South Australia. 5014

**S.A. (08) 268-6122 N.S.W. (02) 439-1599
VIC. (03) 618-5121**

ETI READER SERVICE 167

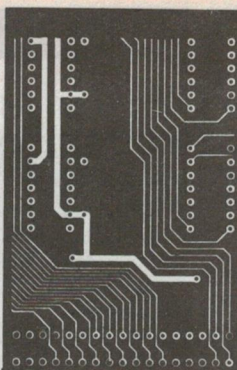

**Chemical
Treatments
& Coatings Pty Ltd**

Incorporated in Victoria

32 Windsor Road,
Croydon, Vic. 3136 Australia.
Telex: AA 139664 SETECE
Telephone: (03) 725 9666

Agents and importers of
sophisticated equipment
and manufacturers of
fine chemicals for the
printed circuit industry.

ETI READER SERVICE 168



Q. WHO IS MACH SYSTEMS ?

A. We are a contract assembly house.
*Whatever stage of production needed,
we fulfill.*

- Research and Development
- P.C.B. Artworks
- Component Sourcing
- Component Insertion
- Wave Soldering
- Board Cleaning
- Testing
- Specialist Assembly

The concept of Mach Systems is to support the
Australian electronics industry in as many aspects as
a complete manufacturing facility can.
From Prototyping to Production.
"DEDICATED TO TECHNOLOGY"

70 Keys Rd, Moorabbin, Victoria, 3189.
Telephone: (03) 555-0133

Telex: AA 151952

ETI READER SERVICE 169

HomeWatch

PROFESSIONAL COMPUTERISED SECURITY KIT



Deluxe kit illustrated.

2 Kits available—Standard or Deluxe. 4 sector Control with switch selection of its many pre-programmed functions. Quality components for reliability. Comprehensive instructions included.

Literature, prices and further information available from:



I.E.I. (Aust) Pty. Ltd.

15-17 Normanby Rd, Clayton, Vic, 3149
Tel (03) 544 8411. Telex AA35780

248 Johnston St, Annandale, NSW, 2038
Tel (02) 692 0999

31 Phillips St, Thebarton, SA, 5031
Tel (08) 352 2066

**INSTALL IT
YOURSELF**

MICROPHONE OF THE MONTH


... A CLOSE LOOK
AT ONE OF OUR 100



SM5B
UNI-DYNAMIC



SM83
Omnidirectional
Condenser Lavalier
Microphone System

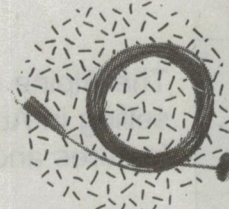

SM83
OMNI
CONDENSER



SM7
UNI-DYNAMIC



SM82
LINE LEVEL
CONDENSER



SM91
HALF-CARDIOID
CONDENSER



SM81
UNI-CONDENSER



SM87
SUPER-CARDIOID
CONDENSER

Doesn't sound like conventional lavaliers THE MICROPHONE -

Absolutely the most natural sounding lavalier ... ever. From high to low frequencies, the sound is clean and lifelike. Unique electronically created dip at 730Hz overcomes the chest resonance phenomenon. Acoustically generated high-frequency boost above 3 kHz for more pleasing, intelligible voice reproduction. Also, a 12 dB per octave rolloff below 100 Hz helps reduce low frequency room noise, and chest resonances.

Virtually invisible

Black matte finish. Unique side exit cord, and innovative mounting hardware makes it easier than ever to conceal the cable behind a tie, blouse, or shirt. Two multi-purpose mounting blocks may be connected to lanyard, or sewn, pinned, or taped onto clothing. Only 19.6mm L x 11.2mm Diameter, 45 grams.

Trouble-free THE AMPLIFIER

Exclusive Shure design - especially for the SM83 system. Lightweight and compact for belt or pocket. Powered by 9V battery or by simplex power from external source providing 5 to 52 Vdc. Extensive RF and hum shielding to reduce effects of electromagnetic or static interference. One of a kind ... from Shure, of course.

For full details contact:
Audio Engineers

342 Kent St, Sydney 2000 (02) 296731
Queensland (07) 44 8947
Western Aust. (09) 361 5954

Sound of the professionals

SHURE®

THE ALPINE VIEW

— Alpine 5900 car CD player


Louis Challis

ALPINE 5900 CD PLAYER


Dimensions: 178mm (wide) x 50mm (high) x 155mm (deep)
 Weight: 1.8kg
 Manufacturer: Alpine Electronics Inc, Japan
 RRP: \$1546

The Alpine 5900 sits loftily as the most expensive CD player selling in Australia. For your extravagance you get some fresh features and a top performance.


Response curves

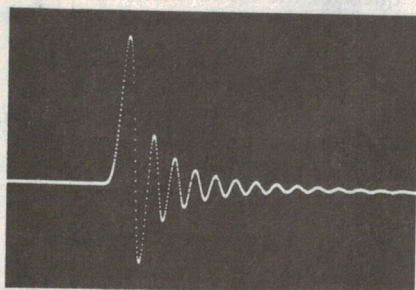

Impulse wave

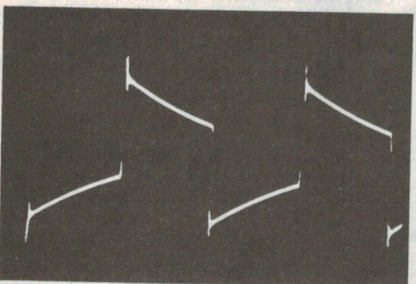

Square wave at 100Hz

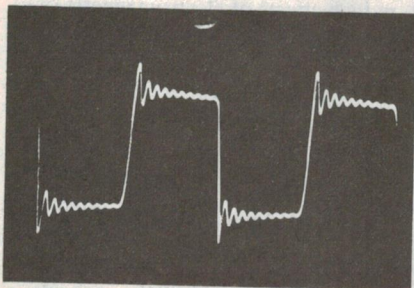

Square wave at 1kHz

VARIOUS PIECES OF electronic equipment have their devotees and it seems that the latest Alpine AM/FM car cassette players have a somewhat unusual 'fan club'. Members will stop at almost nothing to get their hands on one or more of these pieces of equipment. That the equipment in question is someone else's property is really of little interest because this fan club works at night with bricks, hammers, jemmies, screwdrivers and other assorted tools to remove the latest versions of Alpine 7155E and 7273E units, which they know are fitted as standard equipment to recent SAABs (amongst other cars). You might ask how I happen to be aware of such trivia? Well, a member of staff and I have new SAABs, and both of us have had our Alpine units stolen.

With such nefarious admirers, it is questionable whether you need friends to admire your equipment, and it was with some misgivings that I proceeded to evaluate the Alpine 5900 compact disc player.



The 5900 automotive CD player requires an appropriate FM/AM cassette player or external amplifier to provide the amplification and interconnection facilities to utilise the unit. The Australian importers provided us with a top of the line 7273E unit with a base power level of 2 x 20W output and appropriate PRE OUT/IN interconnecting cable facilities. Before I realised that the 7273E was not intended to be reviewed, I had evaluated its objective performance characteristics as well. It was only after I finished the testing and subjective reviewing that Alpine provided a DIN-to-RCA adaptor (part no 4308) to connect this unit to other brands of amplifier and more specifically to facilitate direct testing without introducing the problems created as a result of performance limitations in the FM/AM cassette player.

Design and appearance

The front panel of the CD player is sized to match the standard DIN dimensions to which most manufacturers' units now conform. On the left hand side of the black moulded plastic escutcheon is a large concentric VOLUME and BALANCE control. The volume control is provided with a series of indents so that once a level setting is selected, it will not be easily knocked or displaced to a different level. Immediately below these controls are recessed spring loaded BASS and TREBLE volume controls which pop out on touch and similarly return to provide a neat and uncluttered access to VOLUME and BALANCE controls with which they would otherwise interfere.

At the top of the panel is a recessed slot into which you partially push a CD disc before the power loading capabilities take over. This facility literally draws the disc from your fingers and digests it within the internal workings of the unit before dropping down a dust cover. Immediately below the left hand end of the slot is an elongated REPEAT button. To the right of this is the display module which looks very much like the 7273E unit provided with it. It displays the repeat mode (ONE or ALL), as well as elapsed time (in minutes and seconds) and track number by means of a large blue plasma display. It also displays the PLAY and PAUSE functions at the right hand end.

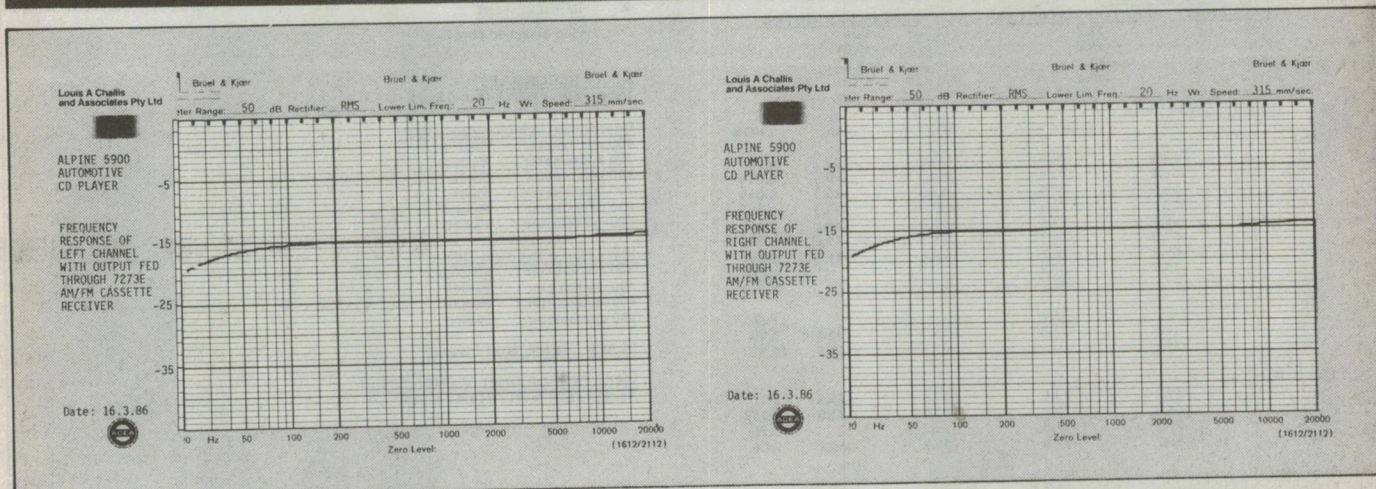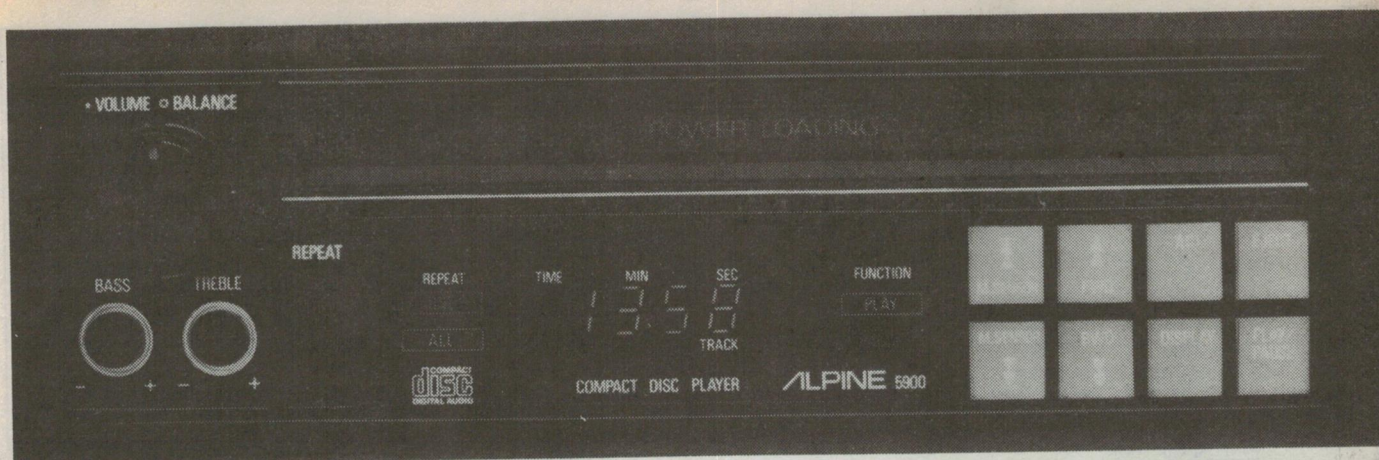At the lower right hand corner of the panel are eight pushbuttons with soft rear illumination. These buttons are arranged in two rows. The first two buttons, labelled M SENSOR, allow you to move progressively forwards or backwards track by track. Adjacent to these are the buttons providing conventional FAST FORWARD and BACKWARD capabilities. The next but-



ton is labelled ADI (auto disc initialiser) which returns the laser tracking system to the beginning of the disc and also functions as a partial reset button, whilst immediately below is the DISPLAY button, which flips the display between elapsed time and the remaining time and track number.

The last two buttons are the EJECT button (at the top) and the PLAY/PAUSE button at the right hand corner. These controls are accompanied by the same "bleep" when pressed, regrettably irrespective of function. A better approach would have been a different tone for each function so that you could identify the accuracy of your probing (without looking) as you drive.

One additional control which is not labelled is provided at the extreme right hand end of the power loading socket. This takes the form of a small hole which requires a sharp needle or probe tip and is the total function RESET button. This should only need to be activated in the event of a total functional failure.

The rear of the unit is provided with a number of special cables. One of these has the high voltage supply (with its noisy components) terminating its end so that the electronic interference that would otherwise be produced is sensibly located outside the main cabinet. The rear panel also incorporates a pair of multi-core cables fitted with specially moulded and unusually large DIN sockets. These have locking facilities into which a matching pair of normally intercon-

nected plugs and sockets (on the 7273E unit) are then plugged. These cable harnesses simplify the interconnection and powering of the unit for minimal problems when fitting the unit into the dashboard.

Inside of the unit space limitations are, it would appear, primarily the result of the power loading facilities which not only require considerable space but, I believe, considerable ingenuity as well. The result is that the base of the unit incorporates a large mother board over which a number of supplementary printed circuit boards are installed. These are supplemented by additional printed circuit boards at the rear of the unit and at the top of the chassis immediately behind the volume control. Although beautifully executed and supplemented by appropriate ribbon cables with plugs and sockets, the unit would present some 'exciting' problems for the serviceman, if and when he has to work on it. Even so, the unit is very solidly constructed with good commercial components although, it should be noted, the resistors and a large number of other components are positively miniscule!

The main chassis and cabinet of the unit, together with the chassis frame for the laser power loading system, are well made from heavy folded steel. A closer inspection inside the chassis reveals that the laser tracking system is the well-proven Sony system, apparently as are many of the other critical components used in the system design.

Objective performance

With the 5900 CD player interconnected with the 7273E FM/AM cassette player, we were able to undertake a slightly less than critical evaluation of the CD player's performance. As it transpires, far too many of the performance parameters are dominated by the FM/AM cassette player, rather than by the characteristics of the CD player. The frequency response is a good example of this, being controlled by the cassette player's amplifier circuitry. The performance is +1 -3dB from 30Hz to 20kHz. By referencing the measured performance of the FM/AM cassette player, it is apparent that the low frequency response of the CD player is virtually flat.

One parameter that was not affected by the interconnection was the linearity performance of the player. This is within 0.1dB to -60dB, within 0.2dB to -70dB, within 0.4dB at -80dB, and is 2.4dB high at -90dB. This linearity performance is excellent and far better than that provided by many 'domestic' CD players.

The channel separation is in no way comparable with that provided by most domestic CD players because of the feedthrough within the amplifier section of the car cassette player as well as by the interconnection cables. The separation is a modest -56dB at 100Hz, -58dB at 1kHz, -45dB at 10kHz and -40dB at 20kHz. These figures are, however, far better than you would

MEASURED PERFORMANCE OF ALPINE CAR COMPACT DISC PLAYER

MODEL NO. 5900

SERIAL NO. 51124134 C/22708

1. FREQUENCY RESPONSE 20 Hz to 20 kHz +1 -3 dB

2. LINEARITY @ 1kHz

NOMINAL LEVEL	LEFT OUTPUT	RIGHT OUTPUT
0 dB	0.0	0.0
-1.0	-1.0	-1.0
-3.0	-3.0	-3.0
-6.0	-6.0	-6.0
-10.0	-10.0	-10.0
-20.0	-20.1	-20.1
-30.0	-30.0	-30.0
-40.0	-40.0	-40.0
-50.0	-50.0	-50.0
-60.0	-59.9	-60.0
-70.0	-69.8	-69.9
-80.0	-79.7	-79.6
-90.0	-87.6	-87.6

3. CHANNEL SEPARATION

FREQUENCY	RIGHT INTO LEFT dB	LEFT INTO RIGHT dB
100Hz	-57.2	-56.1
1kHz	-58.8	-59.0
10kHz	-45.2	-49.8
20kHz	-40.6	-47.2

4. DISTORTION (@ 1kHz)

Level	2nd	3rd	4th	5th	THD%
0	-68.8	-73.9	-79.2	-80.1	0.044
-1.0	-68.5	-73.1	-80.2	-80.4	0.046
-3.0	-68.6	-73.5	-82.3	-80.5	0.044
-6.0	-69.1	-75.4	-80.3	-79.3	0.042
-10	-69.2	-73.8	-79.9	-79.6	0.043
-20	-69.3	-74.5	-78.5	-79.6	0.042
-30	-69.2	-74.7	-79.4	-81.5	0.041
-40	-79.7	-73.2			0.024
-50		-57.7			0.013
-60					
-70		-35.7			1.64
-80	-34.9	-27.0	-35.9	-35.6	5.40
-90	-22.1		-27.8	-15.0	19.9
(@ 100 Hz)					
0	-59.5	-73.4	-80.6	-83.3	0.11
-20	-66.4	-74.6	-83.8	-85.0	0.052
-40	-51.9	-67.9			0.26
-60	-31.7	-47.4	-54.8	-50.4	2.66
(@ 6.3 kHz)					
0	-59.2	-60.6	-76.1		0.14

5. EMPHASIS

Frequency	Recorded Level	Output Level (L)	Output Level (R)
1 kHz	-0.37 dB	-0.4	-0.4
5 kHz	-4.53 dB	-4.8	-4.8
16 kHz	-9.04 dB	-9.4	-9.4

6. SIGNAL TO NOISE RATIO

Without Emphasis	56.6 (Lin)	73.2 dB(A)
With Emphasis	56.6 (Lin)	73.2 dB(A)

7. FREQUENCY ACCURACY

(19,999 kHz) ± 2 Hz for 20kHz test signal

8. SQUARE WAVE RESPONSE

(See attached photos)

9. IMPULSE TEST

(See attached photo)

DIRTY RECORD TEST

Using Philips NR4A (410-056-2)

Interruption in Information Layer

400 micrometer ;	Passed
500 micrometer ;	Passed
600 micrometer ;	Passed
700 micrometer ;	Passed
800 micrometer ;	Passed
900 micrometer ;	Passed

Black Dot at Read out Side

300 micrometer ;	glitches
500 micrometer ;	Passed
600 micrometer ;	Passed
800 micrometer ;	Passed

BLACK STRIPE TEST (passed)

VIBRATION OR DISPLACEMENT TEST

Acceleration level 1g'rms failed

reasonably require in an automotive environment.

The distortion characteristics of the CD player are almost completely dominated by the performance of the amplifier. They were measured at 0.8 volts output from the amplifier so as to limit the effects that this unit has on the figures. Between 0dB and -30dB, the distortion is typically 0.4% rising to 0.13% at the -50dB level. It is not until the signal drops to -70dB that we see any significant rise in the distortion, and by -80dB the distortion rises to more than 5%. At -90dB (where it would be impossible to hear the distortion above the road noise), it rises to 20%. The distortion figures at 100Hz and 6.3kHz are also dominated by the car cassette player amplifier distortion but it is clear that the basic CD player has particularly low distortion characteristics.

The 'emphasis' circuit characteristics of the player are reasonably accurate while the signal-to-noise ratio (relative to 0dB signal level) is still a healthy 73dB(A) even with the added burden of the cassette player amplifier. It is questionable whether you will ever be able to use that performance capability except in a boat, caravan or with the car's engine switched off.

The frequency accuracy is excellent at 2% but the square wave performance is also

dominated by the characteristics of the car cassette player, particularly at low frequencies. The impulse response is clean although it shows the signs of the analogue filter's steep 'skirt selectivity'. This characteristic also shows through in the square wave response.

The laser tracking circuitry is able to track all the nasty sections of the Philips tracking disc including interruptions in the information level of up to 900 micrometres without any sign of a problem. When it comes to the Black Dot readout test, the laser tracking system is only able to cope with surface dust and imperfections of up to 1mm (which is extremely commendable).

The player cannot cope with eccentric discs but is able to operate when vibration levels in the critical 2-10Hz region are as high as 15g'rms. This would correspond to the road conditions of many bush tracks and means that most suburban roads with pot holes would be handled adequately.

Subjective performance

Although I requested that the agents find a car with the CD player installed, I was unsuccessful and had to be 'happy' with a laboratory evaluation because of the complexity of interconnections. This was performed with a pair of JBL L4301 monitors interconnected to the output of the 7273E. With this

set-up in operation, the performance of the 5900 CD player proved to be exciting and I was hard pressed to detect any subjective difference in comparison with a Sony CDP-101 player interconnected with a Yamaha 101M amplifier.

Even though the performance of this unit is extremely good, I am still apprehensive at the thought of a potential user gingerly loading an unprotected disc into the loading port whilst driving. Although many users may develop the necessary skills of holding the disc by its edges, I feel they will be the minority.

The Alpine 5900 CD player has been designed to cope with disc 'grabbing' and even re-ingests the disc if it is not withdrawn from the slot within 15 seconds. Even so, the laser tracking system has to cope with many other problems including dust, grime, and dirty fingers, all of which will ultimately take their toll.

At this early point, our testing indicates a performance coping with most of these problems.

The Alpine 5900 automotive CD player is an excellent unit and certainly provides overall advances in automotive music listening potential when compared to an AM/FM cassette player. However, with its recommended retail price at \$1546 the importers may have limited the size of their market.●

\$599*
MAY NOT
BUY YOU A
LOT OF
SPEAKER -
UNLESS IT'S
A DALI-3



*R.R.P.

DALI
does it all by design.

The DALI design philosophy is not one which follows the insincere trend towards vinyl cabinets, cosmetic trims, flashy lights and other useless gimmicks. DALI spends effort into making the best sound possible. Which creates such comments as -
"This speaker sounds better than I'd expected at the price."

Hi-Fi & Electronic, Denmark.
"Stereo imaging is quite stable and spacious, and transient response is quite good. Tonal balance and freedom from coloration also struck us as remarkably good for the price."

High Fidelity, USA.
"The sound was very clean and 'British-sounding' - almost neutral with excellent definition and separation...the DALI-3 is another reason why hi-fi lovers on a limited budget should not have to put up with lo-fi sound."

Australian Hi-Fi Magazine.

For a most comprehensive brochure and the name of your nearest DALI dealer, please contact the Sole Australian Distributor:

SCAN AUDIO Pty. Ltd.
52 Crown St, Richmond Vic. 3121.
Telephone (03) 429 2199
Queensland Office: (07) 57 7433
West Australian Office: (09) 382 3370

DALI

ETI READER SERVICE 172

SA 3786A



Rockwell

65XXX — 68000
SAVE \$\$\$\$

6500 SERIES		DISPLAY CONTROLLERS	
R6502P	8.50	10937P-50	11.02
R6502AP	9.28	10951P-50	11.02
R6503AP	7.24	10938P	9.44
R6504AP	7.24	10939P	9.44
R6505AP	7.24	10941P	9.44
R6507AP	7.24	10942P	9.44
R6511Q	21.26	10943P	9.44
R6511AQ	23.28		
R6520P	5.19		
R6520AP	5.98		
R6522P	6.77		
R6522AP	7.55		
R6532P	9.44		
R6532AP	10.39		
R6541Q	19.17		
R6541AQ	21.09		
R6545-1P	9.13		
R6545-1AP	10.70		
R6545AP	12.27		
R6549P	60.58		
R6551P	9.91		
R6551AP	10.70		

16 BIT 68000 SERIES I.C.'s	
R68000C10	69.24
R68000Q10	33.04
R68465P	16.52
R68C552P	27.07
R68561P	58.22
R68802P	61.37

MEMORY I.C.'s	
2114	1.35
4116	2.65
4164	1.35
41256	6.67
6116	7.18
6264	20.26
2716	4.81
2732	POA
2764	3.18
27128	5.75

CRYSTALS	
32.768 KHz - CMOS	
Calendar	1.96
1.8432MHz	3.08
2.000MHz	3.08
2.4576MHz	1.96
3.6864MHz	1.96
4.000MHz	1.96
4.9152MHz	2.80
8.000MHz	1.96
12.000MHz	1.96
Quip Socket for R6511Q, R68000Q, R65F12, Modem I.C.	3.12

PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s	
R6500/1EAB3	69.24
R65/11EB2	62.94
R65/11EAB	69.24
R65/41EAB	69.24

MODEMS	
R1212M	358.05
R1212DS	267.51
R2424M	590.22
R2424DS	361.93

Please include \$6.50 for packaging and freight

All prices include sales tax

Prices subject to alteration without notification

energy CONTROL

73 Eric Street, Goodna Q 4300
P.O. Box 6502, Goodna Q 4300
Telephone (07) 288 2455
Telex AA43778 ENECON

ETI READER SERVICE 173



Disco World Pty. Ltd.

Showrooms:

300 Main Street, Lilydale
P.O. Box 509, Lilydale, 3140
Melb. Vic. (03) 735-0588
673 High Street, Preston
(03) 470 5822

AMPLIFIERS
ZPE Series II (600W) \$1950.00

DISCO MIXERS
Citronic SM 350 \$840.00
Arista with equaliser \$350.00

JUMBO STROBE
Scanner \$179.19
\$120.45

HELICOPTER
2 ARM Spinner \$252.00
4 ARM Spinner \$495.70
6 ARM Spinner \$536.44



PINSPOT
Par 36 \$52.75
Par 46 \$70.79



MIRROR BALLS
MB 008-8" \$49.67
MB 012 \$77.49
MB 014 \$112.25
MB 018 \$150.41
MB 020 \$181.10

SMOKE MACHINES
Great for Special Effects
Hand Held 240V \$352.00

Dynamite Smoke 1200 Machine
Has remote control lead to operate off-stage. We are so excited about this that full money back guarantee will be valid for 10 days from purchase date
Our own product \$1800.00
Fluid—1 litre \$15.00

MIRROR BALL MOTORS
AC 240V \$37.30
Heavy Duty \$95.94

ROLLING LIGHTS
8 x 4515 lamps \$1450.00

AUDIO CHASER
(DW4LC4000) \$295.00
Musicolor and chaser all in one!!
Our own product



COSMO
24 lamps \$1990.00
Half Ball rotary light 6 lamps \$428.74

LAMPS all colours, so cheap!
No Warranty on Breakages
ES 240V 60W box of 25 \$75.00
BC 240V 40W box of 100 \$77.00
BC 240V 25W box of 100 \$75.00

Prices subject to change without notice. Items for hire or sale. Power Cords not included. Send S.A.E. with 60 cents postage for free price list.

Agent for Citronic gear! We have Piezo tweeters, Etone speakers, Rope lights and many other products.

ETI READER SERVICE 174

ETI June 1986 — 33

SPECIAL NEW ANTENNA PICK UP TV THEY DON'T WANT YOU TO WATCH! LETS YOU PICK UP PROGRAMS BLACKED OUT IN YOUR CITY!

You know the story, it's the big footy game, cricket match, boxing fixture, etc. and it's happening in YOUR CITY. Everyone else in the country - including people in nearby towns - can watch it live except you. Well now you can do something about it! Jaycar has produced a TV antenna ESPECIALLY MADE to have VERY HIGH GAIN on channels 4 and 5A. If you live in Sydney, for example, you must mount the antenna as high as possible and point it due south towards Wollongong where there is generally no TV sports

blackout. Maybe not applicable in your city - please check. Hotel publicans have spent fortunes having expensive antennas installed so their patrons can watch sport live - now you can have this benefit in your own home for a fraction of the cost! Start watching live sport NOW!
Cat. LT-3190

**ONLY \$59.95
EXCLUSIVE!!**

**NEW FOR
1986**

BLANK FIBREGLOSS

PCB - Single sided copper clad, for making your own PCB's. 300mm x 300mm.
Cat. HP-9510

**NORMALLY \$8.95
SAVE \$3.95
THIS MONTH ONLY
ONLY \$5.00 ea**

NEW NEW NEW NEW

ETI 1402 DIGITAL SAMPLER

Ref. ETI May - June 1986
This kit enables you to record short bursts of sound i.e. "sample" or behave as a digital delay. It is a very low cost way of getting "into" digital sound techniques. You never know you may end up becoming the next "Frankie Goes to Hollywood"! The Jaycar kit includes case, knobs, plug pack, all board components etc.
Cat. KE-4720

ONLY \$119.00

CD COMPRESSOR

Ref. EA June 1986
This little black box allows you to record from compact disc to cassette without losing the highs and lows, thereby retaining the quality.
Cat. KA-1665

ONLY \$69.50

LOW COST SPEECH SYNTHESISER

AEM 4504 - see AEM Feb 1986
This is the real thing. It can be interfaced to any computer having an 8 bit I/O port. It uses the SP0256A AL2 General Instruments chip. DIP header and computer connector are not supplied. IC sockets ARE supplied.
Cat. KM-3042

ONLY \$39.95

80 + 80WRMS PRE- MAIN AMPLIFIER

A complete preamp and high power amp - with power supply electronics and loudspeaker protector in the one package! All that you need to connect is a power transformer and a signal source! The AA-0310 features TWO huge heatsinks for the power transistors, bass, treble and midrange controls, a microphone preamp and mixer pot, balance and volume control. There is a facility for treamp out (to dub from source to tape) as well as phono out. All in all it's a very well thought out unit. The main board measures 245(W) x 240(D), the heatsinks 130(W) x 75(D) x 70(H)mm are connected to the main amp board by about 150mm of wiring.
Cat. AA-0310

**ONLY
\$149.95**

Suitable
power.

transformer 4361

Cat. MM-2015 **\$55.00**

ETI 4600 DUAL SPEED MODEM

Ref. AEM December 1985
This project enables you to construct a modem that operates at either 300 Baud full duplex or 1200/75 Baud half duplex (i.e. CCITT V.21 Orig, CCITT V.21 Ans; CCITT V.23 (mode 2) Orig & CCITT V.23 back) for a fraction of the cost of equivalent built units. The Jaycar kit uses all original components and after much field testing, has been de-bugged. It works well!
Cat. KM-3040

**NORMALLY \$169.00
SAVE \$20 ONLY
\$149**

**GORE HILL
OPEN UNTIL
4pm
SATURDAY**

MICROPHONE MADNESS JAYCARS UNBELIEVABLE MICROPHONE DISTRESS STOCK PURCHASE

WIRELESS/WIRE MIC UNIDIRECTIONAL DISTRESS STOCK PURCHASE

No more cords! It has a built in FM transmitter that can be picked up by any FM receiver. The signal can be amplified for PA etc. Service area is up to 50 metres. Also usable as a conventional microphone with the supplied cable. Frequency 88 - 108MHz
**THESE WOULD NORMALLY
SELL FOR \$32.50**

Due to distress stock purchase we have a quantity available for only

\$19.95

SAVE \$12.55 - 61%!!!

Cat. AM-4071

SAVE OVER 50% ON SOME

Jaycar has purchased an entire "Job Lot" of quality "Unisound" microphones. Most are below half what you'd expect to pay. Quantities are strictly limited, and once sold can never be repeated.

FM WIRELESS MIC ELECTRET CONDENSER

If you want an FM mic to experiment with or use in a small public address system, this is the one. Only 100 available. Transmitting frequency range 88.1MHz to 106MHz. Omnidirectional. Field strength is less than 50uV/m at 50 feet. Supplied with windscreen, frequency adjuster, Lavalier and battery.
Cat. AM-4072

**NORMALLY SELLS FOR \$27.95
1/2 PRICE SAVE \$14
ONLY \$13.95**

**FM WIRELESS MIC
ELECTRET CONDENSER CARDIOID**
This is a top quality FM mic. Frequency transmitting range 88MHz - 106MHz. Unidirectional.
Cat. AM-4073

**NORMALLY SELLS FOR \$38.50
LESS THAN 1/2 PRICE
SAVE \$20.00
ONLY \$18.50**

PROFESSIONAL ELECTRET CONDENSER UNIDIRECTIONAL DUAL IMP - DUAL TONE

This mic has a unique dual tone switch. At the "flat" position it is suited to music, recording and other Hi Fi purposes due to its perfectly flat character at all frequencies. At the "Vocal" position it is suited to PA work which prevents too much low tone or indistinct sound when mic is held close to the mouth. Freq. Response 30-20,000Hz. Impedance Lo 1k, Hi 10k. Sensitivity Lo -68dB \pm 3dB, Hi -57dB \pm 3dB. Complete with cable and 6.5mm plug. A TRULY PROFESSIONAL MICROPHONE.
Cat. AM-4080

**NORMALLY \$47.50
SAVE \$18.00
ONLY \$29.50**

PA MICROPHONES 2 TO CHOOSE FROM UNIDIRECTIONAL DYNAMIC

Incorporates 155mm gooseneck on a heavy base with on/off switch. Frequency 50-13,000Hz. Impedance 500 ohms. Sensitivity -78dB. 4 metres cable with plug.
Cat. AM-4076

**USUALLY SELLS FOR \$42
SAVE \$20.00
NOW ONLY \$22.00**

OMNIDIRECTIONAL DYNAMIC

With 155mm gooseneck on heavy base with on/off switch. Frequency response 50-13,000Hz. Impedance 400 ohms. Sensitivity -78dB. 4 metres of cable with plug.

**USUALLY SELLS FOR \$34.50
SAVE \$19.50
NOW ONLY \$15.00**

Cat. AM-4077

**Jaycar
ELECTRONICS**
INCORPORATING ELECTRONIC AGENCIES
QLD. BURANDA 144 Logan Rd. (07) 393 0777
Mon - Fri 9 am - 5:30 pm
Thurs until 8:30 pm. Sat 9 am - 12 noon

HEAD OFFICE

115 Parramatta Rd
Concord 2137
(02) 747 2022 Telex 72293

ROAD FREIGHT ANYWHERE IN AUSTRALIA \$13.50

VISA



MasterCard



Cards Welcome

MAIL ORDER VIA YOUR PHONE

MAIL ORDERS
P.O. Box 185 Concord 2137
(02) 747 1888 **HOTLINE**
(008) 022 888 **TOLLFREE**

POST & PACKING	
\$5 - \$9.99	\$ 2.00
\$10 - \$24.99	\$ 3.75
\$25 - \$49.99	\$ 4.50
\$50 - \$99.99	\$ 6.50
OVER \$100	\$10.00

BRAND NEW 100 page 1986/7 ENGINEERING CATALOGUE OUT NOW SEND LARGE S.A.E.

GLITTERING GOLD

— Tannoy M20 loudspeakers

Louis Challis



Tannoy has emerged out of the shadows of the giants of speaker manufacture, glittering. The new M20 "Gold" Loudspeakers reflect some design innovation and pride.

TANNOY M20 "GOLD" LOUDSPEAKERS

Dimensions: 530mm (wide) x 570mm (high)
x 315mm (deep)
Weight: 5.5kg (each speaker)
Manufacturer: Tannoy Ltd, United Kingdom
RRP: \$799 (per pair)

TANNOY IS ONE of Britain's oldest and probably its best known manufacturer of loudspeakers. Until the mid 50s, Tannoy had a virtual strangle-hold on the supply of studio monitors in the UK and provided the BBC with nearly all its critical loudspeakers. In the late 60s and early 70s, the company was eclipsed by a number of other notable English, European and American speaker manufacturers which devoted much more money to research and were thus able to produce more exciting speaker systems.






At this time, Tannoy placed its 'blind faith' in the attributes of its coaxial loudspeaker systems and this, to a large measure, proved to be its undoing. A coaxial

loudspeaker with the supplementary tweeter cone directly coupled to the woofer cone at the edge of the voice coil is just too much of a compromise to work efficiently and effectively at both ends of the audible spectrum. Whilst the low frequency end works out reasonably well, the mid and high frequency ends exhibit various objective and subjective deficiencies that 'not all the blarney' in the world can hide.

It took the management at Tannoy far too long to realise that they were thrashing a dead horse, but when they did, they reapplied their research effort to more conventional tried and proven recipes for loudspeaker configurations.

A number of Tannoy's late 70s designs and even early 80s designs still lacked the refinements and performance that the market place demands (see ETI June 1983) and Tannoy went back to the drawing boards yet again.

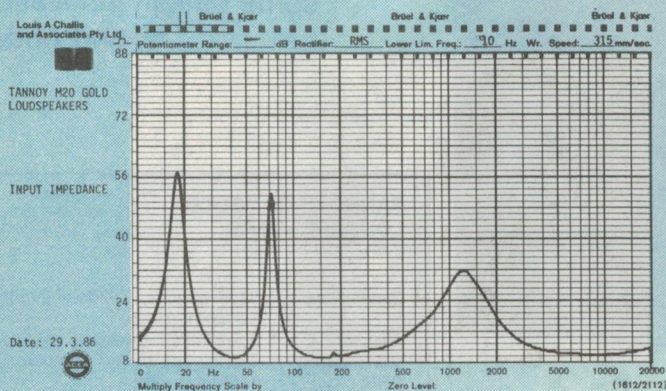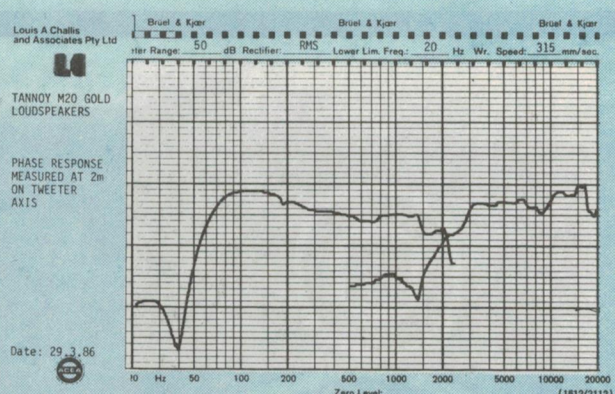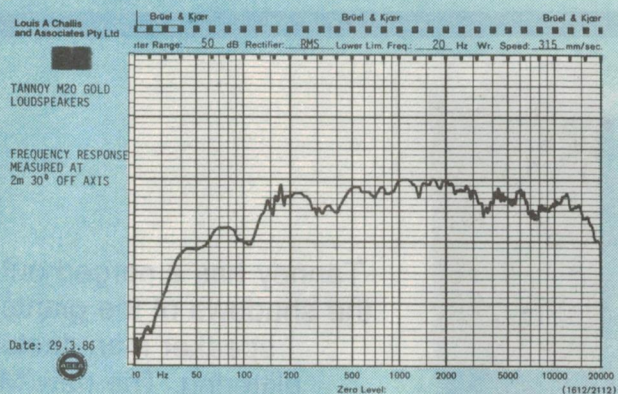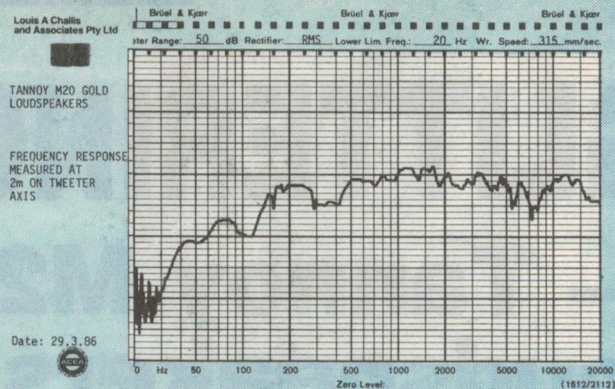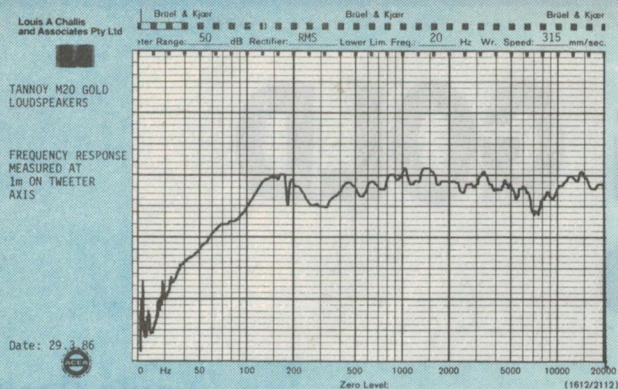The recent M20 "Gold" system is one of the smallest bookshelf speaker systems that Tannoy has marketed to date, yet it contains a number of well-chosen refinements and unusual design features which go a long way towards achieving the superlative performance that most intending purchasers are seeking.



Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Editor.

Design and appearance

The M20 has an overall volume of approximately 90 litres, which means that the cabinets have a particularly small volume especially as the designers have opted to use a conventional venting port to extend the low frequency performance. Most manufacturers use a sealed air-loaded enclosure for such a miniscule volume as this tends to result in a smaller number of resonances and fewer overall design problems. The venting port, which has a diameter of 47mm and a length of 80mm, is located immediately below the 200mm diameter woofer, which is itself of a rather unusual design.

The effective diameter of the woofer is less than 150mm and the cone is constructed


from an unusual translucent polyolefin copolymer, which allows you to view the speaker bracket and voice coil connection leads through the diaphragm. Although the visual effect is not exciting, the polyolefin copolymer is a mighty tough material, appropriate for this demanding service.

The outer edges of the speaker diaphragm are flexibly connected to the inner ring of the speaker basket frame by means of a rolled-EPDM rubber surround, about which I will have more to say later. The active portion of the speaker diaphragm has a far smaller area than appears at first sight and consequently, the acoustical output of the woofer is remarkably efficient when the real area of the speaker is considered. The

woofer's voice coil diameter is 25mm and the speaker magnet appears to be a fairly conventional high energy ferrite assembly designed for reasonably high amplitude (long throw) movement of the speaker.

The tweeter is also of unusual design and, like the woofer, uses a fairly esoteric diaphragm material. In this case, the diaphragm is a soft dome, plastic impregnated, woven material carefully selected to achieve a wider polar dispersion or radiation pattern than most of the comparable units on the market. This diaphragm is directly connected to a 25mm diameter voice coil, which ensures that its power handling capacity and peak output are way above average.

Decay response spectra.

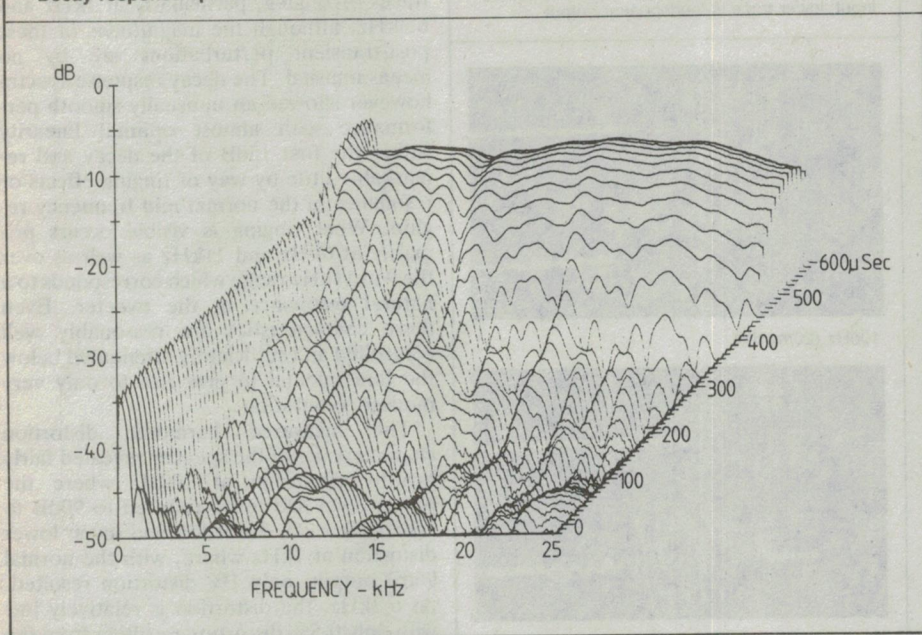

The tweeter diaphragm has been supplemented by an "acoustic matching plate" which Tannoy claims ensures improved acoustical output to the surrounding air mass. It is also to provide an enhanced wide listening window with simultaneous improvements in the frequency linearity at high frequencies (2kHz to 20kHz). This matching plate uses a simple tapered inner edge profile, extended radially into a flush face plate element. The tweeter arrangement sits flush with the face of the speaker cabinet to provide optimal propagation over the primary frequency range. This seemingly obvious approach has been overlooked by most other speaker designers and, when correctly implemented, can readily tailor a specific portion of the frequency response to modify its characteristics. A little more thought leads one to the obvious conclusion that by introducing extended contouring of the taper, wider and more significant enhancement could be achieved over a greater range of frequencies.

All the primary exposed surfaces of the cabinet, as well as all the front surfaces which are not normally exposed, are well finished with genuine walnut veneer. With the cloth-covered, tapered face speaker grille attached (by means of plastic plug-in clips), the unit presents an extremely neat and particularly attractive appearance. The cabinet is constructed from moderately heavy medium density particleboard, the surfaces of which are reasonably well damped on the top and bottom panels, but not as well damped on the two sides or rear.

The inside of the cabinet uses a glue bonded open cellular urethane foam on all secondary surfaces and the speaker cross-

over uses hard-wired second order low pass and high pass filter sections, which are screw fixed on the inside of the back panel. The recessed speaker terminals use a pair of gold-flashed screw terminals of unusual design, which will accept both spade lugs or bared wires up to 4mm in diameter.

Objective testing

I was a little apprehensive before the first stage of the objective testing, as I had previously been very critical of the Tannoy "Little Red" monitors. The first series of tests to determine frequency response in my anechoic room, revealed a rather unusual phenomenon, namely a strange notch in the response at 180Hz which the second speaker also showed. A closer examination of the speaker revealed something that neither my staff nor I had seen for quite a while. The design of the speaker's rolled flexible edge gives rise to a 'rim resonance' effect where the flexible surround interacts with the oscillating section of the diaphragm to produce an effective null at one specific frequency. This cancellation phenomenon is both frequency and position dependent, so that the interference frequency drops with increasing distance from the speaker cabinet. The interference is more significant when measuring on the direct axis of the speaker and is relatively insignificant at 30° off-axis. You would be hard pressed to easily hear or even detect this interference phenomenon during normal programme content because of the selectivity of the interference pattern, but it did disturb me for more than a few minutes until I worked out what was happening.

When I had overcome my initial distract-

tion, I was able to observe that the frequency linearity of the M20s from 100Hz to beyond 20kHz was remarkably good and, although the output dropped off fairly quickly below 100Hz, it was still reasonably good all the way down to 60Hz. With increased measurement distance from the face of the speaker (on-axis measurements at 2m), the picture did not change markedly although the interference between the venting port and the woofer does affect the shape of the low frequency response in the 80Hz to 140Hz region.

The response at 30° to the main axis is still exceptionally good and the output at 20kHz is only 6dB down from the on-axis response, which is more a credit to the designers of the tweeter than it is to the designers of the system. The near-field measurements at 5cm from the face of the woofer and tweeter revealed that the cross-over frequency is approximately 2.2kHz, rather than the 3kHz frequency specified in the technical literature. The woofer response is particularly smooth and when measured at such close proximity, the problems of interaction with the venting port are insignificant.





The frequency response exhibits a degree of linearity which is comparable with that provided by many monitor speakers and which quite a few would be hard pressed to match.

The impedance characteristics are very unusual in that they exhibit two high peaks at 18Hz and at 71Hz where the impedance values are 57 and 51 ohms, respectively. Whilst most modern amplifiers would not be disturbed by such unusually high impedances, there is always a possibility that cheaper amplifiers or even low-powered amplifiers would be driven into overload or instability as a result of these characteristics.


The measured phase response of the speaker proved to be exceptionally smooth and the level recording exhibits a degree of phase linearity which is very much in keeping with the more comprehensive picture provided by the decay response spectra. In this respect, although the speaker may be only modest in price, the designers have achieved very commendable results.

Having seen these characteristics, I was not the least bit surprised to find that the polar responses are equally good. Each of the plots recorded at 1kHz, 3kHz, 6.3kHz is clearly excellent. The 6.3kHz response provides a bandwidth which is within 6dB over an arc of 150° whilst the bandwidth and uniformity of the response at 10kHz is outstanding at within 6dB over a 110° arc. The overall performance within the conventional specification arc of 60° is more than somewhat better than that provided by most other quality speakers selling at two or even three times the price.


Polar response plots.

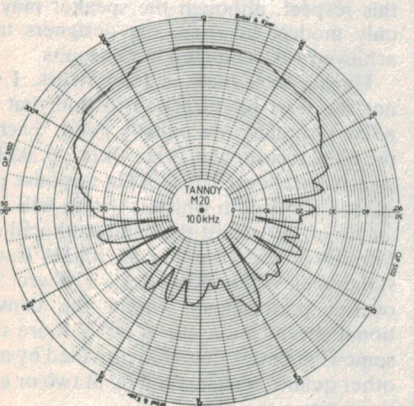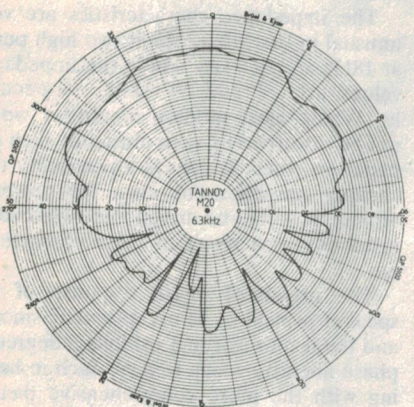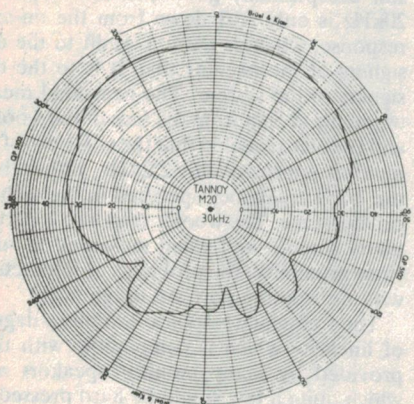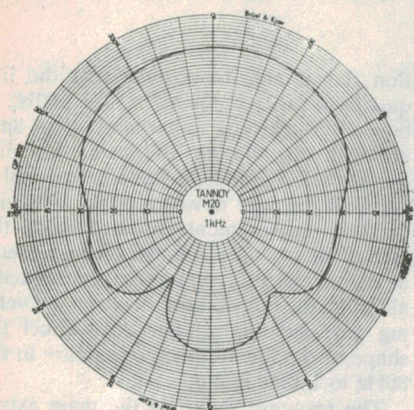

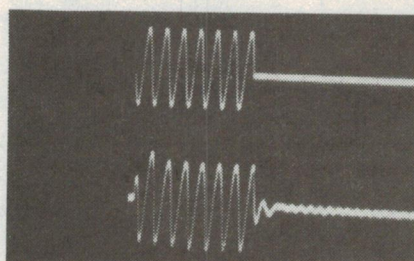
Tone burst response. Upper trace is electrical input; lower trace is loudspeaker output.



100Hz (20ms/div)

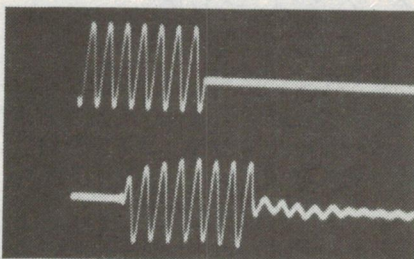

1kHz (2ms/div)

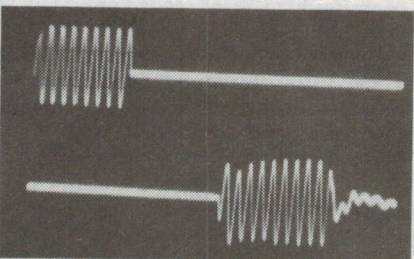

6.3kHz (0.5ms/div)

The tone burst evaluation revealed some traces of ringing, particularly at 1kHz and 6.3kHz, although the magnitudes of these post-transient perturbations are by no means unusual. The decay response spectra however showed an unusually smooth performance with almost optimal linearity within the first 15dB of the decay and remarkably little by way of ringing effects or resonance in the normal mid-frequency region. What ringing is visible occurs primarily at 6kHz and 11kHz as well as over the 9 to 11kHz range which corresponds to a natural resonance in the tweeter. Even these characteristics are reasonably well controlled and sufficiently attenuated below the fundamental to give rise to only very modest colouration.

The measured harmonic distortion characteristics of the speaker revealed fairly healthy distortion at 100Hz where the power level had to be reduced to 90dB to achieve a 4.2% distortion and much lower distortion at 1kHz where, with the normal 96dB output, only 1% distortion resulted. At 6.3kHz, the distortion is relatively low with only 0.5% distortion resulting from the 96dB output at 1m.

The sensitivity is moderately low as the speaker requires an indicated 10 watts of power to provide 96dB at 1m. My overall impression of the objective performance of the Tannoy M20s is that they provide an above average performance which is essentially very good.

Subjective testing

The initial subjective impressions of the M20s was derived using the Swedish Hi-Fi Institute test record "LJUD och hur det ska

MEASURED PERFORMANCE OF : TANNOY M20 GOLD LOUDSPEAKERS
SERIAL NO : 885811

FREQUENCY RESPONSE : On-axis 60 Hz to 20 kHz -10 dB
30° Off-axis 60 Hz to 20 kHz -10 dB
CROSSOVER FREQUENCIES : 2.7 kHz

SENSITIVITY :
(for 96 dB average at 1m) 9.0 V r.m.s. = 10.1 Watts (nominal into 8 Ohms)

HARMONIC DISTORTION: (for levels indicated)	90 dB			96 dB			96 dB		
	100Hz	1kHz	6.3kHz	100Hz	1kHz	6.3kHz	100Hz	1kHz	6.3kHz
2nd	-27.8	-40.5	-47.3	-27.8	-40.5	-47.3	-27.8	-40.5	-47.3
3rd	-41.0	-49.6	-52.5	-41.0	-49.6	-52.5	-41.0	-49.6	-52.5
4th	-56.1	-67.5	-	-56.1	-67.5	-	-56.1	-67.5	-
5th	-51.3	-69.6	-	-51.3	-69.6	-	-51.3	-69.6	-
THD	4.2	1.0	0.49	4.2	1.0	0.49	4.2	1.0	0.49

INPUT IMPEDANCE

100Hz/7kHz 4:1

100 Hz	11.6 ohms
1 kHz	31.2 ohms
6.3 kHz	9.6 ohms
Min at 150 Hz	9.2 ohms

PEAK IMPEDANCES

at 18 Hz, 71 Hz and 1200 Hz.

lata". The results of this were to confirm that the speaker provides a crisp, relatively clean output with modest colouration and extremely neutral performance on most orchestral music. The last and most difficult test track on the record surprisingly revealed that the speaker had no difficulty handling its nasty low frequency content with input peak power levels of up to 300 watts and outputs in excess of 105dB at my normal monitoring position.

With the test 'speech and singing' reference content, the immediate impression gained was of a speaker with a degree of natural reproduction, which is above average and both male and female voices sound as they should. With Virgil Fox's "The Digital Fox" (Ultragroove UG9001), the speakers happily replayed the strident and persuasive power of the Garden Grove Community Church pipe organ with a realism and fidelity which I found positively surprising. My B&W 801F monitors provided a cleaner low frequency on the lowest organ notes, but considering the price difference, I was nonetheless impressed.

With the Sheffield Tract Record, the immediate impression I gained was of a speaker which provides superlative re-

sponse for percussive instruments, remarkable stereo imaging, crisp rise times, clean decay times and acceptable colouration with peak power levels ranging up to 600 watts. Had I a more powerful amplifier than the Yamaha M80 that I was using, I think I would have been scared to apply it for fear of destroying the drivers as this speaker system does not incorporate a protection circuit. Even so, I really belted the speakers with continuous average listening levels of over 60 watts input and peak levels repeatedly pushing the stops on the amplifier, and failed to destroy the speakers.

The next series of test material came from CD discs, including Sheffield Lab's "Crème de la Crème", track 2 "The Higher You Rise", track 4 "Gone Buttlefishin'" and track 5 "Cripple Creek Breakdown" which provided superb examples of snare and kick drum, organ and xylophone in which the Tannoys absolutely revelled.

With the first track of Elton John's "Ice on Fire" (Rocket 826-213-2), I pushed the peak input levels again to beyond 600 watts, whilst with track 3 "Soul Glove" I pushed as hard as I dared with the amplifier's input line attenuators set to minimum. The peak signal levels were by this stage topping

110dB and the distortion, although clearly audible was still acceptable

The last disc I used was Don Dorsey's "Bachbusters" (Telarc CD 80123) which is a remarkable moog synthesiser-based disc of some of Bach's finest organ and orchestral works. The subsequent discs that I used were all classical, and I must acknowledge played at lower, more acceptable levels.

My overall impression of the Tannoy M20 "Golds" is of a well designed speaker which achieves a surprisingly good subjective performance for most recorded classical music, good performance on popular music and more than acceptable performance when pushed hard to reproduce rock music.

Considering the miniscule size of their enclosures, the M20s provide a healthy performance with truly exceptional stereo imaging over an unusually broad arc. This is matched by a superlative high frequency response over the critical 10kHz to 20kHz region where most other speakers in their price range do not perform nearly as well.

Whilst I have previously been critical of Tannoy loudspeakers, I believe that their designers have achieved an unusually noteworthy result with the M20 "Gold" speakers which justly deserve the *gold* title. ●

READER INFORMATION SERVICE COUPON

Electronics Today

READER INFORMATION SERVICE

POST TODAY!

To find out more about the products and services in this issue, circle the READER SERVICE NUMBER from the advertisement, photocopy this coupon, enclose it in an envelope and send to: FREEPOST No 4

The Federal Publishing Company
PO Box 227
Waterloo, NSW 2017

No stamp necessary if posted in Australia

A. Engineer/Designer

B. Technician

C. Manager

D. Hobbyist

E. Interested Consumer

Please circle
the category
that best
fits you.

Name

Address

Postcode

1	26	51	76	101	126	151	176	201	226	251	276	301	326
2	27	52	77	102	127	152	177	202	227	252	277	302	327
3	28	53	78	103	128	153	178	203	228	253	278	303	328
4	29	54	79	104	129	154	179	204	229	254	279	304	329
5	30	55	80	105	130	155	180	205	230	255	280	305	330
6	31	56	81	106	131	156	181	206	231	256	281	306	331
7	32	57	82	107	132	157	182	207	232	257	282	307	332
8	33	58	83	108	133	158	183	208	233	258	283	308	333
9	34	59	84	109	134	159	184	209	234	259	284	309	334
10	35	60	85	110	135	160	185	210	235	260	285	310	335
11	36	61	86	111	136	161	186	211	236	261	286	311	336
12	37	62	87	112	137	162	187	212	237	262	287	312	337
13	38	63	88	113	138	163	188	213	238	263	288	313	338
14	39	64	89	114	139	164	189	214	239	264	289	314	339
15	40	65	90	115	140	165	190	215	240	265	290	315	340
16	41	66	91	116	141	166	191	216	241	266	291	316	341
17	42	67	92	117	142	167	192	217	242	267	292	317	342
18	43	68	93	118	143	168	193	218	243	268	293	318	343
19	44	69	94	119	144	169	194	219	244	269	294	319	344
20	45	70	95	120	145	170	195	220	245	270	295	320	345
21	46	71	96	121	146	171	196	221	246	271	296	321	346
22	47	72	97	122	147	172	197	222	247	272	297	322	347
23	48	73	98	123	148	173	198	223	248	273	298	323	348
24	49	74	99	124	149	174	199	224	249	274	299	324	349
25	50	75	100	125	150	175	200	225	250	275	300	325	350

For a prompt reply: Post today!

METEUX MULTIMETERS

These instruments are compact, rugged, battery operated, hand held 3 1/2 digit multimeters. Dual-slope A-D converters use C-MOS technology for auto-zeroing, polarity selection and over-range indication. Full overload is provided.

SAVE \$20 DURING JUNE

METEUX 3800 MULTIMETER

- Features...**
- Push-button ON/OFF power switch.
 - Single 30 position easy to use rotary switch for FUNCTION and RANGE selection.
 - 1/2" high contrast LCD.
 - Automatic over-range indication with the "1" displayed.
 - Automatic polarity indication on DC ranges.
 - All ranges fully protected plus Automatic "ZERO" of all ranges without short circuit except 200 ohm Range which shows "000 or 001".
 - High Surge Voltage protection 1.5 KV-3 KV.
 - Diode testing with 1 mA fixed current.
 - Audible Continuity Test.
 - Transistor hFE Test.

SPECIFICATIONS
Maximum Display: 1999 counts 3 1/2 digit type with automatic polarity indication.
Indication Method: LCD display.
Measuring Method: Dual-slope in A-D converter system.
Over-range Indication: "1" Figure only in the display.
Temperature Ranges: Operating 0°C to +40°C.
Power Supply: one 9 volt battery (006P or FC-1 type of equivalent).
Cat. Q91530 Normally \$99.95
SPECIAL \$79.95

SAVE \$20 DURING JUNE

METEUX 3530 MULTIMETER

- Features...**
- Push-button ON/OFF power switch.
 - Single 30 position easy to use rotary switch for FUNCTION and RANGE selection.
 - 1/2" high contrast LCD.
 - Automatic over-range indication with the "1" displayed.
 - Automatic polarity indication on DC ranges.
 - All ranges fully protected plus Automatic "ZERO" of all ranges without short circuit except 200 ohm Range which shows "000 or 001".
 - High Surge Voltage protection 1.5 KV-3 KV.
 - Capacitance measurements to 1pF.
 - Diode testing with 1 mA fixed current.
 - Audible Continuity Test.
 - Transistor hFE Test.

SPECIFICATIONS
Maximum Display: 1999 counts 3 1/2 digit type with automatic polarity indication.
Indication Method: LCD display.
Measuring Method: Dual-slope in A-D converter system.
Over-range Indication: "1" Figure only in the display.
Temperature Ranges: Operating 0°C to +40°C.
Power Supply: one 9 volt battery (006P or FC-1 type of equivalent).
Cat. Q91540 Normally \$129
SPECIAL \$109

SAVE

PC BOARD HOLDER

Better than an extra pair of hands! A must for all PCB work.
Cat. T12442 Normally \$9.95
SPECIAL, ONLY \$8.95

SAVE

TV INTERFERENCE FILTER
Cuts CB/Ham signals interference.
Cat. L11048 Normally \$5.95
SPECIAL, ONLY \$4.95



SOLDER ROLLS

Cat.No.	Description	Price
T31000	71mm 250gm	\$8.95
T31002	71mm 500gm	\$15.95
T31010	91mm 250gm	\$7.95
T31012	91mm 500gm	\$14.95
T31020	1.6mm 250gm	\$7.50
T31022	1.6mm 500gm	\$13.95
T31030	91mm 1 metre	\$1.50
T31032	91mm 1 metre	\$1.25
T31034	1.6mm 1 metre	\$1.00




Cat.No.	Description	Price
P17016	16 pin	\$14.50
P17024	24 pin	\$14.50
P17028	28 pin	\$19.50
P17040	40 pin	\$22.50



COMPUTER AND DISK DRIVE CASES AND POWER SUPPLIES


5 1/4" DRIVES		
1 x 5 1/4" Slimline Drive Case	X11001 Bare Case	\$49
1 x 5 1/4" Slimline Drive Case	X11011 Case & Pwr Supply	\$109
2 x 5 1/4" Slimline Drive Case	X11002 Bare Case	\$69
2 x 5 1/4" Slimline Drive Case	X11012 Case & Pwr Supply	\$149
1 x 5 1/4" Standard Drive Case	X11003 Bare Case	\$45
1 x 5 1/4" Standard Drive Case	X11013 Case & Pwr Supply	\$109
2 x 5 1/4" Standard Drive Case	X11004 Bare Case	\$59
2 x 5 1/4" Standard Drive Case	X11014 Case & Pwr Supply	\$149

8" DRIVES		
1x 8" Standard or 2 x 8" Slimline. and computer Case (BB1)	X11006 Bare Case	\$99
1x 8" Standard or 2 x 8" Slimline. and computer Case (BB1)	X11016 Case & Pwr Supply	\$399
2 x 8" Slimline Drives and Computer Case (BB1 and BB2 etc)	X11007 Bare Case	\$145
2 x 8" Slimline Drives and Computer Case (BB1 and BB2 etc)	X11017 Case & Pwr Supply	\$399
1 x 8" Slimline Drive Case	X11020 Bare Case	\$95
1 x 8" Slimline Drive Case	X11022 Case & Pwr Supply	\$159
Dual 8" Slimline Drive Case	X11025 Bare Case	\$99
Dual 8" Slimline Drive Case	X11026 Case & Pwr Supply	\$275

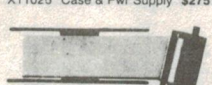


GREY FLAT RIBBON CABLE

Cat No.	Description	S/Mtr
W12614	14 Way	\$1.90
W12616	16 Way	\$2.00
W12620	20 Way	\$2.30
W12624	24 Way	\$2.60
W12625	25 Way	\$2.70
W12626	26 Way	\$2.80
W12634	34 Way	\$3.50
W12636	36 Way	\$3.60
W12640	40 Way	\$3.90
W12650	50 Way	\$4.90
W12660	60 Way	\$6.90

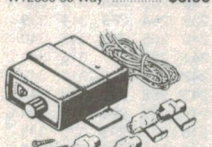

WIPER DELAY CONTROLLER AND LIGHT ON REMINDER

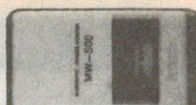- Triggers if lights are left on and ignition is turned off.
 - Has both an audible and visible alarm.
 - Allows windshield wipers to be delayed for up to 20 seconds.
 - Underdash or on dash mounting.
 - Designed for 12 volt negative earth electrical systems.
 - Complete with mounting hardware.
- Cat. A15070 **\$24.95**



MICROWAVE LEAKAGE MONITOR

Simple to use, this microwave leakage detector can be used to protect you and your family by periodically checking around the hinges, door seals, etc. of your microwave for hazardous excessive leakage.
Cat. A30001 **only \$12.95**



NEW SLOPING CASES

Plastic with metal front panel, available in two sizes:
Cat. H10450 190x120mm **\$12.95**
Cat. H10455 250x185mm **\$21.95** (measurements are approx. only)



RITRON 19" RACK CASE

Tremendous Value! Dimensions 480(W) x 134(H) x 250(D)mm.
Cat. H10415 Normally \$47.95
SPECIAL, ONLY \$37.95



RITRON KEYLESS CAR ALARM

- The first shipment sold out immediately to the trade. They didn't reach our own retail stores!
- Activated and disarmed by ignition key, so you never forget to turn it on.
 - Multi-function, built in siren or external siren, car signal horn output.
 - Easy to install, no door switch required.
 - Automatic reset after 60 seconds (avoids noise pollution).
 - Special sensor protects Stereo or CB.
 - 12V DC
- Cat. S15054 Normally \$39.95
NOW \$29.95



OMNI-DIRECTIONAL WIRELESS MICROPHONE

Tunable: 92 - 104MHz
Freq. Response: 50 - 15kHz
Range: Over 300 feet in open field.
Modulation: FM
Power Source: 9V Battery
Type: Electret Condenser
Dimensions: 185 x 27 x 38mm
Weight: 160 grams
Cat. A10450 **\$19.95**



ARLEC SUPER TORCH

- A sophisticated rechargeable torch ideal for use in and around the home, the car, the boat, etc.
- FEATURES:**
- Powerful built-in Nicad batteries.
 - Reflector head swivel through 90 degrees.
 - 3 position switch gives on/off and dim.
 - Indicator lamp when recharging.
 - Charges from mains, electricity or from a car battery.
 - Supplied complete with (A) SEC approved battery charger (B) Plug and cord for car lighter socket.
 - Handy charging bracket with fixing screws.
 - 12 months guarantee.
- Cat. A15055 Normally only \$44.95
SPECIAL, ONLY \$39.95

WHAT'S NEW?



CENTRONICS GENDER CHANGER

- Female to Female.
 - Saves modifying or replacing non-mating Centronics cables.
 - All 36 pins wired straight through.
- Cat. X15662 **\$33.95**



ARGUS 726 ADJUSTABLE MAGNIFIER WITH LAMP

Absolutely perfect for close up work! Intricate PCB's, projects, etc. will be a breeze under this superb, adjustable magnifying lamp.

- Magnifies 1.75 times
- 40 watt incandescent lamp
- 2 spring-balanced arms, extendable to 95cm
- Adjustable head for optimum viewing angle
- Fantastic Value!

Cat. **only \$89**




CIS 5 1/4" D/S DISKS

100% certified and error free guaranteed! Where else can you get 100% guaranteed D/S D/D disks for just \$24.95?!!
Cat. C12440 **ONLY \$24.95**
"Less 10% for 10 or more!!"




PROGRAMMABLE 24 HOUR TIME SWITCH

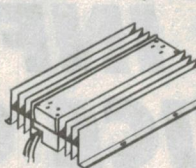- 48 switching possibilities per day
 - 240V AC, 2400 watt, 10 amp
 - Suitable for turning on... Heaters/Coolers pool filter electric blankets cooking appliances waking you, even making the coffee! lights etc for security while you're away from home!
 - Bargain Price!
- Cat. M22002 **only \$19.95**




REGULATED DC-DC CONVERTER

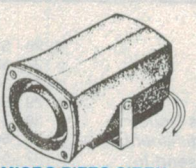- Built on to a heavy duty aluminium heatsink with 7 amps. Ideal for trucks and boats.
- Input 24V DC
 - Output 12V DC at 7 amps
 - Fully regulated with short circuit protection
 - Size: 180(L) x 94(W) x 33(H)mm
- Cat. A15056 **\$33.95**



MICRO PIEZO SIREN

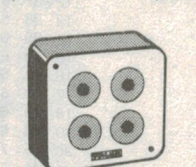- Very small and easy to install.
 - High impact plastic, (white).
 - Input 12V DC - 150mA
 - Output 110dB at 1 metre, dual tone.
- Cat. S15069 **\$13.95**



PIEZO SIREN

- 4 piezo units in a high impact plastic cabinet
 - Input 12V DC - 200mA
 - Output 115dB at 1m, dual tone
 - Compact size 105 x 85 x 45mm
 - Smart design suits interior use
- Cat. S15071 **\$23.95**



"SNAP TOGETHER" PLASTIC CABINET

Top and bottom simply snap together (no screws required), removable front and back panels.
Dimensions: 186(W) x 125(D) x 50(H)mm
Cat. H10116 **\$6.95**



HI FI SPEAKERS

A comprehensive range of matched appearance speakers, all with square silver grey frames and black cones - ideal for building up low cost speaker systems that will look and sound superb.




1 1/2" TWEETER

SPECIFICATIONS:
Sensitivity: 90dB
Freq. Response: 1.2 - 20 kHz
Impedance: 8 ohms
Power RMS: 10 watts
Magnet Weight: 2 oz
Cat. C10200 **\$4.95**



2 1/2" TWEETER

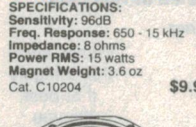SPECIFICATIONS:
Sensitivity: 94dB
Freq. Response: 1.1 - 17 kHz
Impedance: 8 ohms
Power RMS: 10 watts
Magnet Weight: 2 oz
Cat. C10202 **\$5.95**



4" MIDRANGE WITH SEALED BACK

SPECIFICATIONS:
Sensitivity: 96dB
Freq. Response: 650 - 15 kHz
Impedance: 8 ohms
Power RMS: 15 watts
Magnet Weight: 3.6 oz
Cat. C10204 **\$9.95**



4 1/2" MIDRANGE WITH SEALED BACK

SPECIFICATIONS:
Sensitivity: 97dB
Freq. Response: 600 - 8 kHz
Impedance: 8 ohms
Power RMS: 20 watts
Magnet Weight: 5.4 oz
Cat. C10206 **\$12.95**



6 1/2" WOOFER

Cloth edge roll surround. SPECIFICATIONS:
Sensitivity: 96dB
Freq. Response: 55 - 7 kHz
Impedance: 8 ohms
Power RMS: 15 watts
Magnet Weight: 5.4 oz
Cat. C10208 **\$15.95**




8" WOOFER

RIBBED CONE Cloth edge roll surround. SPECIFICATIONS:
Sensitivity: 94dB
Freq. Response: 55 - 8 kHz
Impedance: 8 ohms
Power RMS: 15 watts
Magnet Weight: 5.4 oz
Cat. C10210 **\$18.95**



10" WOOFER

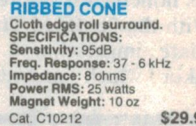RIBBED CONE Cloth edge roll surround. SPECIFICATIONS:
Sensitivity: 95dB
Freq. Response: 37 - 6 kHz
Impedance: 8 ohms
Power RMS: 25 watts
Magnet Weight: 10 oz
Cat. C10212 **\$29.95**



12" WOOFER

RIBBED CONE Cloth edge roll surround. SPECIFICATIONS:
Sensitivity: 92dB
Freq. Response: 32 - 4 kHz
Impedance: 8 ohms
Power RMS: 30 watts
Magnet Weight: 13.3oz
Cat. C10214 **\$39.95**



PIEZO DIRECT RADIATING TWEETER

Requires no crossover, handles up to 100 watts.
Sensitivity: 96dB
Maximum input: 24 volts
Freq. Response: 3.2 - 30kHz
Dimensions: 95mm diameter.
Cat. C12104 **\$11.95**



12" HIGH POWER MUSICAL SPEAKER

• Aluminium die cast chassis
• Carbon fibre impregnated cone paper
• Foam edge
• Light grey cone, silver dust cap
• High temperature "NOMEX" voice coil.
SPECIFICATIONS:
Sensitivity: 97dB
Frequency Response: 50-4kHz
Impedance: 8 ohms
Power RMS: 60 watt
Magnet Weight: 30 oz.
Cat. C10216 **\$59.95**



10W HORN SPEAKERS
White durable plastic, 8 ohms
Cat. C12010 Normally \$9.95
SPECIAL, ONLY \$7.95



UV EPROM ERASER
Erase your EPROMs quickly and safely. This unit is the most effective solution to your problems. It will erase up to 9 x 24 pin devices in complete safety, in about 40 minutes (less for less chips).
Features include:
• Chip drawer has conductive foam pad
• Mains powered
• High UV intensity at chip surface ensures EPROMs are thoroughly erased
• Engineered to prevent UV exposure
• Dimensions 217 x 80 x 68mm
Cat. X14950 **NORMALLY \$99.95**
SPECIAL, ONLY \$89.95



STANDARD DESOLDERING PUMP
Light weight, powerful suction, teflon tip. Replacement tips teflon and ceramic. Length 195mm.
Cat. T11241 **\$16.95, Now \$14.95**

MINI DESOLDERING PUMP

Light weight, powerful suction, teflon tip. Replacement tips teflon and ceramic. Length 165mm.
Cat. T11251 **\$15.95, Now \$13.95**


DELUXE DESOLDERING PUMP

Light weight, non conductive, powerful suction, ceramic long life tip. One of the best in the business. Length 210mm, replacement tip HT3C ceramic.
Cat. T11261 **\$22.95, Now \$19.95**



CORDLESS RECHARGEABLE SOLDERING IRON

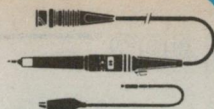• Built in solder point illumination
• Easy replacement of solder tip
• Protective stand which also functions as charging unit
• Sponge pad attach to stand
• Plug pack power adaptor
• Includes Nicad battery
• Instruction manual
• 12 months warranty
Cat. T12480 **Normally \$59.95**
SPECIAL, ONLY \$49.95



BESWICK 88100 PROBE SET

CONTAINS: Compensated probe lead with:
• Detachable 6 inch earth lead
• Retractable hook
• IC test tip
• Tip insulator
• BNC adaptor
• Trimming tool
SPECIFICATIONS:
Bandwidth: 10:1 position :250MHz at -3dB into 20 pF
Rise Time: 10:1 position less than 1.4ns nominal
Switch Function:
(a) 10:1 attenuation +/- 1%, with oscilloscope of 1 Mohm input resistance.
(b) 1:1 attenuation with bandwidth of 10 MHz approx.
(c) Reference position, tip grounded via 9 Mohm, oscilloscope input grounded.
Input Capacitance: 16pF typical depending upon oscilloscope input capacitance.
Compensation Range: oscilloscopes of 15 to 60 pF input capacitance.
Working Voltage: 600V DC or peak AC
\$34.95



WELLER WTCPN SOLDERING STATION
The WTCPN Features:
• Power Unit 240 V AC
• Temperature controlled iron, 24 V AC
• Flexible silicon lead for ease of use
• Can be left on without fear of damaged tips!
The best is always worth having.
Cat. T12500 **R.R.P. \$129**
SPECIAL, ONLY \$99



ARLEC SUPER TOOL
A versatile 12V electric tool for...
• Sanding
• Engraving
• Grinding
• Polishing
• Cutting
• Drilling
• Milling
• Erasing, etc.
Features:
Operates on safe, low 12 volts from mains electricity via AC adaptor (supplied). Light and easy to handle with touch switch and lock for continuous running. High torque motor, 10,000 R.P.M. Can drill 2mm holes in steel. 2 year guarantee
Contents:
• 12V Super Tool
• Plugpack AC adaptor
• 1 spherical milling cutter
• 1 wire brush
• 1 grinding wheel
• 4 drill bits, 0.6, 0.8, 1.0, 1.2mm
• Set of 5 chuck collets
• 6 eraser sticks
• Instruction sheets
Cat. T12300 **NORMALLY \$49.95**
SPECIAL, ONLY \$44.95



AA NICADS (ROCKET BRAND)
Save up to 50% off the regular price of \$2.80!
1-9 10+ 100+
\$1.75 \$1.65 \$1.40



DIGITAL SPEEDO/DIGITAL TACHO/SPEED ALERT
• Digital readout (LED) for both tacho and speed.
• Alarm with sound at variable preset speed.
• Audible beeper and visual indicator.
• In built light indicator for night illumination.
• Designed for 12 volt negative earth electrical systems.
• Speed: 0 - 199kph
• Tachometer: 0 - 9900kph
• Speed alert: 40 - 120kph
• Complete with mounting hardware.
Cat. A15064 **Normally \$69.50**
SPECIAL, ONLY \$59.50



FREE STANDING, FOLD UP MAGNIFIER
An economically priced "hands free" magnifier, lets you take care of all those tricky fine detailed jobs so often encountered in electronics, or any of many other practical uses such as home, work, hobbies etc.
Cat. T12083 **Normally \$14.95**
SPECIAL, ONLY \$12.95



RECHARGEABLE 12V GELL BATTERIES
Leakproof and in 3 convenient sizes, these long service life batteries are ideal for burglar systems, emergency lighting or as a computer backup power supply. Ideal for many power needs.
Cat. S15029 12V 1.2 AH **\$12.95**
Cat. S15031 12V 2.6 AH **\$39.50**
Cat. S15031 12V 4.5 AH **\$49.95**



LOGIC PROBE 3800A
Features 20MHz memory. TTL/CMOS operation. Normally \$29.50
Cat. Q11272 **\$34.50**
SPECIAL, ONLY \$29.30

SAVING'S BONANZA!

No.1 FOR COMPONENTS!

IC SPECIALS!

	1-9	10+	100+
4116	\$2.95	\$2.75	\$2.50
4164	\$2.95	\$2.75	\$2.50
2716	\$5.90	\$5.50	\$5.50
2732	\$6.25	\$5.95	\$5.50
2764	\$6.25	\$5.95	\$5.00
27128	\$6.95	\$6.50	\$6.25
6116	\$2.95	\$2.75	\$2.50
41256	\$6.95	\$6.50	\$6.00
6264	\$6.50	\$5.50	\$5.25
27256	\$11.50	\$10.50	\$10.00

WORLD MODEM CHIP
Cat. U21614 **Normally \$49.50**
Save \$20, SPECIAL \$29.50

IC SPECIALS! 8000 SERIES!

	1-9	10+
8085	4.50	3.50
8212	1.50	1.40
8216	1.50	1.40
8226	1.70	1.50
8243	4.50	3.90
8251	3.90	3.50
8253	3.50	3.30
8255	2.90	2.50
8257	3.50	3.10
8259	3.50	3.10
8279	3.50	3.10
2532	7.50	6.90
2764	5.50	5.10
27128	7.50	6.90
1488	55	45
1489	55	45

DIODES SPECIALS

	1-9	10+	100+	1000+
IN4148 Cat. Z10135	3c	2 1/2c	2c	1 1/2c
IN4002 Cat. Z10150	4c	3c	2 1/2c	3c
IN4004 Cat. Z10107	5c	4c	3c	2 1/2c

CRAZY SPECIAL!

CRYSTALS SPECIALS
We simply have too many of these prime spec. crystals in stock!

Description	Cat.No.	1-9	10+
1MHz	Y11000	\$6.00	\$5.20
1.8432MHz	Y11003	\$6.00	\$5.20
4MHz	Y11020	\$2.00	\$1.60
4.194304MHz	Y11022	\$2.00	\$1.60
4.433618MHz	Y11023	\$2.00	\$1.60
4.75MHz	Y11025	\$2.00	\$1.60
4.915200MHz	Y11026	\$2.00	\$1.60
5MHz	Y11030	\$2.00	\$1.60
6MHz	Y11040	\$2.00	\$1.60
6.144MHz	Y11042	\$2.00	\$1.60
6.670MHz	Y11045	\$2.00	\$1.60
8MHz	Y11050	\$2.00	\$1.60
8.867238MHz	Y11055	\$2.00	\$1.60
10MHz	Y11060	\$2.00	\$1.60
12MHz	Y11070	\$2.00	\$1.60
14.31818MHz	Y11072	\$2.00	\$1.60
15MHz	Y11075	\$2.00	\$1.60
18MHz	Y11082	\$2.00	\$1.60
18.432MHz	Y11085	\$2.00	\$1.60
20MHz	Y11090	\$2.00	\$1.60

RCA GOLD PLATED PLUGS AND SOCKETS
For those who need the ultimate in connection. Essential for laser disc players to get that fantastic sound quality.
Plug Cat. P10151 **\$3.50**
Socket Cat. P10150 **\$2.75**



RELAYS

	1-9	10+
Massive 3A connectors.		100+
S.P.D.T. S14060	\$1.20	\$1.00
D.P.D.T. S14061	\$1.50	\$1.25

MINIATURE BUZZER
5-15V White or black.
Cat. C15062 **\$0.95**

RS232 & 'D' TYPE SPECIALS

Part Description	Cat.No.	Price
DE9S 9 pin Female	P10881	\$1.75
DE9P 9 pin Male	P10880	\$2.25
DE9C 9 pin cover	P10882	\$1.95
DA15P 15 pin Male	P10890	\$2.10
DA15S 15 Female	P10891	\$2.25
DA15C 15 pin cover	P10892	\$1.15
DB25P 25 pin Male	P10900	\$1.95
DB25S 25 Female	P10901	\$2.95
DB25C 25 pin cover	P10902	\$1.20

12 WAY TERMINAL BLOCKS

	Price
P18052 240V 10AMP	\$1.50
P18052 240V 15AMP	\$1.75

TRIGGER TRANSFORMERS
Cat. M10104 **\$1.20**

ECONOMY ROTARY SWITCHES

Cat. No.	Description	Price
S13021	1 pol 2-12 pos.	\$1.95 \$0.95
S13022	2 pol 2-6 pos.	\$1.95 \$0.95
S13033	4 pol 2-3 pos.	\$1.95 \$0.95
S13035	3 pol 2-4 pos.	\$1.95 \$0.95

20% OFF ALL TOGGLE SWITCHES!

TOGGLE SWITCHES

Cat.No.	Description	Price
S11009	SPST mini	\$1.20
S11010	SPDT econ mini	\$1.75
S11020	DPDT econ mini	\$1.95
S11025	C/Off econ mini	\$2.25
S11030	DPDT C/Off econ	\$2.50
S11034	4PDT mini	\$6.95
S11036	SPST std 125V 3A	\$1.30

SPRING RETURN TOGGLE SWITCHES

	1-9	10+
S.P.D.T. Cat. S11012	\$2.25	\$1.95
D.P.D.T. Cat. S11022	\$2.50	\$2.25




ROD IRVING ELECTRONICS
425 High Street, NORTHCOE, 3070 VICTORIA, AUSTRALIA
Phone (03) 489 8866
48 A Beckett St. MELBOURNE, 3000 VICTORIA, AUSTRALIA
Ph. (03) 663 6151
Mail Order and correspondence: P.O. Box 620, CLAYTON 3168
TELEX: AA 151938

MAIL ORDER HOTLINE (03) 543 7877 (2 lines)

POSTAGE RATES

\$1-\$9.99	\$2.00
\$10-\$24.99	\$3.00
\$25-\$49.99	\$4.00
\$50-\$99.99	\$5.00
\$100-\$199	\$7.50
\$200-\$499	\$10.00
\$500 plus	\$12.50

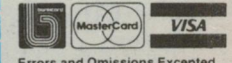This is for basic postage only. Parcel Road freight, bulky and fragile items will be charged at different rates.
Certified Post for orders over \$100 included "free"! Registered Post for orders over \$200 included "free"! All sales tax exempt orders and wholesale inquiries to RITRONICS WHOLESALE, 56 Renner Rd., Clayton. Phone (03) 543 2166



Errors and Omissions Excepted.

DIGITAL SAMPLER

Part 3: The sound of music

With the digital sampler built it's time to plug it in and put it to work. In this final part to the series we tell how to solve a problem like no echo as well as a few of our favourite things for the sampler.

**Glen Thurect
& Andrew Robb**

IN THIS, the final part of our series on the sampler we look at testing and using the unit. Before getting into that, we should outline what else is needed. The essentials are a microphone and some sort of amplifier. Obviously the better the mic, the better the sound, but that is up to you. The variable gain stage will accommodate most microphone types.

The sampler output level is around 140mVrms so the amp used should be able to handle this. You could use a home stereo set-up or, if available, a more rugged instrument amp.

Testing

Before applying the power, double check to see that the diodes are correctly orientated, all electrolytic capacitor polarities are in the right place, all integrated circuits have pin number one in the proper place (note that all the ICs face the same direction), wiring is as per the wiring diagram and that no solder has bridged between tracks during construction.

Now assuming all is well connect the 9V power supply plugpack and turn the power on. No smoke? Good, we can connect the amplifier and the sound source. Set the frequency control to about 50%, DELAY mode switch to DELAY, INT/EXT switch to INT and PLAY/RECORD to RECORD. Also keep MIX at 50% and REGEN to 0%. The gain control depends on the amplitude of the input signal and must be set by experimentation. Next make a short sound on the input. If the sampler is operating correctly, you should hear the original sound and shortly after, the delayed sampled sound. Set the gain to a point just below where distortion can be heard. If the unit passes this test it is almost certainly in proper working condition. If it produces no echoed signal, or no sound at all don't panic since troubleshooting will be looked at next.

To check the other modes of operation, firstly connect the 9V battery if you wish to keep the sample after power is removed and

then go on to "Using it".

The first thing to do when troubleshooting is to check all the power supplies. Using a multimeter set to dc volts see that the input 9Vdc from the powerpack does not exceed 15V. If it is above 15V or below 8V then the pack is probably faulty.

Before we continue you should remember that there are two system commons (or grounds) that are used. One is an analog common and the other is a digital common. When taking a voltage measurement at any point you must know what common it is referred to. If in doubt at any stage refer to the circuit diagram.

So, with reference to the analog common (say pin 3 or 5 of IC1) see that +V (pin 4, IC1) is between +4 volts and +7.5 volts. Also -V (pin 11, IC1) should be between -4 volts and -7.5 volts. Now if the two analog rails are unbalanced by more than 2 volts, IC1 or IC2 is drawing too much current and problems should be looked for in this region. Also look to see that R38 and R39 are the correct values. Switch your common connection to the digital one (say pin 12 of IC6) and look at pin 24 of IC6. This should be very close to 5 volts. If not, IC13 is likely to be faulty.

If the power supplies are working correctly and there is still no sound, re-check the wiring to the frequency pot to make sure that the clock is operating correctly. If you are not lucky enough to own an oscilloscope you can still test the clock by measuring the voltage on pin 3 of IC11 on the dc volts range of a multimeter. This should read between 2 and 3 volts since the clock is a square wave with fairly even mark/space ratio. If the reading is 0V or +5V (ref digital common) then the clock is not working so check all associated components R45, R44, C22, RV5 and, as a last resort, change IC11.

If there is a dc voltage of more than 20mV on the output (ref analog common) then IC1 is the likely culprit but check to see that the gain pot has been wired correctly,

specifically looking for dry joints on the connections.

For problems associated with the unit not triggering properly look firstly at the wiring of the threshold pot. Then measure on the 2Vdc range the voltage at pin 13 of IC1. This should vary between -10mV and approximately 1V as the pot is rotated. If not check values and solder joints of R33, R34, R35. Next, with no signal present, pin 12 of IC1 should be around -20mV. As an input is applied the dc voltage should change and go positive. If it doesn't, check for an ac signal at pin 1 of IC1 with an input present. For no ac voltage check components around IC1a, b, c. When the ac signal is there the fault lies with the precision rectifier based around IC4d.

If all these are OK but there is still no triggering, make sure D8 is the correct way around. The incorrect wiring of any of the switches will also prevent triggering, so carefully review this. Again, as a last resort if nothing else can be found, look at the input and output levels on IC10b, c, d, and IC9a, b, c, d. For a NOR gate if there is +5V on either input the output will be 0V. A NAND gate will have +5V output if either input is 0V. If the gates don't obey these rules replace the IC.

Another possible problem may arise if Q1 and Q2 are placed in the pc board the wrong way. This could mean that the chip select signals are not getting through to the memories. This can also cause large standby currents to be drawn from the battery when power is removed.

Now we will look at a few problems that could possibly occur when the unit is working but not sounding terribly good. Firstly, even though turning the frequency control to zero gives an apparent 3.4 second sample time, the sampler is only designed to give a 1/2 second sample. So if you set the frequency to below the 1/2 second point two things will occur: clock noise will be heard, and aliasing will corrupt the original signal. As a result, the frequency control should be

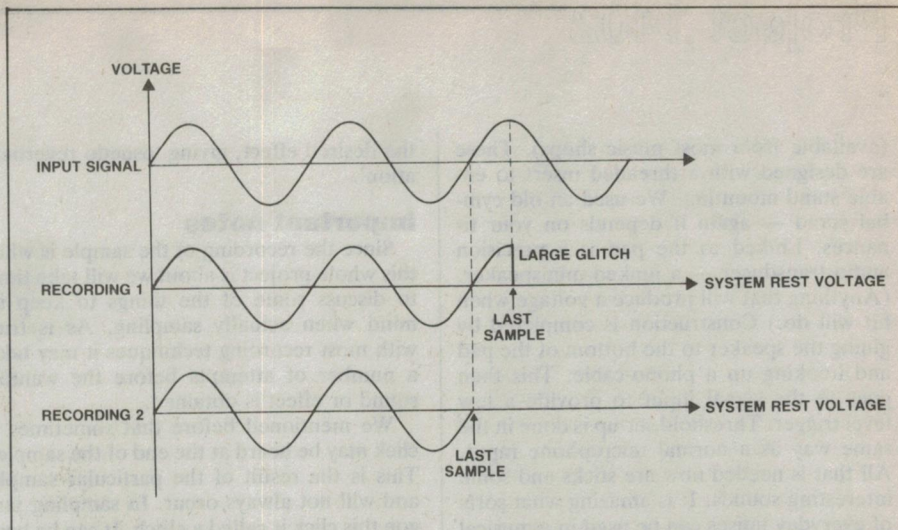


Figure 1. If it is not close to the system rest voltage, the last sample can produce an audible click.

set to approximately 60% or greater to do sound quality tests.

Assuming this has been done and the sampled sound is still squawking like a dalek then the anti-aliasing filter is not working. Check all component values associated with IC1b and IC1a paying particular attention to the capacitance values. If the signal is getting through to the ADC nothing much can be wrong other than incorrect filtering.

If the clock noise is heard at the output then the output filtering is at fault. Check all components around IC4a, b, and c.

Using it

Hopefully your sampler has passed the power-up smoke test without too much trauma — now we can properly explain how to use it and what all that unusual triggering logic is there for.

Throughout the testing you probably jumped the gun and started experimenting, but we will go through the complete operation anyway. Starting with a recording, switch to INTERNAL and RECORD (DELAY off). In this mode as soon as you hit the TRIGGER button, recording begins. Set REGEN to zero and GAIN about half way. The correct gain setting will depend on your mic. MIX should be fully clockwise, giving just the sampled sound. As you should know, having digested the theory part of this series, the sampler is designed around a storage time of a 1/2 second with a corresponding sampling rate of 8kHz. The actual clock design allows for a variable sample rate to produce pitch variation during playback. We'll talk more about this later, for now keep FREQ at about half way.

Now clear your throat and simultaneously speak and press. You should also hear the sound go directly to the amp (the DAC converts anything on the bus). Switch to PLAY and press again. Hopefully your voice should be faithfully reproduced.

There may be some clicks at the end of

the recording, we'll get on to them later as well. Now you can hear the result of varying FREQ — noting that clock noise will be expected below 1/2 second replay. Recording using INTERNAL triggering is useful when the sound being recorded is continuous. In this case manual control over the duration of recording is necessary. If the playback sounds distorted lower the gain accordingly for future recordings.

EXTERNAL recording allows more control over the triggering, particularly for sharp bursts of sound. Because it relies on the actual sound for triggering, an 'arming' phase is incorporated. This means you can set the unit up for recording without having to worry about accidentally bumping the microphone and triggering the thing off. Then, after arming, the next sound to cross the threshold-level triggers the recording. Unless you have ultra fast reflexes, this is the only way to fully record any sound. The sampler is armed to record by switching to EXTERNAL and pressing the TRIGGER pushbutton when ready. The only external trigger source of use when recording is the actual input signal. A bit of trial and error is needed to get the threshold setting to a point where it doesn't trigger until the desired moment, but is still sensitive enough to capture the complete sound.

Externally triggered, playback bypasses the arming step but is otherwise set up the same way. You don't need to switch to EXTERNAL (this control is only recognised when recording). If the TRIGGER threshold is turned fully anti-clockwise, the biasing set-up on the EXT TRIG input enables a short-circuit to trigger the comparator. A remote footswitch can then be used in the same way as the built-in pushbutton.

Increasing the threshold changes the biasing so that the comparator expects a more positive voltage for triggering. Thus any piece of equipment capable of generating a positive-going voltage pulse (not greater than about 5V) can be plugged into EXT TRIG (high level triggering). Alternatively

the low-level signal input can be used.

Because playback allows retriggering at any time, feeding an input signal straight into EXT TRIG would cause problems. The system would continually retrigger on every positive-going section of the waveform. To overcome this the signal, when fed into the low-level input, passes through a precision rectifier and filter which forms an accurate positive envelope follower. This ensures only one major leading edge per sound burst. For one trial we used a guitar to trigger the unit. Some rapid-retriggering did still occur occasionally until the threshold was increased to the level of the initial 'pick' spike.

That about covers the essential operations. More advanced recordings can be made by using the regeneration control. This controls the amount of playback signal fed back to the input. Beginning with REGEN off, record a simple sound. Now turn it to about half way and record another sound. The result will contain both recordings. By adjusting the amount of 'previous' sound you can create your own multi-part harmony. If the REGEN is set too high, the additional gain added with each regeneration will rapidly cause distortion.

Some interesting noises can be generated by using the feedback produced by the amplifier/microphone to trigger the unit. It is a bit hard to describe the result, so hold the microphone in front of your amp and trigger in EXTERNAL mode. The sound should retrigger continually at a particular point dependent on the distance between the mic and amp.

So far the unit has been fine for playing around with at home, but if you're more musically oriented you'll probably want something more dynamic. Instead of a continually bruised thumb (from rapping a microphone) you should rig up a drum-pad. Of course, if you have the bucks, you can buy professionally made pads but the home-made style will work just as well.

Begin with a commercial practice pad ▶

Project 1402

(available from most music shops). These are designed with a threaded insert to enable stand mounting. We used an old cymbal stand — again it depends on your finances. Linked to the pad is a precision audio transducer — a junked minispeaker. (Anything that will produce a voltage when hit will do.) Construction is completed by gluing the speaker to the bottom of the pad and hooking up a phono-cable. This then goes to the signal input to provide a low level trigger. Threshold set-up is done in the same way as a normal microphone input. All that is needed now are sticks and some interesting sounds. It is amazing what sorts of everyday noises can be used in a musical way. For every hour of our testing we spent another hour playing around with the wide variety of noises created simply using a microphone.

There is a lot of emphasis placed on communication or synchronisation between electronic instruments nowadays, the most prominent being the microprocessor-based MIDI interfacing system. On a less complex scale most synthesisers, sequencers and drum machines also have a separate trigger output suitable for use with our sampler. Depending on the type of pulse, you may have to use the low level input rather than the high level one. High level accommodates open/closed contacts or positive-going pulses. One drum machine we tested, a Korg model, provided a +6V signal which went low on triggering. In this case the low level input must be used. (There is sufficient attenuation provided on this input to handle +6V.) This pulse duration was measured to be about 15ms and hence easily passed by the input ac coupling. The pulse is then inverted by the precision rectifier to give a positive going trigger signal. When using the signal input for this purpose the gain should be decreased to unity.

Finally, the DELAY mode — keeping in mind the limited specifications, the delay is still good enough for most purposes. It is activated by switching to RECORD, EXTERNAL and DELAY ON. The frequency pot now controls the delay length, from 88ms to 3.4 seconds. It is in this mode that the MIX control is needed to enable the original signal to be louder than the delayed version. With REGEN set to zero, one echo should be produced. Increased regeneration increases the number of repeats, until infinite regeneration, and finally feedback swamping is reached. With very short delay and a bit of regeneration the sound produced should be similar to the reverberative ringing of your favourite small room. Formally, reverberation is a mixture of the signal passing through many different delays (analogous to the sound taking longer to bounce off the roof than the walls of a room). Although the sampler has only one delay, the sound produced is quite similar to

the desired effect, giving 'psuedo reverberation'.

Important notes

Since the recording of the sample is what this whole project is about we will take time to discuss some of the things to keep in mind when actually sampling. As is true with most recording techniques it may take a number of attempts before the wanted sound or effect is obtained.

We mentioned before that sometimes a click may be heard at the end of the sample. This is the result of the particular sample and will not always occur. In sampling jargon this click is called a glitch. It can be best explained by looking at the diagram in Figure 1. This shows two different samples being taken of the same input signal. The first recording is the worst case example of a large glitch. This happens when the last sample that is taken is furthest away from the system rest voltage (the system rest voltage is the idle or non-operative voltage output of the DAC). This glitch is heard as a click if it is large. The loudness of the click varies depending on how close to the system rest voltage the final sample is. The best case condition is shown in recording 2. The last sample here is exactly the rest voltage and hence no click will be heard at all.

In some of the more sophisticated sampling devices there is the opportunity to define the start and end points of a particular sample on playback. This means that a glitch can be removed by backing up the end point to the first sample that is very close to the rest voltage. But alas, we do not have this facility. We can get around it though, by simply recording the same sound until the glitch is too small to be heard. This is usually not much of a problem since the sounds are mostly easily repeatable.

Another interesting recording technique that can be used is to alias the sample on purpose. This means that the recording is made with the frequency control between 0 and 50%. The sound is recorded as normal but when replayed it is a very warped (but still intelligible) replica of the original. This can give some strange synthesised sounds that can be quite useful, ranging from daleks to chipmonks. After the recording, try turning the frequency up on playback — it's even stranger.


But most of the time aliasing is not wanted. Keep the frequency control above 60% and the input filter will do the rest.


Sometimes a very distorted or noisy sample is obtained. This may be the result of either the gain being too low and hence not using the full dynamic range of the ADC or gain is too high and the input is clipping. In either case a little experimentation is called for in trying different gain settings until the correct one for your input signal is found. Once it is found, however, it will probably

not be changed until you use a new sound source.

It is also very important to keep in mind the way in which the sampling will be started or triggered. Totally different effects can be obtained using different triggering methods. For instance, say we wish to record someone saying 'hello', we can use external triggering with a low threshold setting and get 'hello' or with a higher threshold setting and get 'ello'. We could use internal triggering and get 'hello' or 'hel'. Each of these techniques gives a different sound so try them to get a few ideas.

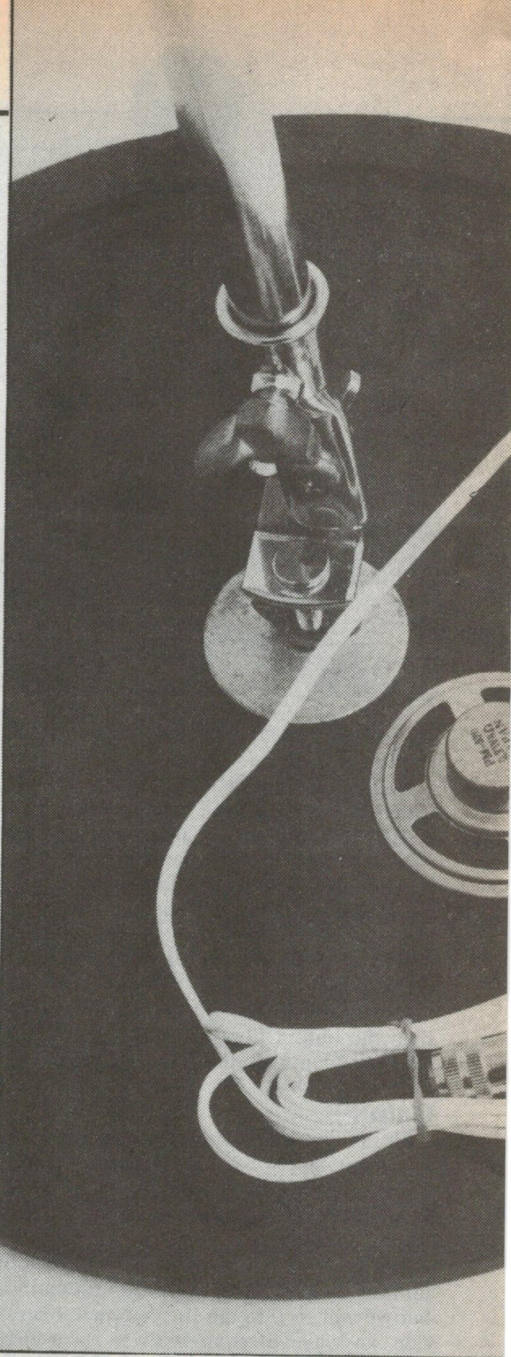When playing back a sample there are a number of sources that can lead to retriggering the sound when it is not needed. Firstly, if a microphone is connected to the input, acoustic feedback from the speakers may have enough level to retrigger. This can be fixed by turning the gain down or setting the trigger threshold high.



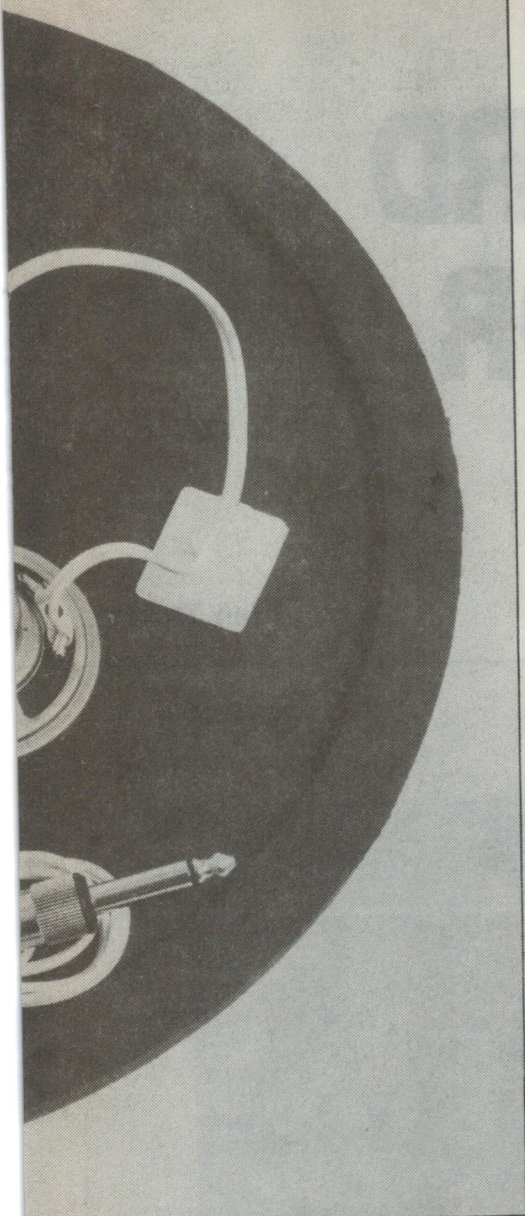

Secondly, if the regeneration control is not set to zero the sampled signal may re-trigger itself. This can be very useful in some circumstances to get a sound retriggering at regular intervals but can be very annoying if not wanted.

So there it is, a complete audio sampling system. It has numerous practical applications in the music industry and can provide hours of fun for friends and family. All the techniques and theory discussed can be applied to digital acquisition systems in general and it is in no way limited to audio sampling.

Sampling is only going to get more and more entrenched in modern day recording so understanding the fundamentals will go a long way. In the future with semiconductor memory prices falling and microprocessor-controlled sampling, flexibility will increase and 'real life' sounds of sampling will be heard coming from the strangest places. ●

MINIMART

FOR SALE: EIGHT 256K PARALLEL Printer buffer short form kit \$39, serial converter board to suit \$18, printer shaver board to suit \$12. For more info send SAE to Don McKenzie, 29 Ellesmere Cres, Tullamarine 3043.

FOR SALE: IBM PC type printer cables, DB-25-to-Centronics 36-way, 2 metres long, \$25 plus \$3 p&p. Don McKenzie, 29 Ellesmere Cres, Tullamarine 3043.

FOR SALE: OSBORNE O1 CP/M portable computer with 2 single-density single-sided drives; Fax-80 printer (Epson clone), 80 characters per second; Zenith amber monitor; software, documentation, and manuals included; \$1500 (whole lot). Joanne Ellis, Block C, Flat 2, Hayman Is, Qld 4801. (079) 46-9100 ext 693.

FOR SALE: CO-1686 CO-PROCESSOR. Runs MS-DOS on a CP/M RAM-DISK driver, & Z80 source code. \$570 ono. (07) 359-1740 ah, (07) 221-1124 bh.

FOR SALE: VZ200 SOFTWARE: 25 exciting games on one cassette for the incredible price of \$20 (inc p&p). Send cheque or money order to Lee Tait, PO Box 13, Auburn, SA 5451 for prompt delivery.

FOR SALE: GOODMAN SPEAKERS, Triaxiom 212C, beautiful sound, large enclosures, \$280 pair. Also Audiom 61, Audiom 70, Axiom 201, Triaxiom 212C and Axiom 150 MkII from \$20 each. (02) 869-1840.

WANTED: EARLY BOOKS, magazines and literature on wireless, radio, electronics, hi-fi and test equipment. Also early wireless sets and hi-fi equipment. Cash buyer. (02) 869-1840.

PC Assembly and Manufacturing Service

As an economical alternative to in house production.

- Latest Computerised Assembly and Soldering Equipment
- Competitive Prices
- Fast Turnaround

for further information contact.

**DUET
ELECTRONICS**
414 St. Georges Rd
Thornbury 3071
480-5803 484-4420

ETI READER SERVICE 175

TECHNICAL OFFICER — SENIOR

(REF. 252)

THE UNIVERSITY OF NEW SOUTH WALES

An experienced person is required to take charge of the design activities of the electronics workshop. Considerable experience in the design and construction of state-of-the-art electronic circuitry and a good knowledge of the current commercial availability of components and modules is required. The appointee will work in a stimulating environment and will be responsible for the planning and execution of the specialized instrumentation required by various research projects throughout the School.

Applicants must hold an appropriate Technical College certificate or have completed the equivalent of one full-time year of a relevant degree or diploma course.

Further information from

Mrs P. Shaw
(02) 697-4589

SALARY:
Up to \$28,673

*Please submit written
application to the*


**General Staff Office,
P.O. Box 1,
Kensington, N.S.W. 2033
by June 13, 1986**

*Equality of employment is
University policy.*

ESD HAZARD DETECTOR

Electric shock therapy is about the last thing you want for your vulnerable semiconductor components. But electrostatic discharge can be as hazardous as any pair of probes in a cuckoo's nest. This device gives warning of any moving electrostatic field which might zap your precious parts.

Ian Thomas

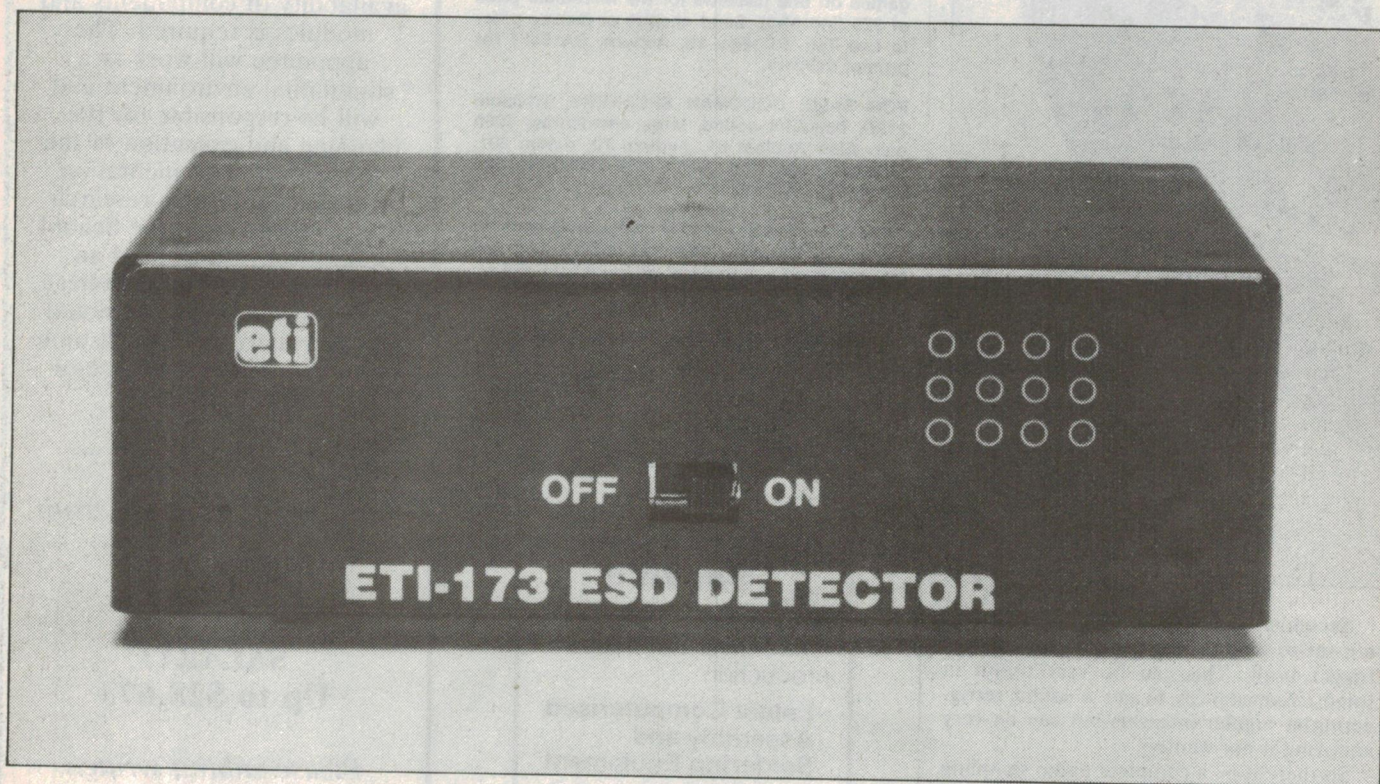

TO THOSE LESS aware than most, this title might appear to be about a device to detect some of the more brain disrupting chemicals that are currently around. However it isn't brains that this device protects, it's silicon.

Everyone's aware that on a cold dry winter's day you tend to build up an electrostatic charge on your body so that when you touch some metal object such as a tap or door knob you cop a most unpleasant ZAP! This zap is called an electrostatic discharge and if it happens to jump on to a lead of an IC or transistor then the poor device is

never quite the same again. In the last few years it has become more and more commonly recognised that semiconductor devices are extremely sensitive to these stray high voltage transients, and MOS devices more than most. From a manufacturing point of view it isn't so much the outright broken bits that matter (they can be found during test) but the bits that are somewhat bent. They appear to work but will go toes-up after the equipment has been in use for a few days or weeks.

IC manufacturers are aware of this problem and go to great pains to build protection

into the devices where pins are connected out. There is, however, a limit to what you can do without degrading the device performance. In general the distributors are pretty good and try to do the right thing; but you, dear reader, may not.

An electrostatic charge is generated when two insulating dissimilar materials are rubbed together or even touched together then pulled apart. The degree of dissimilarity and the amount of charge generated is a function of the position of the two materials in an order known as the Triboelectric Series, part of which is given in Table 1. It is

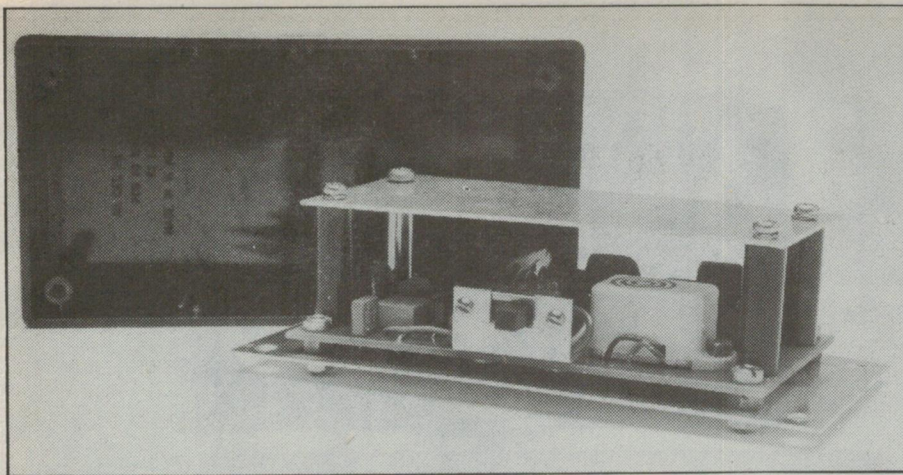


Table 1. THE TRIBOELECTRIC SERIES

Air	}	POSITIVE
Human skin		
Glass		
Human hair		
Wool		
Fur		
Paper	}	NEGATIVE
Cotton		
Wood		
Hard rubber		
Acetate rayon		
Polyester		
Polyurethane		
PVC (vinyl)		
Teflon		

also a function of the humidity of the air, intimacy of contact of the two materials and the rate of separation and is in general a pretty inexact sort of thing but there are clear trends. You can see from the table that cotton is pretty much neutral (and hence cotton shirts don't charge up and zap you). In general it's the materials that tend to reject moisture that create the worst charge problems as moisture tends to conduct and bleed charge away.

To give you an idea of the sorts of potentials that can be built up, Table 2 shows the effect of various actions on a dry day and a relatively humid one. It's easy to see why you can get a belt by walking across a carpet on a cold winter's day! A normal human body insulated by your average sort of running shoes has a self capacitance in the order of 100pF. A few quick prods at a calculator shows that the stored energy in your delicate body is about 60 millijoules. The energy per discharge in the ETI-342 Pulse Shaped CDI (Feb '85) was only 120 millijoules which explains why it hurts when you touch something. Obviously a piece of silicon, the dimensions of which are measured in micrometres, is blown to a thin haze!

In general MOS devices tend to be the most delicate as a fundamental part of their structure is a very thin layer of silicon dioxide which can be absolutely guaranteed to rupture at the order of a 100 volts or so. For this reason even power MOSFETs that can cope with tens of amps at hundreds of volts can be ruined by one little zap on the gate lead. This certainly doesn't mean that you can do what you want with bipolar devices. If sufficient energy is dumped into the input junction then the device will fail.

In industrial situations where it's absolutely essential that these terrible things don't happen, quite exotic precautions are taken. The top of the bench being worked on is covered with conductive material (usually a type of conductive rubber) which is grounded. The workers wear conductive wrist straps which are grounded (through a large resistor). Ionised air (which is slightly conductive) may be blown over the work area. On top of all this there is a whole bunch of specifications and procedures to cover all phases of assembly. About this

Table 2. TYPICAL ELECTROSTATIC VOLTAGES

Means of generation	Humidity	
	10-20%	60-90%
Walking across carpet	35,000	1500
Walking on vinyl floor	12,000	250
Worker at bench	6,000	100
Vinyl envelopes as per work instructions	7,000	600
Common poly bag picked up from bench	20,000	1200
Work chair padded with polyurethane foam	18,000	1500

stage you're probably thinking it's a miracle anything ever worked and you might as well give it all away. But ETI has a simple, precautionary device that should help.

Design

Whenever a body is charged up to a high potential then it is surrounded by an electrostatic field normally expressed in volts/metre, and if the body moves then the field moves with it. If you've just been dancing on your lovely new nylon carpet and charged yourself up to 10 zillion volts then the field from that charge spreads out from your body quite a long way.

It seemed to me that an instrument that detected the approach of this field and sounded an alarm would go a long way to avoiding blasted silicon. At least you would be warned to discharge yourself. It's extremely difficult (read expensive) to detect a completely static electrostatic field but a moving one is not such a great problem. A simple thought experiment will explain the problem and show how a detector could be built.

Suppose we have two parallel plates of a capacitor magically suspended in space 25mm apart and with an area of about 5000mm², a not inconvenient size for a detector. The capacitance between its plates works out to be very roughly 2pF. Suppose a field of 500 volts/metre is suddenly imposed across these capacitor plates (definitely ESD hazard conditions!). The potential between the plates will immediately rise to 12.5 volts (500 volts/metre times 2.5/100 metres). The problem is that any attempt to measure the voltage (cheaply) will immediately bleed the charge away. Even a 10 megohm resistor gives a time constant of only 20 microseconds.

This transient could possibly be detected except for another major problem. The whole world is filled with (it would seem) literally thousands of volts/metre of 50Hz mains hum and if a detector was built with a bandwidth sufficient to detect the spikes then it would be continually set off by mains. This means that the detector needed to operate on our parallel plate capacitor must have a filter that cuts off fast before 50Hz to keep mains out. If the detector doesn't respond to frequencies above 50Hz then the input RC time constant needs to be very long, about a second! Hence the problem in building such a device. It must have an incredibly high input impedance or alternatively huge capacitor plates to up the sensing capacitance. With 2pF input capacitance this gives a detector input resistance of 500 gigohms! Even though the input impedance of some MOS input op-amps approaches this figure, it isn't a lot of use as an actual resistor is needed to define reference voltages. As 500 gigohm resistors are just a little hard to buy this basic approach won't work.

It then occurred to me that we were trying to detect voltages in the order of tens of volts. This combined with the fact that these days gain is cheap gave me the clue. If one plate of the sensor capacitor plates was connected to the other through say a 5000pF capacitor then the input tens of volts would be attenuated to fours of millivolts, but then the detector capacitor forms a potential divider with the 5000pF and increases the size of the source capacitance. In this case the needed detector input resistance drops to around 100 megohms to be usable. This is still a bit gross but getting closer. From an engineering point of view ►

Project 173


you can get 100 megohm resistors but they are expensive and hard to procure. About the largest I could find at Geoff Woods' was 10M. He had 22 megs but I settled for 10M for reasons I'll go into later.

The next problem is how one can magically change a 10 meg resistor into a 100 meg resistor. The method goes by the delightful term "bootstrapping". Consider a resistor with a voltage applied to one end as shown in Figure 1. The current through the resistor due to the imposed voltage is I . If a buffer amplifier with a very high input impedance is connected to the top of the resistor with a gain of say 0.9 and its output is connected to the earth end of the resistor then the voltage drop across the resistor is no longer V as in Figure 1 but $V-0.9V$ or only $0.1V$. This means that even though the full V volts is being imposed on the resistor, the current flowing into it is only $0.1I$ so the effective resistance is multiplied by 10. This would seem to be a pretty good trick to use. It does have bad side effects like multiplying all offset problems by 10 but if these can be managed then a 10 meg resistor can be changed into a 100 meg resistor.

Given the ability to artificially create a very high input impedance amplifier, the idea of a detector of changing strong electrostatic fields seemed to be quite workable. It should be in a small box to one side of the work area and preferably run off batteries. As the detector does not need a large bandwidth (in the final device there is a lot of circuitry to reduce it) a very low power op-amp such as the National LM4250 can be used. The power drawn by this IC can be set to almost any value required by an external resistor. The op-amp bandwidth varies accordingly but even at microamp levels has more than enough. The LM4250 is specified down to 3 volts total supply voltage so the detector could be powered off two penlight cells. If the total IC power drain is kept below a few microamps then the life of the cells in the detector is effectively their shelf life.

Circuit details

The actual filter used to attenuate the 50Hz is straightforward and 10M resistors were used throughout. As there is effectively 30 megohms between the positive input and ground it is necessary to add in about 30 megohms between the negative input and the output to balance the effect of bias currents in the op-amp. For the LM4250 operating at a few microamps the offset current (that is the difference in bias currents of the op-amp inputs) is still up to 5 nanoamps. With 30 megohms this generates a differential offset voltage at the input in the worst case of 150 millivolts. This could be adjusted out with an offset adjust pot but the problem is further aggravated by the bootstrapping with R7 and R8. C7 had to be

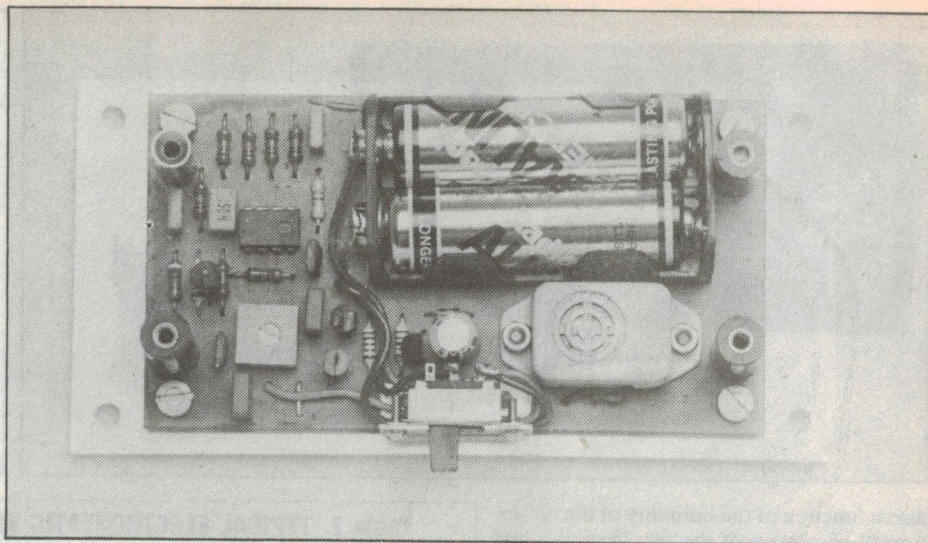

added to remove both the bootstrapping and the high gain for very low frequencies or the input simply floated all over the place.

However, for frequencies between 0.5Hz and 15Hz the detector gain is pretty much flat and set by the ratio of R10 to R7+R8. When I slogged through the algebra to calculate the transfer polynomial for the circuit, one very interesting fact emerged: the gain of the detector is proportional to the size of C8. You will recall that the input to the detector is actually a capacitive divider made up of the detector plates and C8 so the larger C8 is the higher the input capacitive divider attenuation *but then so is the amplifier gain!* They cancel out. Most serendipitous! Once again, there are always limits like offset problems that don't show up in the mathematics but basically it's whatever is convenient in the filter for C8.

Transistors Q1 and Q2 act to turn on the Darlington transistor Q3 when the op-amp output exceeds one V_{be} . I wanted a nice loud alarm when there was a hazard situation so I used one of the small 3 volt self contained alarms. They're nothing if not loud. A quick estimate of the board area needed showed it would fit nicely into a plastic jiffy box 130mm x 70mm x 40mm with a metal bottom. The metal case bottom serves as one plate of the sensing capacitor so plastic cases aren't any good.

Construction

Everything is mounted on the pc board including the batteries. You can copy the artwork provided or purchase transparencies from ETI, or do it the easy way and buy from the kit suppliers. However you do it, try to stick exactly to the layout given.

Mounted over the board on 25.4mm spacers is the second plate of the sensing capacitor. Three of the spacers are made of insulating material and the fourth is metal and carries the received voltage to the detector input. I even chose to put a tiny slide switch and the buzzer on the board (both of which I got from Tandy) just to make things complete. The switch is included in case a situa-

tion arises where high fields can't be avoided (say you're building a Van de Graaff generator and you don't want to have to throw it out the window).

Before the board components are assembled it's a smart idea to use it as a template to drill the holes for the base plate and the detector plate.

Hold the board *exactly* in the centre of the base plate for the four mounting holes. A dimensional drawing is given for the detector plate but it's a lot easier to simply hold the board and plate together and drill them (more accurate too!). *Note that the detector plate is offset if you wish to use the small slider switch mounted on the board.*

Make sure that the IC and the electrolytic capacitors are in the right way. The battery case I used was one which held four penlight cells. You can get battery holders that only take two cells but if you look at where the holder is mounted you'll see that it would be impossible to get one of the cells in. The four cell holders come in various brands, some with nickel plated steel contacts and some with aluminium. The aluminium ones aren't so good here as it's necessary to solder to the springs and you can't solder aluminium! It's difficult enough with the nickel.

Carefully cut away the side of the battery holder that doesn't have terminal clips. This will leave you with a spring protruding which should be straightened out. On the piece of holder that was cut away there is a second spring still riveted to the plastic. Drill, bash or bend the rivet out and retrieve the spring. Straighten out the end of the spring that was riveted so it can be inserted in a hole in the printed circuit board. Mix up some Araldite or similar and glue down the battery holder then insert the straightened out spring so as to make a neat two cell battery holder as pictured.

The next and nastiest bit is to solder the nickel plated springs on to the large ground area of the printed board. Nickel is a beast of a material to solder and I must confess I weakened and used el corodo Bakers soldering flux but it has to be washed off com-

ETI-173 — PARTS LIST

Resistors.....all 1/4W, 2% metal film

R1, 2, 3, 4, 5 10 megohm
 R6 4M7
 R7, 12 1k0
 R8 9k1
 R10, 9 2M2
 R11 100k
 RV1 100k trimpot

Capacitors

C1, 2 100n 10% met poly*
 C3, 4 1n 10% met poly*
 C5 150p 10% met poly*
 C6 6n8 10% met poly*
 C7 100µ 10% 3V tag tantalum
 C8 47µ Al electro
 C9 4n7

Semiconductors


IC1 LM4250
 D1 1N914
 Q1, 2 BC559
 Q3 Motorola MPS-A14

Miscellaneous


ETI-173 pc board; 2 x AA batteries; battery holder; Piezo buzzer; slide switch; 3 x 25.4mm insulated spacers; 1 x 25.4mm metal spacer; hookup wire; 130mm x 70mm x 40mm jiffy box with metal bottom; 5cm x 100cm metal plate; 4 x 4BA 3/8" screws and nuts; Scotchcal front panel.

Price estimate: \$25

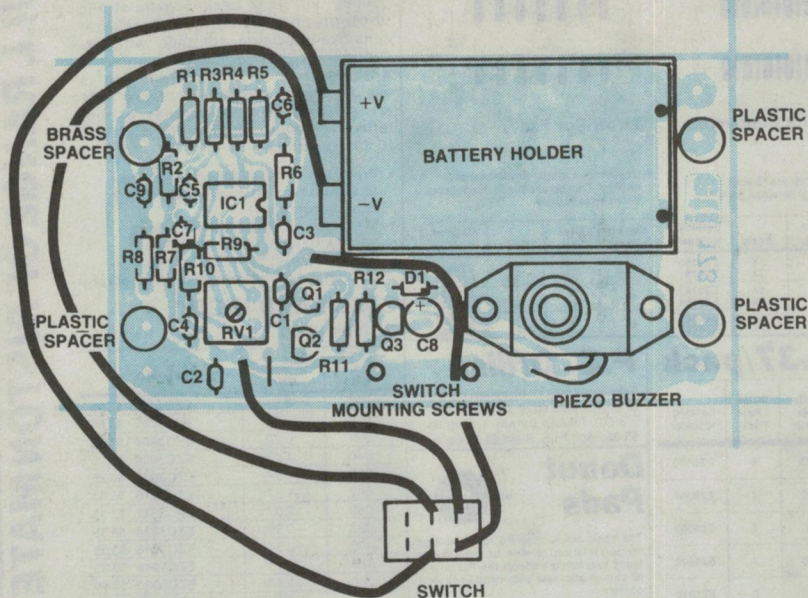*The prototype used metallised polyester film caps such as ERO MKT1817 or MKT1826, or Wima PR21 or PS21 but greencaps could be substituted.



DETECTOR PLATE

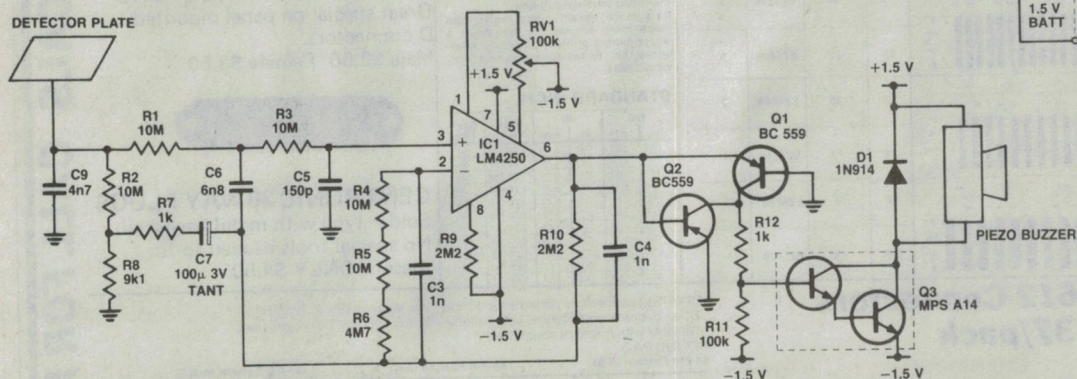

ETI-173 — HOW IT WORKS

The alarm detects electrostatic fields by sensing the potential difference they generate on a parallel plate capacitor. One plate is the base plate of the case and the other is a plate held by spacers above the detector.

Resistors R1 and R3 form a low pass filter with C5 and C6 to attenuate mains hum. Further attenuation is provided by C4 which rolls off the operational amplifier IC1's response. R7 and R8 serve two purposes. The first is to act as a gain determining element which, together with R10 sets the gain of

the op-amp at 220. Also the node of R7 and R8 has a voltage of 0.9 times the voltage on the positive input of the amplifier (and the negative input too — such is the nature of operational amplifiers). R2, the input bias setting resistor, is connected to this node so that any signals that appear at the input to the detector are also imposed, multiplied by 0.9, on the other end of R2. This is known as bootstrapping and effectively multiplies the value of R2 by 10.

The overall effect of this is that any voltage that would be induced on a capacitor


with plates about 20mm apart appears with a low source impedance at the output of the op-amp, attenuated 10 times when everything is taken into account.

Transistor Q1 is turned on if the op-amp output goes more than 0.6 volts positive and Q2 is turned on if it goes negative. Both collectors drive the base of the Darlington transistor Q3 which in turn powers the alarm. Thus excursions of ± 0.6 volts set off the alarm or, tracing back through the circuit, the detector will pick up fields of greater than 300 volts/metre.

EVERYTHING YOU NEED TO MAKE PRINTED CIRCUITS

NOW STOCKING COMPLETE RANGE OF E-Z CIRCUIT DRAFTING AIDS

Dual in Line Packages All \$4.37/pack

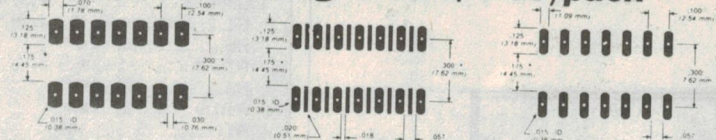

Cut Pad

No. of Leads	Qty/ Pkg.	Scale	Catalog Number
14	32	1X	EZ6014
16	32	2X	EZ6038
18	28	2X	EZ6004
24	12	1X	EZ6535
28	12	2X	EZ6536
40	8	1X	EZ6900
	8	2X	EZ6901

Cut Pad With Conductors

No. of Leads	Qty/ Pkg.	Scale	Catalog Number
14	32	1X	EZ6760
16	32	2X	EZ6761
18	28	2X	EZ6763
24	12	1X	EZ6764
28	12	2X	EZ6984
40	8	1X	EZ6985
	8	2X	EZ6986

Narrow Cut Pad

No. of Leads	Qty/ Pkg.	Scale	Catalog Number
14	32	1X	EZ6017
16	32	2X	EZ6031
18	28	2X	EZ6453
24	12	1X	EZ6454
28	12	2X	EZ6987
40	8	2X	EZ6988


Pre-Spaced Pads \$4.37/pack

Center to Center Spacing	Pad Type	Scale	Pads Per Strip	Strips Per Pack	Catalog Number
.100"	1X	1X	40	6	EZ5000
	2X	2X	20	7	EZ5001
	1X	1X	40	6	EZ5003
	2X	2X	20	7	EZ5004
.125"	1X	1X	40	6	EZ5017
	2X	2X	20	7	EZ5018
	1X	1X	40	6	EZ5020
	2X	2X	20	7	EZ5021
.156"	1X	1X	25	6	EZ5014
	2X	2X	13	7	EZ5015

Edge Connectors \$4.37/pack

Center to Center Spacing	Scale	Contacts/ Strip	Catalog Number	Strips/ Pack
.100"	1X	44	EZ6805	2
	2X	22	EZ6809	5
.125"	1X	35	EZ6704	2
	2X	17	EZ6716	4
.156"	1X	28	EZ6708	3
	2X	14	EZ6720	5

DIN41612 Connectors All \$4.37/pack

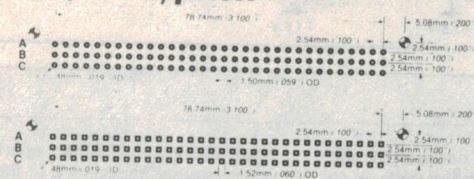

DIN41612 connectors patterns have three row designations A, B and C. Three pattern combinations are available AB, AC and ABC. They are also available with round or square pads.

ROUND PAD

64-Pin Pattern (A-B)

Scale	Symbols Per Pkg.	Catalog Number
1X	2	EZ6869
2X	2	EZ6870

64-Pin Pattern (A-C)

Scale	Symbols Per Pkg.	Catalog Number
1X	2	EZ6875
2X	2	EZ6876

96-Pin Pattern (A-B-C)

Scale	Symbols Per Pkg.	Catalog Number
1X	2	EZ6871
2X	2	EZ6872

SQUARE PAD

64-Pin Pattern (A-B)

Scale	Symbols Per Pkg.	Catalog Number
1X	2	EZ6878
2X	2	EZ6879

64-Pin Pattern (A-C)

Scale	Symbols Per Pkg.	Catalog Number
1X	2	EZ6881
2X	2	EZ6882

96-Pin Pattern (A-B-C)

Scale	Symbols Per Pkg.	Catalog Number
1X	2	EZ6884
2X	2	EZ6885

Precision Slit Tapes

"Super" 201 is a flexible extra-strong photographically opaque, pressure-sensitive precision slit tape with exceptional adhesive characteristics. It will not creep or lift if stretching is avoided during application. "Super" 201 is extremely flexible and has a non-reflective matte finish. Only .005" (0.13 mm) thick.

- Precision slit to exacting tolerances to assure highest quality PC artwork and photography
- Manufactured from the same high quality materials as E-Z CIRCUIT PREKUT TAPE SHAPES to insure compatible PC artwork and photography

STANDARD INCH

20 Yds./Roll

Tape Size	Cat. No.
.020	EZC3000 \$3.05
.026	EZC3002 \$3.05
.031	EZC3004 \$3.25
.040	EZC3006 \$3.25
.050	EZC3008 \$3.25
.062	EZC3010 \$3.35
.080	EZC3012 \$3.35
.093	EZC3014 \$3.35
.100	EZC3016 \$3.35
.125	EZC3018 \$3.35
.200	EZC3020 \$3.46
.250	EZC3022 \$4.57
.500	EZC3024 \$5.70

Accurate Grids

Grids are produced on accurate stable film with 0.1" pattern for maximum accuracy. Matte one sided. .003" thick.

Sheet Size	Catalog Number
8" x 11"	EZ1463 \$2.63
11" x 17"	EZ1466 \$4.87

CONNECTOR SPECIALS

25 WAY 'D' CONNECTORS

Great special on panel mounted D connectors.

Male \$2.50 Female \$3.50



CENTRONIC 36 WAY PLUGS

Solder type with metal backshell.


No special tools needed to fit these!! ONLY \$4.50

8.30 to 5 Monday to Friday, 8.30 to 12 Sat.
Mail Orders add \$3.00 to cover postal charges.
Next day delivery in Sydney add \$5.00.

All prices INCLUDE sales tax.
Tax exemption certificates accepted if line value exceeds \$10.00.

BANKCARD, MASTERCARD, VISA, CHEQUES

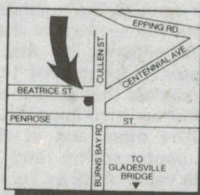specialising in electronic components for the professional and hobbyist.



GEOFF WOOD ELECTRONICS P/L (02) 427 1676

INC IN NSW

229 BURNS BAY RD.
(CORNER BEATRICE ST.)
LANE COVE WEST N.S.W.

TWX 71996
P.O. BOX 671
LANE COVE N.S.W. 2066

OR CASH CHEERFULLY ACCEPTED

pletely. The buzzer is screwed down and both its leads soldered into the relevant pads. Be careful as the polarity must be right. Finally the board must be cleaned absolutely scrupulously of all fluk and residue. There are a lot of high impedances and leakage could be a nuisance.

You need three insulating spacers and one metal one to support the pickup plate. The metal one connects to the pad that has C8, R1 and R2 connected to it. If you choose to use the little slide switch you'll find it necessary to trim one side of the pickup plate so the electronics can be assembled into the box. If you use another type remember that both the positive and negative supplies must be switched. I didn't bother with the clip leads for the battery holder but simply soldered pieces of hookup

wire on to the terminals as they will never be disconnected.


The board assembly is mounted on the base plate of the box with four 4BA 3/8 screws. The screws are passed through the board and one nut done up tight on each screw, then the protruding ends of the screws are passed through the four holes in the base plate and another four nuts done up to hold the board neatly in place.

Testing

Testing is really quite easy. Insert two batteries and turn it on. The alarm should sound for about 20 seconds or so as C7 charges to the offset voltage then it shuts off. Let it settle for a few minutes then measure the voltage between pin 6 of the IC and ground. Adjust RV1 until it averages out to

zero. This is a fiddly and odious task as you only have to (literally!) wave your hand near the detector input and pin 6 slams up against the rails. Fortunately, it isn't all that critical. Once this is done, screw on the detector plate and the unit is ready to go into the box.

Finally before fitting the unit together you'll have to cut a hole for the power switch. It makes sense to drill a few holes to let the buzzer sound out. Slip the unit into the box and screw it in place with the four screws provided then turn it on. If you keep well away from it, it should sound for 10 seconds or so then go quiet. Just waving your hand close over it or touching the box will set it off. Then you may leave it on in a corner of your workbench and breathe a bit easier! ●

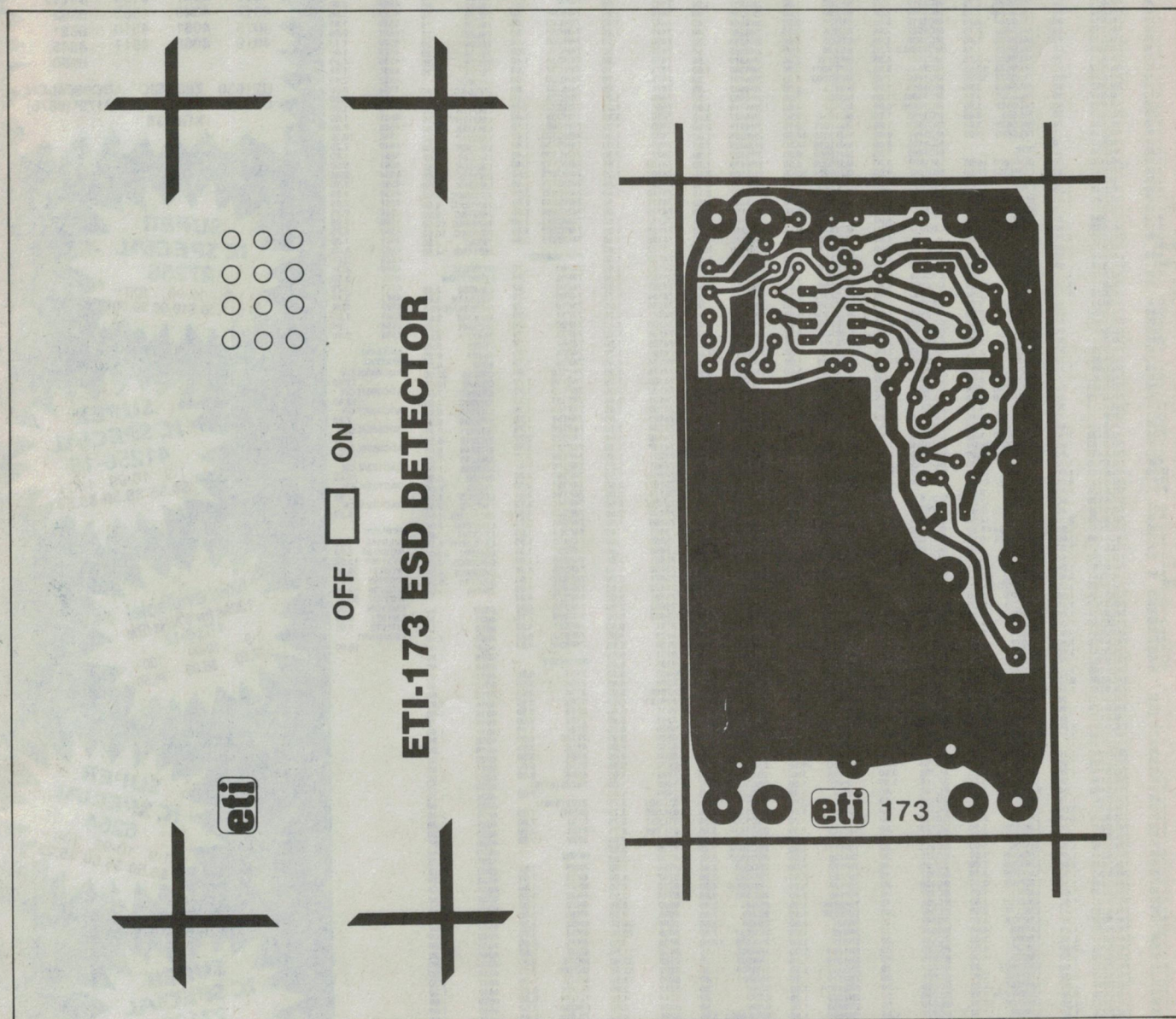

SUPER IC SPECIAL 2732

1-9 10-99 100+
\$6.25 \$5.95 \$5.50

SUPER IC SPECIAL AM 7910

WORLD MODEM CHIP
\$29.50

SUPER IC SPECIAL 4164

1-9 10-99 100+
\$2.95 \$2.75 \$2.50

SUPER IC SPECIAL 6116LP-3

1-9 10-99 100+
\$3.95 \$3.75 \$3.50

30% OFF THESE PRICES!

During June, we
are offering the
following semi's at
30% off our
normal prices!
...but be quick!!

4001	4020	4069	4516
4002	4023	4071	4518
4011	4025	4072	4520
4012	4026	4073	4526
4013	4030	4081	40105
4014	4020	4093	40175
4015	4043	4161	40014
4016	4047	4194	45112
4017	4049	4503	6802
4018	4051	4510	6821
4019	4066	4511	6845
			6850

U21630 Z80ASIO ADC0804LCN
U21720 F9001DC F1791(8876)
XR8038

SUPER IC SPECIAL 27256

1-9 10-99 100+
\$11.50 \$10.00 \$9.00

SUPER IC SPECIAL 41256-15

1-9 10-99 100+
\$6.95 \$6.50 \$5.50

Now available!
120ns for 8 MHz IBM
41256-12

SUPER IC SPECIAL 6264

1-9 10-99 100+
\$6.50 \$5.50 \$5.25

SUPER IC SPECIAL 27128

1-9 10-99 100+
\$7.00 \$6.50 \$6.25

THESE PRICES!

During June, we are offering the following semi's at 30% off our normal prices! ...but be quick!...

4001 4020 4069 4516
4002 4023 4071 4518
4011 4025 4072 4520
4012 4026 4073 4526
4013 4030 4081 40105
4014 4020 4093 40175
4015 4043 4161 40014
4016 4047 4194 45112
4017 4049 4503 6802
4018 4051 4510 6821
4019 4066 4511 6845
6850

U21630 Z80ASIO ADC0804LCN
U21720 F9001DC FD1791(8876)
XR0838

SUPER IC SPECIAL 27256
1-9 10-99 100+
\$11.50 \$10.00 \$9.00

SUPER IC SPECIAL 41256-15
1-9 10-99 100+
\$6.95 \$6.50 \$5.50

Now available!
120ns for 8 MHz IBM
41256-12
1-9 10-99 100+
\$7.50 \$6.95 \$6.50

SUPER IC SPECIAL 6264
1-9 10-99 100+
\$6.50 \$5.50 \$5.25

SUPER IC SPECIAL 27128
1-9 10-99 100+
\$7.00 \$6.50 \$6.25


ICL7106 19.50	74C374 4.45	74LS324 2.20	LM377 4.90	BD238 90	2N3055 1.00	6AMP	8271 89.00	HLM6620 3.95	4056 4.20
ICL7115 18.50	74C390 3.00	74LS326 2.20	LM378 3.90	BD262 1.20	2N3096 1.20	BPC602 2.90	8272 33.00	LEDS	4060 2.50
ICL7117 21.50	74C392 2.00	74LS327 2.20	LM380 8 pin	BD263 1.20	2N3109 1.90	BPC604 3.50	8273 65.00	3mm RED 25	4062 2.50
ICL7611 6.95	74C393 2.50	74LS332 2.20	LM380 14 pin	BD488 1.50	2N3302 1.90	BPC606 4.50	8274 42.50	3mm YELL 30	4066 2.50
ICL7660 5.90	74C394 2.50	74LS333 2.20	LM381 1.90	BD489 1.50	2N3302 1.90	BPC1002 4.20	8275 38.50	3mm GRN 30	4067 9.90
ICM7211 12.50	74C395 15.00	74LS334 3.95	LM381 3.50	BD489 1.50	2N3440 1.80	BPC1004 4.20	8276 28.50	5mm YEL 30	4068 1.00
ICM7216A 48.50	74C396 2.90	74LS336 1.00	LM382 3.50	BD667 1.80	2N3442 3.50	35AMP	8278 8.50	5mm YELL 30	4069 1.00
ICM7216B 44.50	74C397 2.75	74LS367 6.00	LM383 3.50	BD667 1.80	2N3563 3.00	BPC3502 5.90	8282 6.90	5mm GRN 30	4070 9.90
ICM7224A 21.50	74C398 1.00	74LS373 1.90	LM383 3.50	BD667 1.80	2N3563 3.00	BPC3504 5.90	8283 6.50	RED RECT 30	4072 9.90
ICM7224B 48.50	74C399 2.90	74LS374 1.90	LM387A 3.95	BD667 1.80	2N3566 3.00	BPC3510 MDA	8284 8.50	GRN RECT 30	4073 9.90
ICM7227A 19.95	74C401 4.50	74LS375 1.00	LM387A 3.95	BD667 1.80	2N3566 3.00	3510 9.90	8287 6.50	RED CHROME	4076 1.50
	74C402 12.50	74LS377 2.15	LM390 2.95	BD667 1.80	2N3566 3.00		8289 73.00	BEZEL 1.20	4077 8.00
	74C421 12.50	74LS378 1.00	LM391 2.95	BD667 1.80	2N3566 3.00		8291 57.50	YELLOW	4078 8.00
	74C422 12.50	74LS379 1.00	LM395 9.95	BD667 1.80	2N3566 3.00		8292 57.50	CHME BEZEL	4081 8.00
	74C423 12.50	74LS380 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8293 57.50	GRN CHRM	4085 2.20
	74C424 12.50	74LS381 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8294 57.50	BEZEL 1.20	4086 2.20
	74C425 12.50	74LS382 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8295 57.50		4093 3.35
	74C426 12.50	74LS383 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8296 57.50		4094 3.35
	74C427 12.50	74LS384 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8297 57.50		4095 2.40
	74C428 12.50	74LS385 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8298 57.50		4096 2.40
	74C429 12.50	74LS386 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8299 57.50		4097 2.40
	74C430 12.50	74LS387 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8300 57.50		4098 2.40
	74C431 12.50	74LS388 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8301 57.50		4099 2.40
	74C432 12.50	74LS389 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8302 57.50		4100 2.40
	74C433 12.50	74LS390 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8303 57.50		4101 2.40
	74C434 12.50	74LS391 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8304 57.50		4102 2.40
	74C435 12.50	74LS392 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8305 57.50		4103 2.40
	74C436 12.50	74LS393 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8306 57.50		4104 2.40
	74C437 12.50	74LS394 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8307 57.50		4105 2.40
	74C438 12.50	74LS395 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8308 57.50		4106 2.40
	74C439 12.50	74LS396 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8309 57.50		4107 2.40
	74C440 12.50	74LS397 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8310 57.50		4108 2.40
	74C441 12.50	74LS398 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8311 57.50		4109 2.40
	74C442 12.50	74LS399 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8312 57.50		4110 2.40
	74C443 12.50	74LS400 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8313 57.50		4111 2.40
	74C444 12.50	74LS401 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8314 57.50		4112 2.40
	74C445 12.50	74LS402 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8315 57.50		4113 2.40
	74C446 12.50	74LS403 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8316 57.50		4114 2.40
	74C447 12.50	74LS404 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8317 57.50		4115 2.40
	74C448 12.50	74LS405 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8318 57.50		4116 2.40
	74C449 12.50	74LS406 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8319 57.50		4117 2.40
	74C450 12.50	74LS407 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8320 57.50		4118 2.40
	74C451 12.50	74LS408 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8321 57.50		4119 2.40
	74C452 12.50	74LS409 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8322 57.50		4120 2.40
	74C453 12.50	74LS410 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8323 57.50		4121 2.40
	74C454 12.50	74LS411 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8324 57.50		4122 2.40
	74C455 12.50	74LS412 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8325 57.50		4123 2.40
	74C456 12.50	74LS413 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8326 57.50		4124 2.40
	74C457 12.50	74LS414 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8327 57.50		4125 2.40
	74C458 12.50	74LS415 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8328 57.50		4126 2.40
	74C459 12.50	74LS416 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8329 57.50		4127 2.40
	74C460 12.50	74LS417 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8330 57.50		4128 2.40
	74C461 12.50	74LS418 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8331 57.50		4129 2.40
	74C462 12.50	74LS419 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8332 57.50		4130 2.40
	74C463 12.50	74LS420 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8333 57.50		4131 2.40
	74C464 12.50	74LS421 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8334 57.50		4132 2.40
	74C465 12.50	74LS422 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8335 57.50		4133 2.40
	74C466 12.50	74LS423 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8336 57.50		4134 2.40
	74C467 12.50	74LS424 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8337 57.50		4135 2.40
	74C468 12.50	74LS425 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8338 57.50		4136 2.40
	74C469 12.50	74LS426 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8339 57.50		4137 2.40
	74C470 12.50	74LS427 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8340 57.50		4138 2.40
	74C471 12.50	74LS428 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8341 57.50		4139 2.40
	74C472 12.50	74LS429 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8342 57.50		4140 2.40
	74C473 12.50	74LS430 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8343 57.50		4141 2.40
	74C474 12.50	74LS431 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8344 57.50		4142 2.40
	74C475 12.50	74LS432 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8345 57.50		4143 2.40
	74C476 12.50	74LS433 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8346 57.50		4144 2.40
	74C477 12.50	74LS434 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8347 57.50		4145 2.40
	74C478 12.50	74LS435 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8348 57.50		4146 2.40
	74C479 12.50	74LS436 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8349 57.50		4147 2.40
	74C480 12.50	74LS437 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8350 57.50		4148 2.40
	74C481 12.50	74LS438 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8351 57.50		4149 2.40
	74C482 12.50	74LS439 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8352 57.50		4150 2.40
	74C483 12.50	74LS440 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8353 57.50		4151 2.40
	74C484 12.50	74LS441 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8354 57.50		4152 2.40
	74C485 12.50	74LS442 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8355 57.50		4153 2.40
	74C486 12.50	74LS443 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8356 57.50		4154 2.40
	74C487 12.50	74LS444 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8357 57.50		4155 2.40
	74C488 12.50	74LS445 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8358 57.50		4156 2.40
	74C489 12.50	74LS446 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8359 57.50		4157 2.40
	74C490 12.50	74LS447 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		8360 57.50		4158 2.40
	74C491 12.50	74LS448 1.80	LM396K 22.50	BD667 1.80	2N3566 3.00		836		

SERIES 5000

INDIVIDUAL COMPONENTS TO MAKE UP A SUPERB HI-FI SYSTEM!

By directly importing and a more technically orientated organisation, ROD IRVING ELECTRONICS can bring you these products at lower prices than their competitors. Enjoy the many other advantages of RIE Series 5000 kits such as "Superb Finish" front panels at no extra cost, top quality components supplied throughout. Over 1,000 sold!

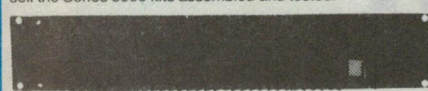For those who haven't the time and want a quality hi-fi, we also sell the Series 5000 kits assembled and tested.



POWER AMPLIFIER

WHY YOU SHOULD BUY A "ROD IRVING ELECTRONICS" SERIES 5000 POWER AMPLIFIER

• 1% Metal Film Resistors
Designed and developed by ROD IRVING ELECTRONICS and is being supplied to other kit suppliers.

SPECIFICATIONS: 150 W RMS into 4 ohms

POWER AMPLIFIER: 100W RMS into 8 ohms (+/- 55V Supply)

FREQUENCY RESPONSE: 8Hz to 20KHz +0/-0.4 dB 2.8KHz to 65KHz, +0/-3 dB. NOTE: These figures are determined solely by passive filters.

INPUT SENSITIVITY: 1 V RMS for 100W output.

HUM: 100 dB below full output (flat).

NOISE: 116 dB below full output (flat, 20KHz bandwidth).

2nd HARMONIC DISTORTION: -0.001% at 1 KHz (0.0007% on Prototypes) at 100W output using a +56V SUPPLY rated at 4A continues -0.0003% for all frequencies less than 10KHz and all powers below clipping.

TOTAL HARMONIC DISTORTION: Determined by 2nd Harmonic Distortion (see above).

INTERMODULATION DISTORTION: 0.003% at 100W, (50Hz and 7KHz mixed 4:1).

STABILITY: Unconditional.

Cat. K44771 \$359

Assembled and tested \$549

packing and post \$10



PREAMPLIFIER

THE ADVANTAGES OF BUYING A "ROD IRVING ELECTRONICS" PREAMPLIFIER

• 1% Metal Film Resistors
Designed and developed by ROD IRVING ELECTRONICS and is being supplied to other kit suppliers.

SPECIFICATIONS: High-level input: 15Hz = 130KHz, +0/-1 dB

Low-Level input: conforms to RIAA equalisation +0.2 dB


DISTORTION: 1KHz -0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation).

S/N NOISE: High-Level input, master full, with respect to 300mV input signal at full output (1.2V): 92dB flat -100dB A-weighted, MM input, master full, with respect to full output (1.2V) at 5mV input 50ohms source resistance connected: -86dB flat/92dB A-weighted MC input, master full, with respect to full output (1.2V) and 200uV input signal: -71dB flat -75dB A-weighted.

Cat. K44791 \$319

Assembled and tested \$599

packing and postage \$10

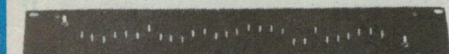

THIRD OCTAVE GRAPHIC EQUALIZER

SPECIFICATIONS: BANDS: 28 Bands from 31.5Hz to 16KHz.

NOISE: -0.008mV, sliders at 0, gain at 0 (=100%)


20KHz BANDWIDTH DISTORTION: -0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation).

REGULATION: see table

Unit: \$219

Assembled and tested \$429

packing and postage \$10

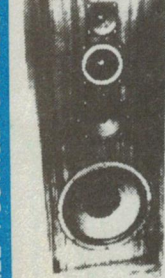

SERIES 4000 SPEAKERS

8 Speakers \$349

8 Speakers with Crossovers \$579


Speaker Boxes (assembled with grill and speaker cutout) \$349

Crossover Kits \$249

Complete kit of parts (speakers, crossovers, screws, innerband boxes) \$899

Assembled, tested and ready to hook up to your system \$995

Errors and Omissions Excepted

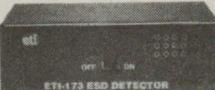

ELECTROSTATIC HAZARD DETECTOR KIT

It's called electrostatic hazard and it's even in your baby brother, jumps on the back of your IC or transistor, then the poor device is never likely to be quite the same again. So, out of a very ordinary collection of bits and pieces, ETI has fashioned a black box that will sit quietly on a corner of your bench for years at a time and beep when ever high tension appears. It may save you a lot of trouble, particularly if you ever work with CMOS. (ETI 173 May '86)

Cat. K41720

Please phone for price and availability

PLAYMASTER FM/AM STEREO TUNER

The new Playmaster FM/AM stereo tuner will out perform anything presently available on the market, regardless of price. As well as including a FM tuner section which is every bit as good as any other synthesised design, it is also the only unit featuring a genuine wideband, low distortion AM stereo tuner. Naturally, it has a digital readout, 12 station memory, automatic seek and an optional infrared remote control. (EA Dec '85 Jan-Feb '86 85u12)

Cat. K86020 \$399



40 W INVERTER

This 12 240 V inverter can be used to power up mains appliances rated up to 40 W, or to vary the speed of a turntable. As a bonus, it will also work backwards as a trickle charger to top up the battery when the power is on. (EA May '82) 82IV5

Cat. K82050 \$69.95

SAVINGS BOON!



50 W AMPLIFIER MODULE (ETI 480)


Cat. K44880

(Heatsink optional extra) \$27.50

100 W AMPLIFIER MODULE (ETI 480)

Cat. K44801

(Heatsink optional extra) \$29.95

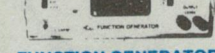

FUNCTION GENERATOR

This Function Generator with digital readout produces Sine, Triangle and Square waves over a frequency range from below 20Hz to above 160KHz with low distortion and good envelope stability. It has an inbuilt four-digit frequency counter for ease and accuracy of frequency setting. (EA April '82, 82A03A/B)

Cat. K82041 \$109



12-240V DC-AC INVERTER

INCLUDING 300 WATTS TRANSFORMER

This EA inverter is capable of driving mains appliances rated up to 300VA and features voltage regulation and full over load protection. (EA June '82) 82IV6

Nominal Supply: Voltage 12V DC

Output: Voltage see table

Frequency: 50Hz +/- 0.5%

Regulation: see table

Maximum Load: 300VA

Current Limiting: 30A (primary)

Efficiency: see table

Unit: \$219

Assembled and tested \$429

packing and postage \$10

OP AMP TESTER

The Op Amp Tester which could save you hours in agonising whether that old op amp that's been sitting in the draw for the last year. (ETI April '85, ETI 153)


Cat. K41830 \$26.50



ELECTRONIC MOUSETRAP

This clever electronic mousetrap disposes of mice instantly and mercifully, without fail, and resets itself automatically. They'll never get away with the cheese again! (ETI Aug '84) ETI 1524

Cat. K55240 \$34.95

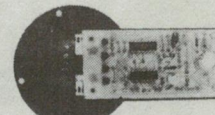

EA SUPER SIREN

Ever wanted to build an earsplitting alarm which would be compact and not draw much current? This is just the circuit for you. It uses a piezo electric tweeter in a pulsed mode to form an arresting and very efficient alarm. (EA Nov '82) 82AL17

Cat. K82111 \$28.95

(battery extra)

AEM KITS!

AEM DUAL SPEED MODEM

The ultimate kit modem featuring 1200/300 baud, case etc. Exceptional value for money! (AEM 4600 Dec '85)

Normally \$169

THIS MONTH, ONLY \$149

AEM ULTRA FIDELITY PREAMP

Now in stock! This superb preamp includes: the case, components, prepunched front panel etc. There's nothing else to buy. (AEM 6100, Oct/Nov '85)

Cat. K90000 \$269

LISTENING POST (AEM 3500)

Cat. K93015 \$37.95

STROBE KIT

Includes perspex cover! (AEM 9500)

Cat. K93018 \$59.95

MULTI SECTOR ALARM STATION

Protect your home and possessions from burglars with this up to the minute burglar alarm system. It's easy to build, costs less than equivalent commercial units, and features eight separate inputs, individual sector control, battery back up and self-test facility.

Specifications:

• Eight sectors with LED status indication.

• Two delayed entry sectors.

• Variable exit, entry and alarm time settings: entry delay variable between 10 and 75 seconds; exit delay variable between 5 and 45 seconds; alarm time variable between 1 and 15 minutes.

• Resistive loop sensing: suits both normally open and normally closed alarm sensors.

• Battery back-up with in-built charger circuit.

• Built-in siren driver.

Complete kit including deluxe prepunched metal work and electronics for only...

Cat. K85900 \$129



PARALLEL PRINTER SWITCH KIT

tired of swapping when ever you want to change from one printer to another? This low-cost project should suit you down to the ground. It lets you have two Centronics-type printers connected up permanently, so that you can select one or the other at the flick of a switch. (ETI 666, Feb '85)

Cat. K46660 \$79.95



STEREO ENHANCER

Think of your stereo as it that sounds good! The greatest stereo hi-fi system loses its magnificence if the effect is so narrow you can't hear it. This project lets you cheat on being cheated and creates an 'enhanced stereo effect' with a small unit which attaches to your amp. (ETI 1405, ETI, MAR '85)

Cat. K45050 \$79.50



COMPUTER DRIVEN RADIO-TELETYPE TRANSMITTER KIT

Here's what you've been asking for, a full transmit-receive system for computer driven radio teletype station. The software provides all the latest "whizz-bangs" like split-screen operation, automatically repeating text message, printer output and more. The hardware uses tried and proven techniques. While designed to team with the popular Microbee, tips are available on interfacing the unit to other computers. (ETI Nov '84) ETI 755)


Cat. K47550 \$135



ZENER TESTER

A simple low cost add-on for your multimeter. This checks zeners and reads out the zener voltage directly on your multimeter. It can also check LEDs and ordinary diodes. (ETI May '83) ETI 164

Cat. K41640 \$11.95

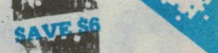

EA AM STEREO DECODER

AM stereo is now broadcast in Australia on an experimental basis. This add-on decoder works with the Motorola C-QUAM system. (EA Oct '84) 84MS10

Cat. K84100 Normally \$26.95

SPECIAL, ONLY \$20.95



ELECTRIC FENCE

Mains or battery powered, this electric fence controller is both inexpensive and versatile. Based on an automotive ignition coil, it should prove an adequate deterrent to all manner of livestock. Additionally, its operation conforms to the relevant clauses of Australian Std 3129. (EA Sept. '82) 82EF9

Cat. K82092 Normally \$19.95

SPECIAL, ONLY \$14.95




TRANSISTOR TESTER

Have you ever doubted a suspect transistor, only to find that it checks OK? Trouble-shooting exercises are often hindered by this type of false alarm, but many of them could be avoided with an "in-circuit" component tester, such as the EA Handy Tester. (EA Sept. '83) 83TT8

Cat. K83080 Normally \$18.95

SPECIAL, ONLY \$14.95

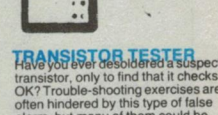

TRANSISTOR TESTER

Have you ever doubted a suspect transistor, only to find that it checks OK? Trouble-shooting exercises are often hindered by this type of false alarm, but many of them could be avoided with an "in-circuit" component tester, such as the EA Handy Tester. (EA Sept. '83) 83TT8

Cat. K83080 Normally \$18.95

SPECIAL, ONLY \$14.95

ROD IRVING ELECTRONICS
48 High Street, NORTHCOE, 3070 VICTORIA, AUSTRALIA
Phone (03) 489 8866
48 A Beckett St. MELBOURNE, 3000 VICTORIA, AUSTRALIA
Ph. (03) 663 6151
Mail Order and correspondence
P.O. Box 620, CLAYTON 3168
TELEX: AA 151938

MAIL ORDER HOTLINE (03) 543 7877 (2 lines)

POSTAGE RATES

\$1-\$9.99	\$2.00
\$10-\$24.99	\$3.00
\$25-\$49.99	\$4.00
\$50-\$99.99	\$5.00
\$100-\$199	\$7.50
\$200-\$499	\$10.00
\$500 plus	\$12.50

This is for basic postage only. Comet Road freight, bulky and fragile items will be charged at different rates. Certified Post for orders over \$100 included "free". Registered Post for orders over \$200 included "free". All sales tax exempt orders and wholesale inquiries to RITRONICS WHOLESALE, 36 Fenwick Rd., Clayton. Phone (03) 543 2166


MasterCard **VISA**

Errors and Omissions Excepted

DEMISTER TIMER

Driving along in the wind and rain with a transparent rear window thanks to your demister is one of life's small satisfactions. Knowing it is heavily draining your battery is one of its small, cruel but typical tradeoffs. Forgetting to turn the demister off is an extra twist you can do without if you install the ETI-345 demister timer.

Neale Hancock

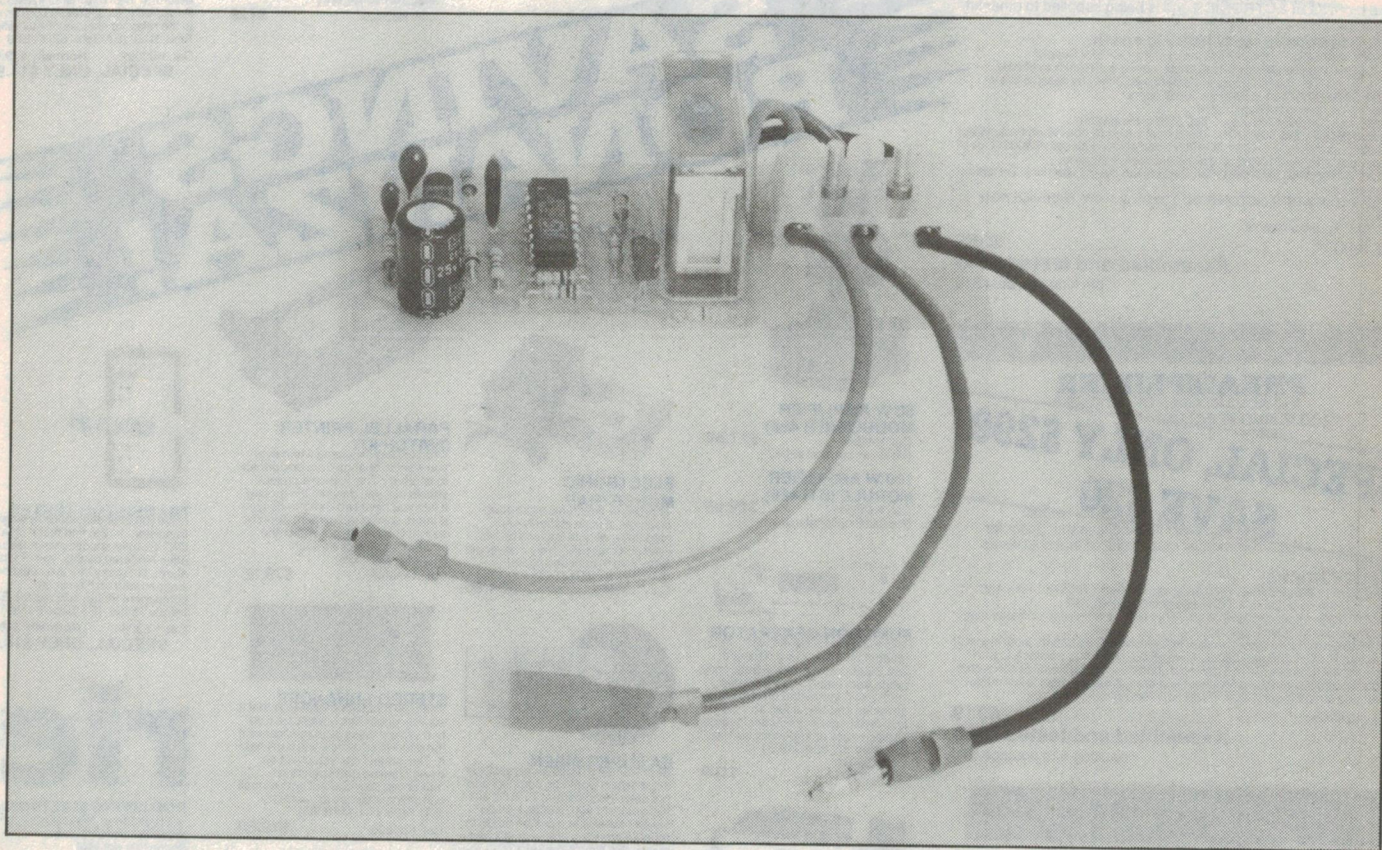

WINTER IS NOW here, bringing with it cold dark mornings and equally unpleasant evenings and a few extra problems for cars. Whenever we brave the elements to go to work or out raging, the electrical systems of

our cars in particular will have heavy demands placed on them.

Driving along with headlights on as well as the internal heater and a few hundred watts of music blasting out from the car hi-fi system, large amounts of current are drawn. Add to this the electrical current needed to supply a rear window demister and the car's ability to supply charging current to the battery is somewhat reduced. This situation is made worse when driving in wet conditions and in heavy traffic, because the alternator is not capable of supplying as much current when the car is travelling slowly. And reduced charging current can cause the car's battery to be undercharged, leading to difficulties in starting the car.

The rear window demister needs to be

switched on only long enough for the window to demist, then it can be switched off. However, when concentrating on the traffic, especially in adverse weather conditions, that is easy to forget and the demister draws current unnecessarily.

The amount of current drawn by a rear window demister can be in excess of 10 amps, which is not surprising considering the area to be heated. Therefore, by reducing the amount of time for which the demister is operating, a lot of current can be saved — current which is better used to charge the battery.

The ETI-345 demister timer has been designed to switch off the rear window demister after a preset time of either 10 or 20 minutes. The circuit is triggered when the

TABLE 1

Timing constant M	Pins connected
1	1
3	1,2
7	1-3
15	1-4
31	1-5
63	1-6
127	1-7
255	1-8

HOW IT WORKS — ETI-345

When power is supplied to the voltage rails of the circuit, the combination of R1, C2, R2 and Q1 creates a delayed positive going pulse. R1 and C2 set the delay time for this trigger pulse to go high. This delay gives the circuit time to settle after the power has been applied to the voltage rails. R2 provides the negative going edge of the pulse. Q1 is a programmable unijunction transistor (or PUT for short) and its unique switching characteristics enable this delayed pulse.

The pulse from Q1 is received by pin 11 of IC1, which is an XR-2240 timer chip. The timing period is set by the combination of R5 and C3; the following formula can be used to calculate this time: $T = M \times R5 \times C3$. When $M = 255$, $R5 = 4.7M$ and $C3 = 1\mu F$, thus $T = 1198$ seconds, which is about 20 minutes. C3 has to be a tantalum capacitor to reduce leakage thus making the timing more accurate.

Since pins 1 to 8 are connected together

the timing constant, M, is equal to 255. When the link connecting pins 7 and 8 is omitted M is equal to 127, making the timing period 10 minutes. This timing constant is determined by the number of pins connected to the output (see Table 1). Resistor R7 provides a signal path from the output to the reset pin (pin 10).

The output signal from IC1 is high when it is counting through the timing period and goes low when it is finished. When the output is high the pnp transistor Q2 turns on, allowing current to flow through the coil of the relay. This current closes the contacts of the relay, thus switching on the rear window demister. When the output from IC1 is low, Q2 turns off and the coil of the relay de-energises via D2.

The zener diode D1 protects the circuit from ignition spikes when the car is started and C1 provides smoothing of ripples or irregularities on the voltage rails.

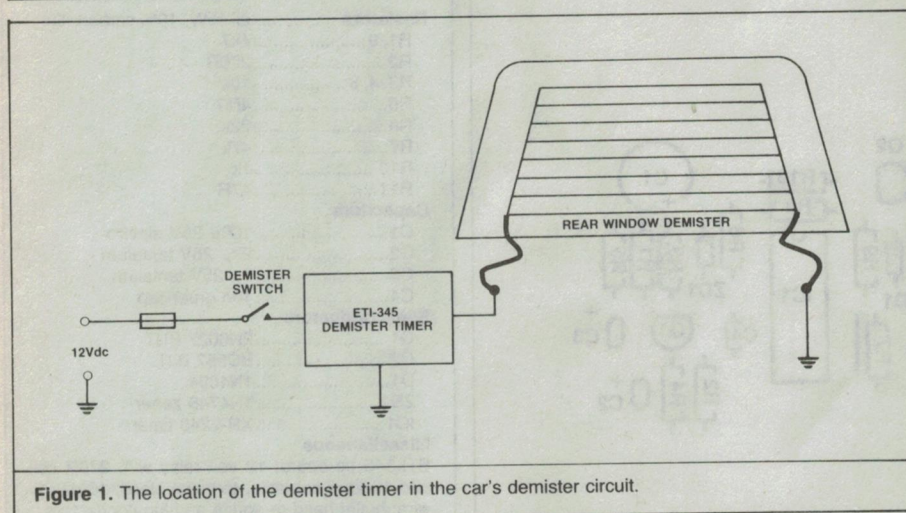


Figure 1. The location of the demister timer in the car's demister circuit.

rear window demister is turned on. Since the timer is triggered in this way, it does not require any external controls, and the circuitry for the timer can be located anywhere in the car.

The demister and the demister timer have a common source of current. Therefore when the demister is turned on, the timer is turned on. And since the timer is triggered by the demister being turned on, the trigger signal has to be delayed to give the circuitry time to settle before it is triggered.

Construction and testing

Firstly check your printed circuit board for shorted tracks especially in the vicinity of the two transistors; also check for breaks in the tracks. Solder in all the resistors and the capacitors, making sure that the tantalum and electrolytic capacitors are orientated correctly. Next mount the semiconductors and the IC, but check their orientation against the overlay before you solder them in.

If you require the unit to time for 30 minutes solder in the link located near IC1; if you require only 10 minutes of timing omit this link. However, to make testing the

unit less time consuming it would be a good idea to leave the link off the board until it has been tested.

Finally mount the relay and the terminal block and solder in three short lengths of 16 gauge wire to connect the pc board to the terminal block. To connect the demister timer to the car, use short lengths of wire with standard automotive connectors, such as bullet head or spade and lug type connectors to one end, then screw the other end into the terminal block.

To test the unit out of the car, connect the circuit to any twelve volt source. The relay contacts should close (this can be checked by testing for continuity between the wires which connect the circuit to the heating element). They should open again after 10 or 20 minutes (depending on whether you have the link in or out). If this does not happen check your pc board for wrongly mounted components or solder bridges.

Mounting and operation

The demister timer can be located anywhere in the car close to the car's demister circuit. Under the rear shelf near the rear

ADVERTISERS' INDEX



Acetronics	25
Amtex	62
Anitech	10
Audio Engineers	29
Australian AMP	68
Australian School of Electronics	69
Australian Telecommunications	
Employees Association	65
AWA Information & Control	7
Capricorn Computing Services	69
Chemical Treatments & Coatings	28
Disco World	33
Duet Electronics	45
Electri Board Design	25
Elmeasco	84
Energy Control	33
Entercom Computer Co	IFC
Entertainment Audio	65
ETI books	76,77
Eversharp	20
Geoff Wood Electronics	50
Heyden Spike	75
Icom	71
IEI Australia	29
Intertronics	9
Jaycar	34
Kalex	23
Kemproof Industries	25
L. M. Ericsson	8
Mach Systems	28
Marconi Instruments	89
Microbee Systems	72
NZ Marketing	11
Panel Print	23
Penn Central	26
Precision Graphics	20
Prepak Electronics	57
Printronic	18
Raychem Australia	25
Rod Irving Electronics	40,41,52,53,81
Rose Music	OBC
Scan Audio	33
Scientific Devices	62
Scope	17
Shreddall	23
Siemens Ltd	97
Soanar	92
STC	IBC
Subscriptions offer	90,91
Teknis	28
Tektronix	4
Telecom	66
Tennysen Graphics	20
Truscott Electronics	98
University of NSW	45

Project 345

window would be an ideal position, as it is accessible to all wiring and is out of the way. Wiring the demister timer into the car's demister circuit is illustrated in Figure 1.

Since the circuit is triggered by switching on the demister, its operation is pretty much automatic, however if the rear window starts to mist up again for any reason (heavy breathing in the back seat?) it can be retrig-gered by switching the demister off then on again. This will begin a new timing cycle.

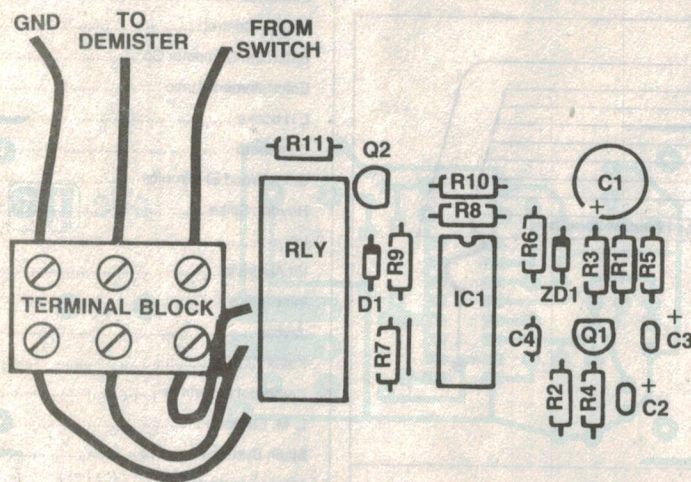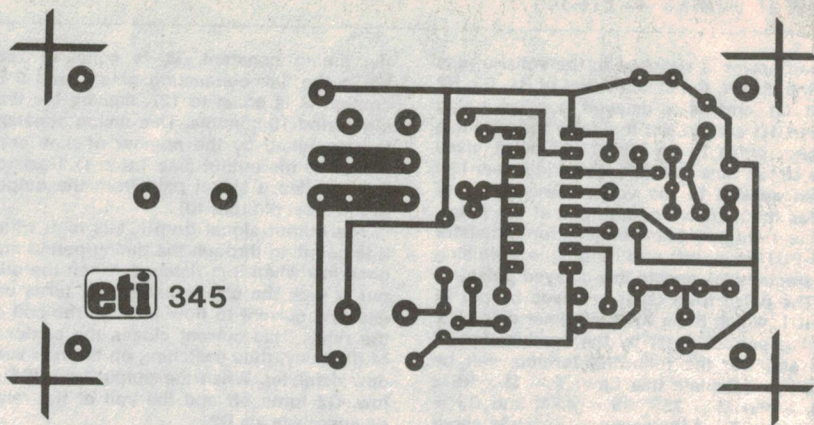Hopefully the ETI-345 demister timer will save our motorist-readers some hassles this winter. Happy and safe motoring!



PARTS LIST — ETI-345

Resistors.....all 1/4W, 10% carbon film

R1, 9.....4k7
R2.....220R
R3, 4, 8.....10k
R5.....4M7
R6.....22k
R7.....47k
R10.....1k
R11.....47R

Capacitors

C1.....100μ 25V electro
C2.....22μ 25V tantalum
C3.....1μ 25V tantalum
C4.....10n greencap


Semiconductors

Q1.....2N6027 PUT
Q2.....BC557 BJT
D1.....1N4004
ZD1.....1N4745 zener
IC1.....XR-2240 timer

Miscellaneous

ETI-345 pc board; 12 volt relay with 270R coil and 16 amp contacts; terminal block; 16 gauge wire; bullet head or spade and lug connectors.

Price estimate: \$15

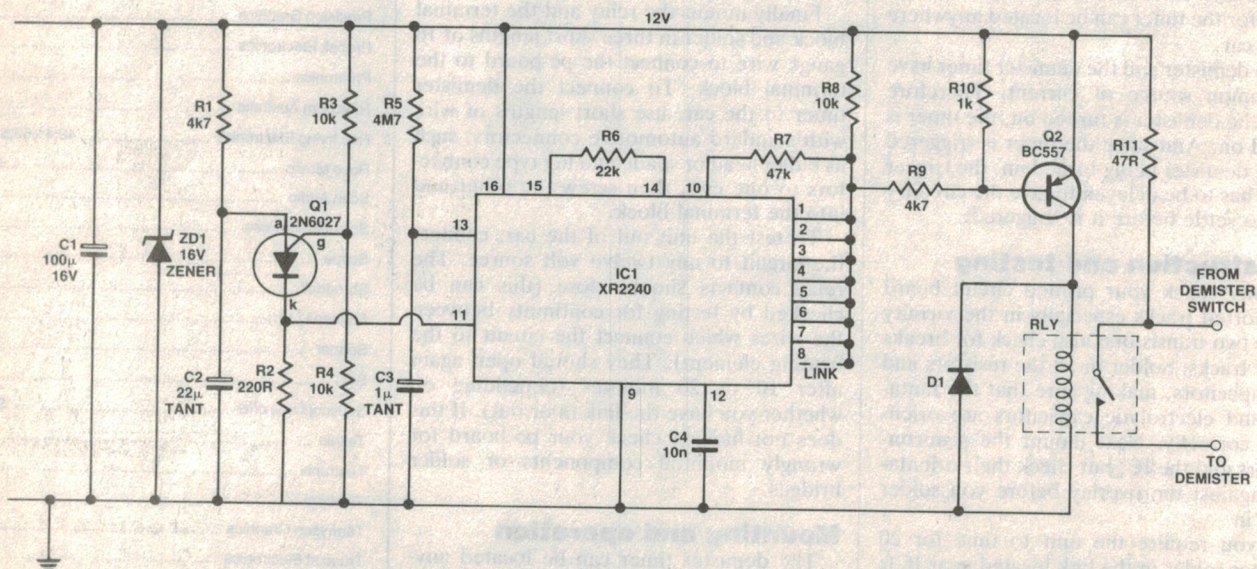

* grab a bargain!

THIS MONTH ONLY!

5 1/4" FLOPPY DISKS
DOUBLE SIDED \$27 per 10
DOUBLE DENSITY \$230 per 100
10 YEAR GUARANTEE (limited qty!)

PREMIUM QUALITY 'FUJI' RELAYS
12V DC \$2.95 ea
1% 3A 10+
CONTACTS \$2.50 ea
330A COIL PCB MOUNTING

PREMIUM QUALITY 'YELLOW' LEDS
20 ^{USUALLY 45c} _{Guaranteed 100%}
EACH or 100 for \$15

PREMIUM QUALITY 'ERNI' DTL SWITCHES
6 WAY PCB mfg.
COLOUR-CODED
\$2.00 ea
10+ \$1.75 ea

THERMALLOY HEATSINKS
for IC's
Suit 14, 16 pins
10+
were 95c now **50c ea 45c**

MINIATURE 12V DC DIL RELAYS
Single pole, 1KA
Electrothermal **3 ea**

PREMIUM QUALITY 'TEXAS' IC SOCKETS
Texas Instruments, so you know they're good!
BUY 100 - LESS 20%
16 Pin 20c 40 Pin 40c

600 PIV 250AMP STUD RECTIFIERS H.D.
\$15 ea **50c**
POSITIVE 8 PIN DIL
VOLTAGE REGULATOR LM376N

UHF CONVERTER for SBS CHAN 28
Tunable UHF 4/5 to VHF channel 1 **\$69**

IBM EXPANSION TYPE CHASSIS
Registered
ADD HARD DISK, UP TO 3x FLOPPY DISKS etc.
5x PC/XT/AT expan. slots
60/100W power supply
Cooling fan \$480 ea Tax free
Connectors \$424

SERIAL/PARALLEL CONVERTER
Ideal for IBM's
High performance CMOS design!
\$150

5 1/4" 40 TRACK DSDD FLOPPY DISK DRIVES
\$150 EA
NEW HALF-HEIGHT National

MINI-AMP for BUSKERS, Practice amp, etc.
Inputs - microphone, electronic organ, cassette
BATTERY OPER. 9V **\$79**

TV SIGNAL AMPLIFIER
4x75 ohm Outputs
12dB gain
VARIABLE **\$49.50**
were \$59.50 now

ADD HARD DISK, UP TO 3x FLOPPY DISKS etc.
5x PC/XT/AT expan. slots
60/100W power supply
Cooling fan \$480 ea Tax free
Connectors \$424

CENTRONICS PARALLEL GENDER CHANGER
36 Pin Socket ea
end-all pins wired through. **\$25**

PRINTER CLEAROUT! MICROLINE 84 EA **\$600**
200 C.P.S. (used) with gtee!
Others from \$300 new and used, daisy wheel from \$495

MINIATURE LAPEL MICROPHONES
CONDENSOR MIKE **\$15.00** EA
FM WIRELESS **\$18.00** EA

Reel-to-Reel 7" VIDEO TAPE
New, by HITACHI
were \$29 ea **ONLY \$15** EA

MAINS TRANSIENT VOLTAGE SUPPRESSOR
Ideal for computer, test equip, etc.
CHEAP **\$20**

24V BELL AC or DC 3" DIAM
English Chloride
Gent, 150mA curr **\$7.50**

MICRO PIEZO SIREN
12V DC 150mA
110dB output **\$17.50** each

ECONOMY FM MIC 88-108MHz
TRANSMITS TO 50W RANGE, CONCORDANCE RX!
Operates on two 1.5V pencil batt **\$10**

SYNCHRONOUS MOTORS WITH GEARBOX
3 MODELS - 4 or 6 RPM or 10 RPH, 240V **\$9.50** ea

ECONOMY CAR ALARM **\$35**
Voltage sensing Entry/Exit delays
Auto-reset
Inbuilt siren
Easy installation

ULTRASONIC CAR ALARMS
Complete and Self-contained, just add siren or horn, auto reset, entry/exit delays, LED light. **\$55**

FANTASTIC! CAR ALARM ULTRASONIC + RADIO KEY.
Interior motion detector, current door sensing, panic alarm button, inbuilt siren, delay, reset **ONLY \$179**

24V to 12V DC 7AMP CONVERTER
for trucks, buses, boats
REGULATED and protected **only \$35**

DOOR ALARM and CHIME
Changeable 3 digit code.
9V batt. **\$29.50** EA
Entry delay

DOOR MONITOR and INTERCOM
'Peep-hole' viewer with inbuilt 2way intercom for front door protection.
was \$14.95 SAVE **\$5** now **\$9.98**

ASSORTED POTS
20 MIXED VALUES Linear, log, our choice!
100 MIXED VALUES Dual, switched, all new
250 MIXED VALUES Bonus bulk package!
\$3 \$10 \$20

12V DC CAR ALARM FLASHING LIGHT
Comes on when the ignition is off! **\$12.90**

NEW! RF SIGNAL GENERATOR
100kHz-100MHz
were \$139 **\$89**

COMMUNICATIONS HEADSET
Low impedance mike - 200Ω
Headphone 32Ω
\$19.50 NEW!

ALARM CONTROL PANEL
• 4 INPUTS - N.O. and N.C. instant or delay.
• 6 LED STATUS INDICATORS
• Entry and Reset ADJUSTABLE DEL
• Inbuilt 24HR PANIC or FIRE alarm circuit.

New Passive INFRA-RED Detectors
12V DC, LED light, N.O./N.C. contacts includes mounting bracket
2 MODELS - 12m Wide beam **\$99** or 25m Narrow beam

JUST IN! WORMALD ALARMS:-
4 SECTOR ALARM CONTROL PANELS by famous maker! Complete and ready to instal was \$225..\$125
8 SECTOR ALARM CONTROL PANELS without case, micro-processor controlled, was \$295, now \$155
A FULL RANGE PASSIVE INFRA-RED & MICROWAVE & ULTRASONIC UNITS

3" 10 MHz OSCILLOSCOPE
AC-DC, 10mV per div
Auto-triggering
Solid state
Internal calibrate
New with warranty!
\$235 WERE \$330

VARIABLE TEMPERATURE SOLDERING IRON **\$29.95**
16-25 WATT

NEW, IMPROVED MODEL!
Dry cell or rechargeable 12V battery operation, heavy duty lockable steel cabinet, inbuilt siren and 12V power outputs. IDEAL FOR HOMES, SHOPS, OFFICES!
\$119

'ALARMING' SPECIALS
Aluminium Foil Tape roll \$5.00
Tape Terminals to suit...\$0.50
Reed Switch & Magnet...\$2.00
Key-operated Switch SPST \$5.00
12V DC Electronic Siren \$19.50
12V 1.2AH Gel Battery...\$19.50
12V 120mA Battery Charger \$8.50

BASIC ALARM MODULES
N.O./N.C. INSTANT AND DELAY CIRCUITS, SIREN and BELL OUTPUTS, 12V DC OPERATION.
was \$29.95 **HALF PRICE \$15**

5" 10MHz OSCILLOSCOPE
AC-DC, 10mV per div
Auto-triggering
Solid state
Internal calibrate
New with warranty
were \$430 **NEW! 4 ONLY!**
\$325

HIGH QUALITY HEAVY DUTY SOLENOIDS
24V AC \$3.90
110V AC \$1.25
240V AC \$4.50

Electromagnetic COUNTERS
Non - resettable
24V DC \$5.50
24V DC CHASSIS \$5.50
110V AC CHASSIS \$2.50
220V AC CHASSIS \$4.95

LGE DC MOTORS POWERFUL 3,000 RPM
6V-12V DC
47mm diam 60mm long
ONLY **\$5** ea

RELAYS
240V AC COIL
4 Changeover
10 Amp contacts
WHILE THEY LAST! **\$4.50** EA

PLASTIC 12 Pole TERMINAL BLOCKS
240V AC 10 AMPS **\$1.20** ea

1N5404 400PIV 3AMP Rectifiers
10 for \$2
100 for \$15

DESOLDER WICK
1.7 metres in plastic dispenser
3 for \$4
were \$2.00

1.5V-3V DC HOBBY MOTORS
\$1.50 EA
P&P \$3 +5% OF ORDER VALUE!

resistors
All Wanted Values 1 ohm-10 Meg. ohm.
WATT OR WATT
CARBON FILM
\$2

CAPACITORS CERAMICS
PACKS OF 100 ONE VALUE **\$4**
Greencaps
2 FOR THE PRICE OF 1

PRE-PAK electronics p/l

1a WEST ST, LEWISHAM, NSW

569-9797
24 HR PHONE ORDER SERVICE

Phone or mail order
BANKCARD accepted

INTELLIGENT MODEM

The ETI-684 is without doubt the most complex software project ever undertaken in an Australian magazine. It has a list of features equal to that of professional models worth twice the price, and conforms to all the principle data transfer standards available in Australia. If you own a micro and need to get into data transfer this is the answer. If you build nothing else this year, build this one!!

Part 4
S. K. Hui

UNFORTUNATELY, SPACE DOES not allow us to publish all the information you need this month. Those of you who are satisfied with kits will find them at quality suppliers with the complete series of articles. The circuit diagrams, artwork and construction instructions will be in next month's issue for those who like to make their own circuit boards.

In a departure from normal practice, we will not be publishing the software listing. It extends over 4K, and we cannot imagine anyone trying to enter it by hand. Copies of the EPROM will be available from ETI for a small fee if you can't get it from a kit supplier. Real suckers for punishment, or the

plain bloody-minded, will no doubt want to disassemble it to see what we did. Go for it!!!

Features

- V21 300/300 full duplex
- V23 1200/75 half duplex
- Automatic baud rate selection on reception (auto bauding)
- Other standards found overseas like Bell 103 and other 600/600 and 1200/1200 standards supported by the hardware
- Intelligent auto answer
- Intelligent auto dialling
- Fully software driven
- 48K RAM buffer

- Cassette interface under Viatel standard control
- Software controlled loudspeaking
- Responds to industry standard Hayes commands
- Especially tailored for use by both professional and hobby users


Protocols

We have only implemented two software protocols in version one of the software, because there are only two worth bothering about in Australia: the CCITT V21 and V23. The V21 standard is used by bulletin boards and in many other data communications that involve personal computers. Indeed, ETI has published several modems already that use this standard.


The V23 standard requires the modem to receive at 1200 baud and transmit at 75. This is the Viatel standard.

The total range of speeds that could be supported is defined mostly by the 7910 modem chip, and could include 75, 300, 600 and 1200 in both directions. If it is desired to use some of the other standards, this can be done by altering the software and it is likely that there will be some discussion on this in a future article. There are some applications where it would be handy to go faster, but the chips necessary to implement these are horrendously expensive.

Another way of increasing speed without recourse to faster chips is to use non-standard coding techniques. For instance, the standard dictates that the modem communicates in a series of bytes, each containing seven bits. The bits are coded according to the ASCII standard. This means that every letter requires seven bits. Often, however, it's possible to put more information into the code than one would think. For instance, the code for A is 42hex. The code for B is 43h. Say we wish to send AB. One strategy might be to code A as 42h and B as 43h, and send 14 bits. Another way might

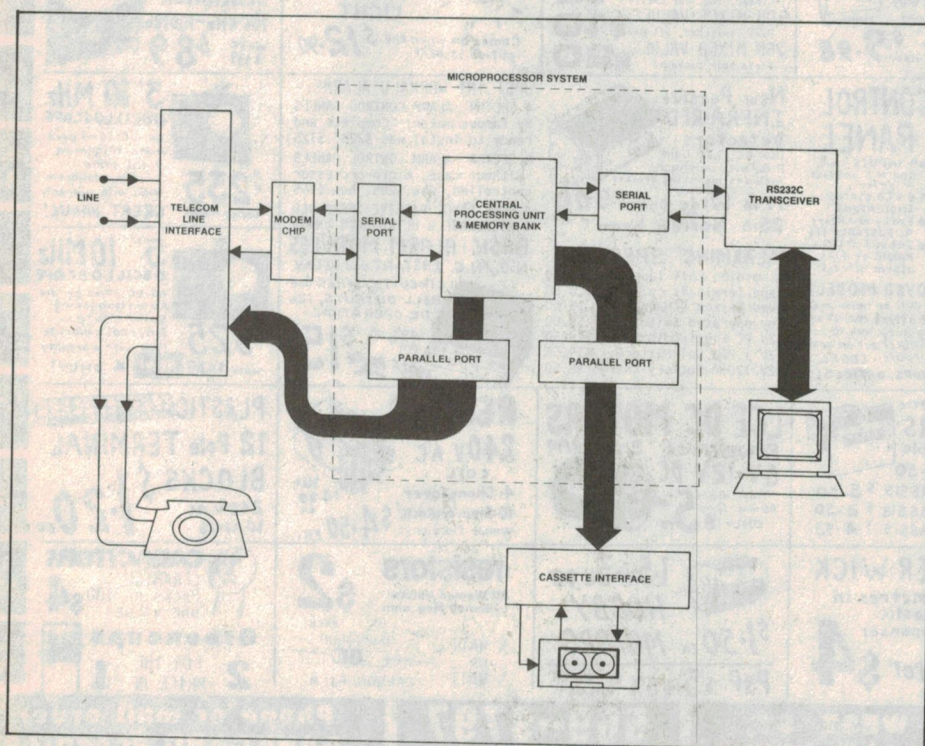

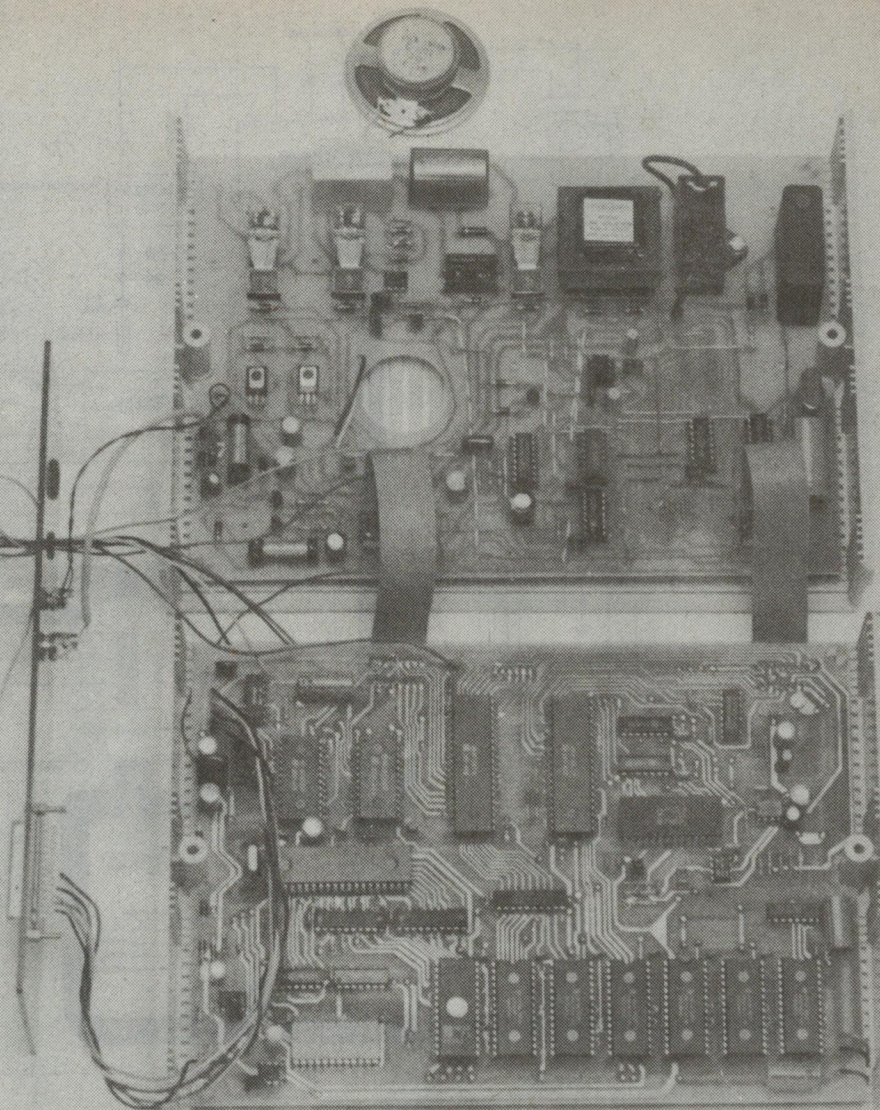This picture shows the architectural layout of the prototype. Despite the numerous components on the pcbs, two boards together with the loudspeaker will be in the same box. Note that since the modem is fully automatic, there are no toggle switches on the front or rear panels.



be to code A as 42h, but B as +1, ie, one more than the previous letter. Thus we need only eight bits to send the two letters.

In practice, it's possible to devise simple codes like this that almost double the speed of the modem, without any change to the hardware. Of course, there are obvious problems in implementing non-standard procedures in any transmission device so we have not offered that as an option in this software. Nevertheless, it's worth thinking about if you are setting up a network where you will have access to the modems at both ends of the line.

The CHDF command has an intelligent coding mode which, when active, sets a flag in the program. This can be used to cause a jump to a custom subroutine. If you are interested in this option it will be necessary to obtain a complete software listing.

One procedure we have adopted in order to increase both flexibility and operator ease is auto bauding. In this procedure, the chip is cycled through the four speeds, looking for the carrier from a sending modem. It

does this automatically when it wakes up, so the operator doesn't need to set it before it can receive.

Intelligence

The automatic dial and answer functions employ a considerable degree of sophistication to enable them to do their job properly. In parts 1 and 2 (December and February) we published in-depth descriptions of how they work.

In our experience, the modem is now intelligent enough to recognise any conceivable situation on the line and respond appropriately. The situation is complicated by the fact that the ETI-684 is designed to be fitted in parallel with the phone. Many auto answer modem designs require a separate dedicated phone line because it's so difficult to handle all the permutations of line condition caused by the local phone.

For instance, we experienced considerable difficulty in making the software recognise the difference between the local phone being picked up and incoming ring tone.


The dial relay pulses from the local phone sent the program berserk. In the end the problem was solved with some discriminating timing.

Of course, it behoves one to be a little bit humble at this point. One never knows what the real world is like until it's been experienced.

Storage

There are two storage mediums on the ETI-684: RAM and cassette. The RAM has a number of uses. It's used to store files, either from the local terminal or from the line. It's necessary to run the software, because stack pointers and other temporary numbers are stored there. Also important: it's used to store user selectable parameters that allow the modem to be configured to the user's requirements.

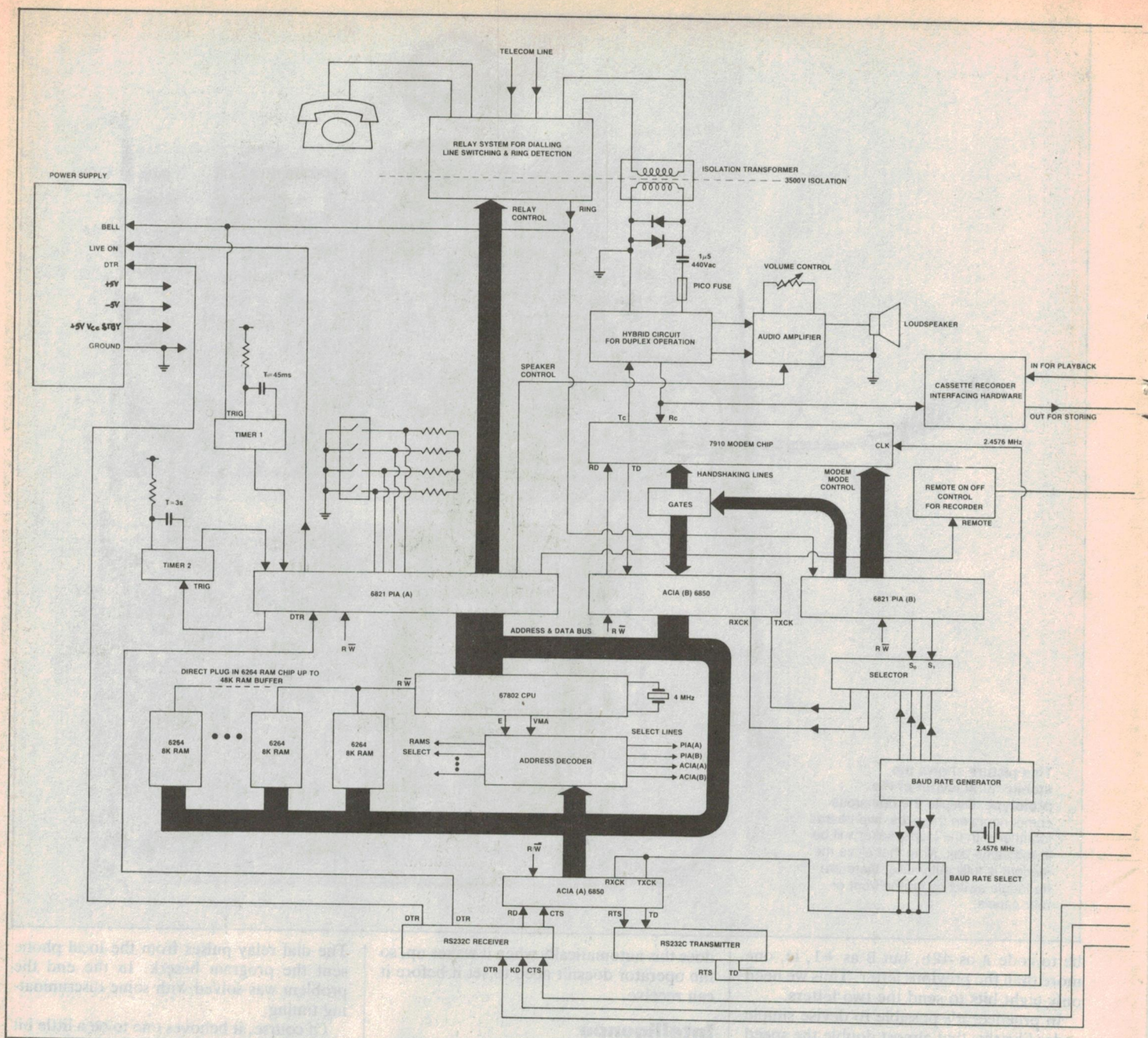A minimum of 8K must be in place for these functions to work. This is contained in one 6264 RAM chip. It's possible to increase RAM size to 48K by simply plugging in another five ICs. The primary function of



the extra RAM is for storing long files when the modem is unattended. It's also useful to transfer files into the modem memory from the local terminal's memory because then the modem can do its transmission while the terminal is used for other things. To extract files from the modem it's merely necessary to enter NEWS at the terminal. This will cause the stored text to be displayed one page at a time on the screen.

48K is a reasonably long text file, but it's rather limiting if you're transferring extensive data files, or programmes. The software will send an overload signal when the RAM overflows, which stops the data coming down. This is probably OK if the operator is in attendance, but the idea of the auto answer facility is that the unit should be able to operate without human interference.

What to do? Bigger memory is certainly a viable answer, but it's a very expensive way of providing sizable mass storage. A disk drive would be a better bet, but the drive and control circuitry is rather complex, and the data storage not all that great, say 360K.



What about some old fashioned storage? Tape has some fantastic advantages. Apart from being cheap, it records the audio signal direct from the line. To operate a disk it's necessary to strip off the audio frequency and then record standard binary bits, together with a substantial overhead in terms of control bits generated within the drive itself. The usual problem with tapes, their slowness, is not really relevant here because it's quite capable of recording at the same frequency as the signal coming down the phone line.

An additional advantage of tape is that a special escape code has been formulated within the Viatel protocol to allow for automatic start/stop of the tape player. This means if the modem receives the escape code IBh 36h, it will start the tape and so record the message. IBh 35h causes the tape to pause, and IBh 37h stops it. To see the tape contents on the screen of the terminal the operator enters PYBK on the keyboard.

Hayes commands

The full extent of the operating ability of the modem will be seen by considering the commands it responds to. Most of these are standard Hayes commands, although there are a couple that are non-standard, which we deal with separately.

Modem block diagram

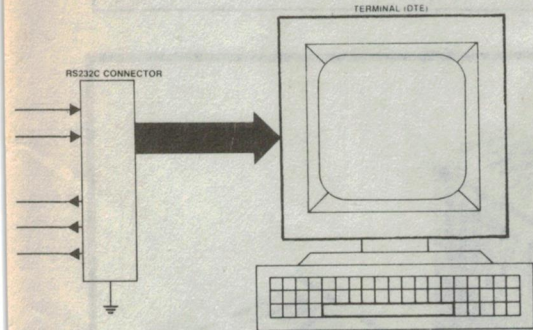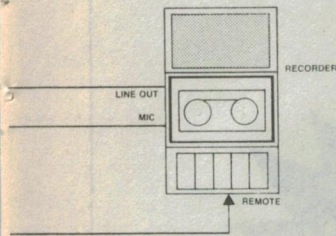

Speaker control:

M0 turns speaker off.

M1 turns speaker on during dialling, answering and call establishment, but off as soon as the call is established.

M2 turns speaker on.

Online/offline control:

ATO go to online.

+++ go to offline after one second wait.

Online means the terminal is connected directly to the line through the modem, so that anything typed on the terminal will be sent directly to line. Offline means that the modem is no longer connected to the line. Anything typed on the terminal and sent to the modem will be interpreted as a command rather than a message.

Project 684

Terminating a call:

ATH hang up the call and go offline.

Response message:

Q0 enable the sending of the modem response message to the monitor screen.

Q1 disable modem response message.

Dialling command:

ATDv,nnnnnnnx dial telephone number nnnnnnn, redial if busy, wait if ringing and put modem into the originate mode as soon as the other end loops the line. Initiate call set-up procedure automatically.

The prefix 'v,' is used if dialling through a PABX. If used, the modem will dial the number v, then wait for dial tone and then dial the number.

The suffix x may be any combination of R,# or ;. R puts the modem into the answer mode, # causes the modem to automatically transmit a user code up to 16 digits entered under the ID command, and ; causes the modem to go to offline mode once the call is established.

For instance, the code ATD9,6639999#R, will dial through a PABX using 9 to get out, call the number 663-9999, send a user code and put the modem into answer mode. On the other hand ATD6639999 just dials the number.

Non-standard commands

ATDnnnnnnnB The argument B instructs the modem to send out messages stored in the buffer automatically as soon as the call to number nnnnnnn is established.

CHDF displays the parameters stored in the RAM and allows them to be changed. These parameters are baud rate, protocol, number of redials, number of repeats to a non-data answer, intelligent coding mode and on/off control.

BUF Every character received from the local terminal will be put into the buffer instead of being transmitted to line. Buffer overflow message will be reported if RAM buffer overflows.

ID sets the Viatel user identity number or bank transaction number (up to 16 digits).

PYBK displays the contents of the tape on the screen.

CS0 turns on the local cassette recorder.

CSF turns off the local cassette recorder.

NEWS displays RAM contents.

KILL instructs the modem to shut down its power supply. It is only used if the terminal does not have a DTR line. If the modem has a DTR line on its RS232 interface, then the power supply will shut down as soon as the terminal is turned off.

Been burgled?

Engine cross-firing?

Light bulbs burning out?

Can't share your printer?

Haven't got a light meter?

Aren't sure of your CRO's calibration?

Can't pick-up stereo on your AM radio?

Don't know where those vibrations come from?

You need Electronics Today's



great new selection of Projects!

Simple for the Beginner!


Great for the Hobbyist!



At your Newsagent now!

Or send \$3.95 plus \$1.50 post and packing to The Federal Publishing Co, PO Box 227, Waterloo 2017 NSW.

LABORATORY POWER SUPPLIES

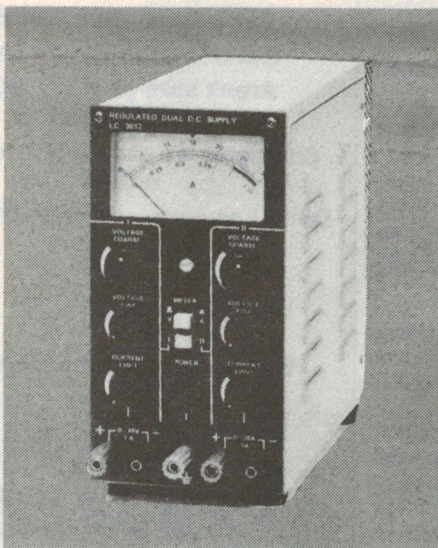

From \$196 (not including sales tax)



SCIENTIFIC DEVICES AUSTRALIA PTY. LTD.

VIC. 2 JACKS RD., SOUTH OAKLEIGH. 3167
PHONE: (03) 579 3622 TELEX: AA32742
NSW: 559A WILLOUGHBY RD., WILLOUGHBY 2068
PHONE: (02) 95 2064 TELEX: AA22978
S.A. 31 HALSEY RD., ELIZABETH EAST. 5112
PHONE: (08) 255 6575 TELEX: AA88125

APLAB offer a complete range of regulated DC bench/rack power supplies combining high precision and regulation capabilities with continuously adjustable outputs.

Designed with single, dual and multiple outputs, these power supplies can be used in either constant voltage or constant current mode of operation.

Standard models include:

SINGLE OUTPUT


OUTPUT: Output
VOLTAGE: Current
0-30V 0-1A to 30A
0-70V 0-2A to 10A

DUAL OUTPUT

0-30V 0-1A to 2A

MULTIPLE OUTPUT

0-30V 0-2A to 5A

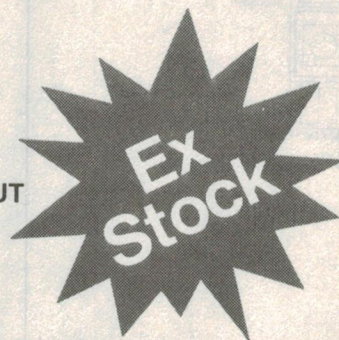


ETI READER SERVICE 178

DC/DC converters

**NOW AVAILABLE OFF THE SHELF,
29 MODELS OF DC INPUT SWITCH
MODE POWER SUPPLIES**

FEATURES

- INPUT-OUTPUT ISOLATION
- FLOATING INPUT AND OUTPUT VOLTAGE ALLOWS EITHER POLARITY
- INPUT VOLTAGES: 12, 24 or 48 V DC
- OUTPUT VOLTAGES: 5, 12, 15, 24 V DC IN EITHER POLARITY IN SINGLE, DUAL OR TRIPLE CONFIGURATION
- OUTPUT POWER: 12.5, 15, 40 or 50 WATT
- SHORT CIRCUIT PROTECTION
- OVER VOLTAGE PROTECTION
- HIGH EFFICIENCY SWITCH MODE
- LIGHT WEIGHT: 250 and 420 GM
- ENCLOSED BOX FOR SHIELDING AND EASY MOUNTING

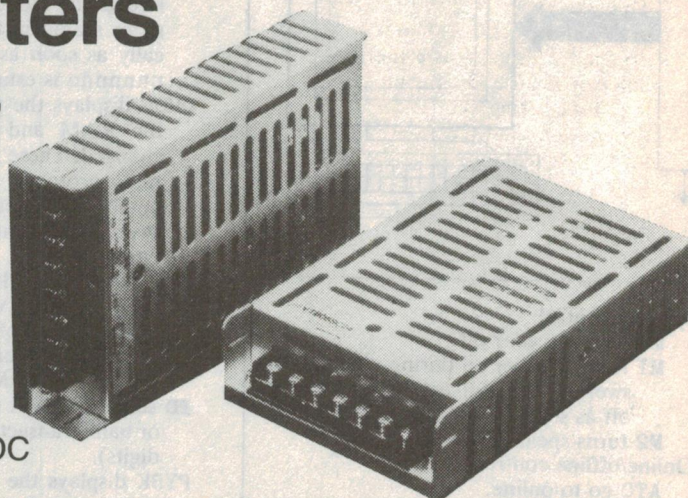

AMTEX

ELECTRONICS


A DIVISION OF TLE ELECTRICAL PTY LTD
36 LISBON ST FAIRFIELD, NSW 2165
Telephone: (02) 728 2121, 727 5444
Telex: AA27922 Attn Amtex
Facsimile: (02) 728 2837

ETI READER SERVICE 179

Mad Max radio

The idea of this circuit from **Todd Groman** of **Swan View, WA** is to adapt a CB radio so that it resembles those used in the movie "Mad Max". This involves hands-free operation, instant PA access and use of a well disguised siren in the car.

In this option, the mouthpiece is from a telephone mounted inside the CB, to provide better pickup. SW1 is the standard power on switch, SW2 and SW3 are for driver and passenger respectively and provide line transmit and voice operated transmit options. SW4 engages the PA option and sets the appropriate volume. SW5 allows the speaker to be used as an extension of the CB. SW6 controls the siren module.

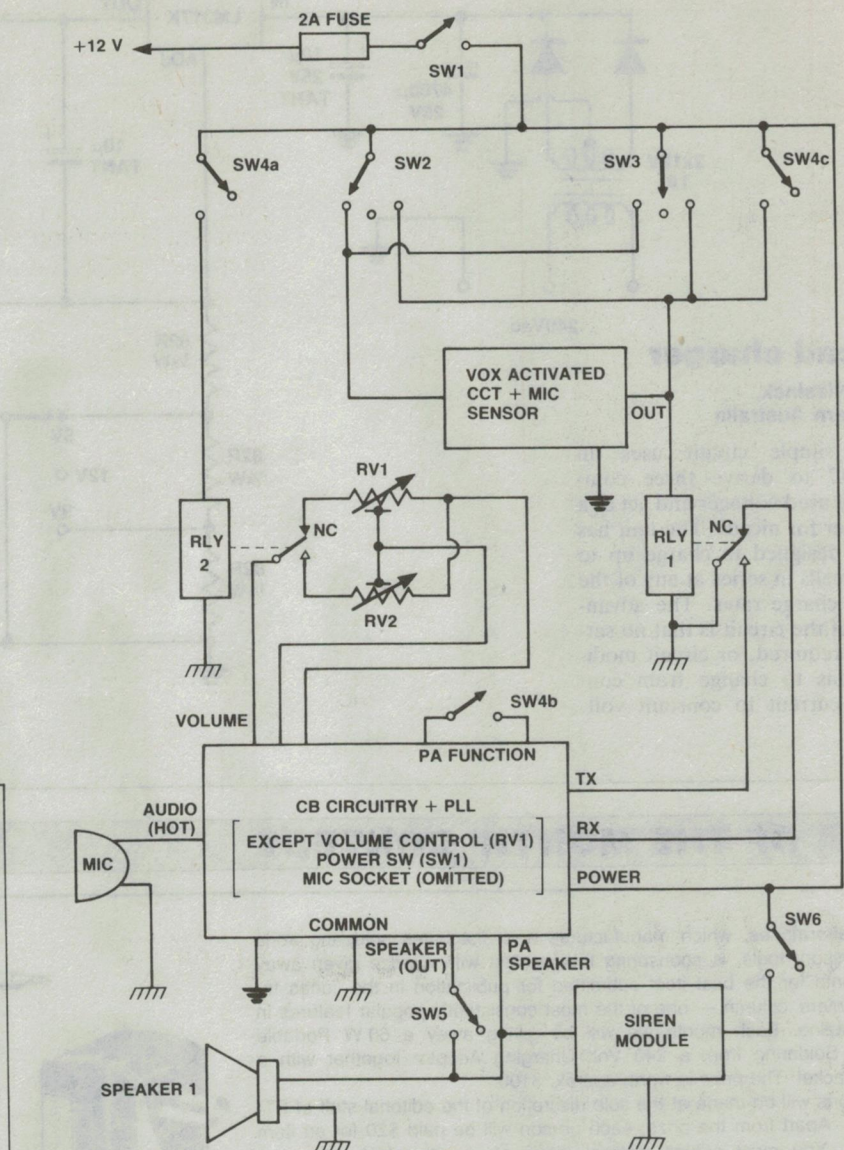


Sensitive heat detector


This idea from **J.P. van Leuven** of **Everton Hills, Qld**, was originally designed as a thermal detector for use in aero modelling. Free flying model aircraft depend on thermal conditions to gain height. A simple electronic detector is not sensitive enough to monitor the rate of increase in temperature necessary for this purpose. It can also be used around the house as a draught detector or to find where heat is being lost from a house.

An LM358 is mounted on a DIL board together with other components and the whole thing mounted in a small zippy box. From this extends a fibre-glass arrow shaft, connected to the box via a coaxial line plug.

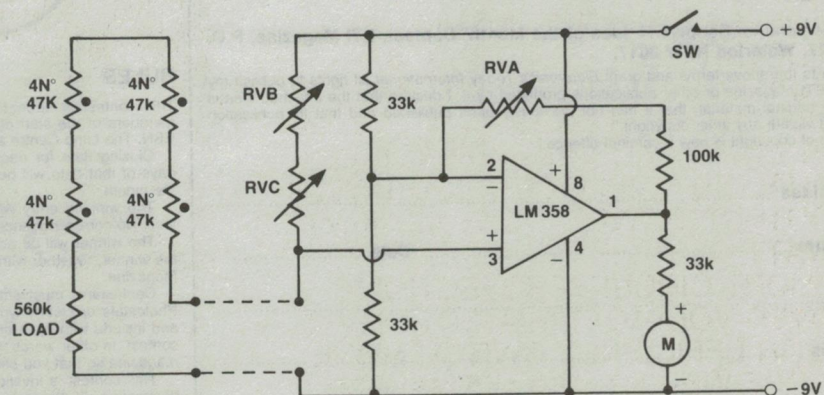At the sensing end four bead thermistors are protected from sun and wind by a shrouded head constructed out of rigid foam and a plastic cup. This assembly is epoxied on to the arrow shaft.



IDEA OF THE MONTH

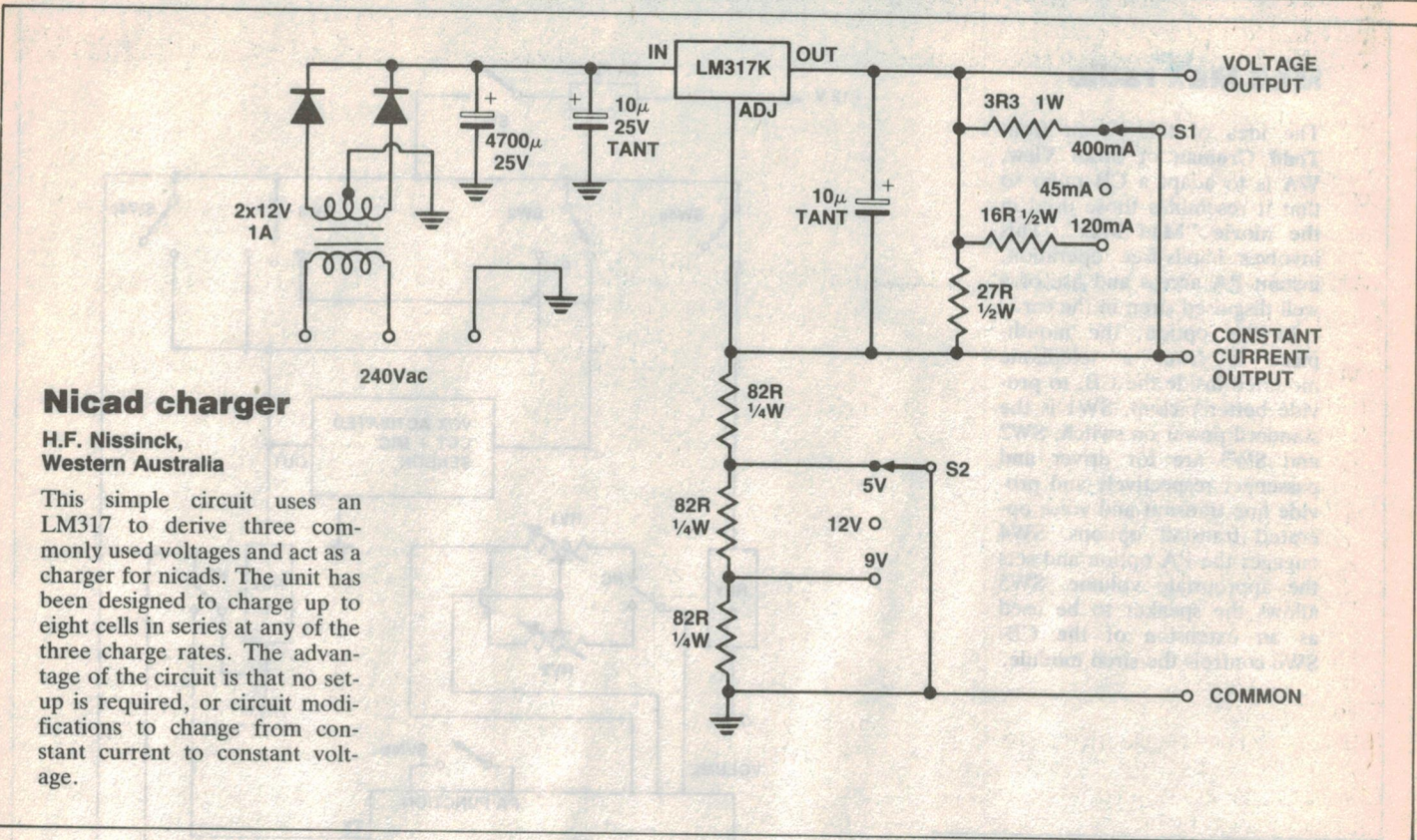

'IDEA OF THE MONTH' CONTEST

Scope Laboratories, which manufactures and distributes soldering irons and accessory tools, is sponsoring this contest with a prize given away every month for the best item submitted for publication in the 'Ideas for Experimenters' column — one of the most consistently popular features in ETI Magazine. Each month we will be giving away a 60 W Portable Cordless Soldering Iron, a 240-Volt Charging Adaptor together with a Holder Bracket. The prize is worth approx. \$100.

Selections will be made at the sole discretion of the editorial staff of ETI Magazine. Apart from the prize, each person will be paid \$20 for an item published. You must submit original ideas of circuits which have not previously been published. You may send as many entries as you wish.

COUPON

Cut and send to: **Scope/ETI 'Idea of the Month' Contest, ETI Magazine, P.O. Box 227, Waterloo NSW 2017.**

"I agree to the above terms and grant *Electronics Today International* all rights to publish my idea in ETI Magazine or other publications produced by it. I declare that the attached idea is my own original material, that it has not previously been published and that its publication does not violate any other copyright."

* Breach of copyright is now a criminal offence.

Title of Idea

Signature Date

Name

Address

Postcode



RULES

This contest is open to all persons normally resident in Australia, with the exception of members of the staff of Scope Laboratories, The Federal Publishing Company Pty Limited, ESN, The Litho Centre and/or associated companies.

Closing date for each issue is the last day of the month. Entries received within seven days of that date will be accepted if postmarked to and including the date of the last day of the month.

The winning entry will be judged by the editor of ETI Magazine, whose decision will be final. No correspondence can be entered into regarding the decision.

The winner will be advised by telegram the same day the result is declared. The name of the winner, together with the winning idea, will be published in the next possible issue of ETI Magazine.

Contestants must enter their names and addresses where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest. In other words, you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry.

This contest is invalid in states where local laws prohibit entries. Entrants must sign the declaration on the coupon that they have read the above rules and agree to abide by their conditions.


INTRODUCING THE TIME-SAVER/MONEY-SAVER CIRCUIT-BOARD-ARTWORK SOFTWARE

For only \$1,250 smARTWORK™ lets the design engineer create and revise printed-circuit-board artwork on the IBM Personal Computer (or equivalent).

Forget the tedium of taping it yourself or waiting for the technician, draftsman, or the CAD department to get to your project.

smARTWORK™ (Version 1.20) is the only low-cost printed circuit-board-artwork editor with all these advantages:

- ☐ Conductor spacing always correct.
- ☐ Lines don't become too narrow.
- ☐ Connecting lines do not intersect other conductors.
- ☐ Automatically seeks and draws shortest route between conductors.
- ☐ Quick correction and revision.
- ☐ Production — quality 2X artwork from a pen-and-ink plotter.
- ☐ Prototype — quality 2X artwork from a dot-matrix printer.
- ☐ Easy to learn and operate.
- ☐ Single-sided and double-sided printed circuit boards up to 10 x 16 inches.
- ☐ Multicolour or black-and-white display.
- ☐ Library storage and retrieval of your own commonly used layouts and pinouts.

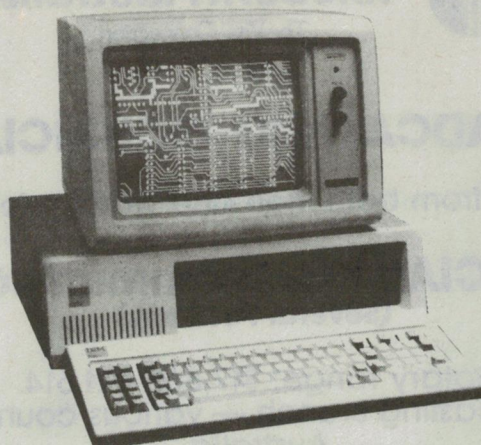

- ☐ Block movement and rotation for on-screen cut and paste editing.
- ☐ Place text on either board layer.
- ☐ Separate silk screen layer.

System Requirements (smARTWORK™ Version 1.20)

- ☐ IBM PC, XT or close compatible with 384K RAM, 2 disk drives.
- ☐ IBM Colour/Graphics Adaptor with RGB colour or B & W monitor.
- ☐ Epson MX/FX80/100 dot matrix printer.

- ☐ Pen-and-ink plotters:
Houston Instrument DMP42, 52
Hewlett Packard HPGL 7470, 75, 7580, 5, 6.

- ☐ Microsoft Mouse (optional), and other compatibles.


This revolutionary software package originates from the U.S.A. where it has a proven record for reliability.

Entertainment Audio of Adelaide are actually manufacturing the product locally, which has obvious benefits:

- ☐ Quicker availability of new releases and upgrades.
- ☐ Experienced engineers available to help or answer enquiries.
- ☐ For a FREE TRIAL of smARTWORK™ and further information, ring (008) 88 8414.



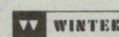Entertainment Audio P/L
A VILLAGE ROADSHOW COMPANY
59 KING WILLIAM STREET,
KENT TOWN, S.A. 5067
Phone (08) 363 0454



Representing WINTERK Corporation (USA) in Australia


ETI READER SERVICE 180

KEEP TELECOM  PUBLIC

ENDANGERED SPECIES

~~YOUR PRODUCT~~
~~YOUR BUSINESS~~
~~YOUR EXPERTISE~~

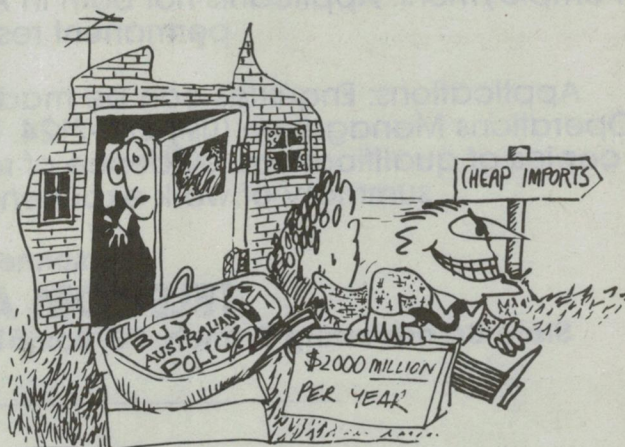If Telecom is privatised, its 'Buy Australian' policy would disappear overseas along with Australian expertise.



Further information: **AUSTRALIAN TELECOMMUNICATIONS EMPLOYEES' ASSOCIATION**
PO Box 472, Carlton South, 3053.



Telecom Australia

The Vital Connection

BROADCASTING TECHNICIANS

Applications are invited from both men and women for the following position:

TECHNICIAN (Telecommunications) (Several Positions)

Salary range: \$17,865-\$21,614.

Locations: State Broadcasting Branch — various country locations, Western Australia.

Duties: Operate and maintain broadcast and television transmitters.

Qualifications: Applicants should possess a Trade Certificate as Technician (Radio) or (Television) and have experience in sound radio or television transmitter operation and maintenance. Possession of a Broadcasting or Television Operators Certificate of Proficiency is a preferred additional qualification but not essential.

NOTE: Shift work could be involved.

Conditions of service: Excellent working conditions exist including permanent appointment to Telecom Australia 9-day fortnight, 4 weeks recreation leave, cumulative sick leave of 2 weeks full pay and 2 weeks half pay per year, maternity leave, 3 months long service leave after 10 years and a contributing superannuation scheme.

The successful applicant must satisfy the prescribed medical standard for permanent appointment which is usually determined prior to commencement of employment. Applicants not born in Australia must provide evidence of their permanent residency status.

Applications: Enquiries can be made by telephoning the Broadcasting Operations Manager on (09) 420-7124. Written applications accompanied by copies of qualifications, evidence of residency if appropriate and detailed summary of work experience to be submitted to the:


Personnel Officer

TELECOM AUSTRALIA

State Broadcasting Branch, PO Box 6155, Hay Street East, PERTH WA 6000

Telecom Australia is an equal opportunity employer.

Epson PC debut

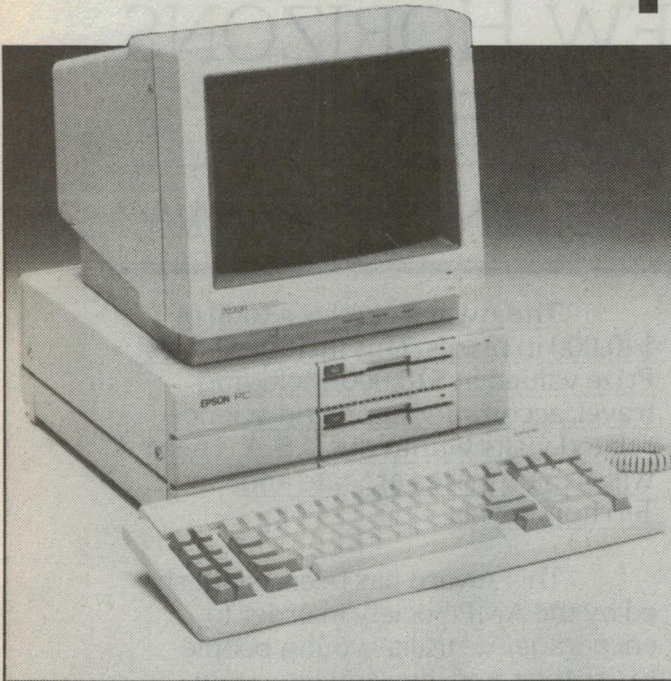

The new Epson PC is a high-performance 16-bit desktop computer that features streamlined design and modularity to meet needs for expansion, at a competitive price.

In base configuration, the Epson PC will sell for \$2450 plus tax while a completely optioned system featuring a Taxan Supervision III colour monitor will retail for \$3450 plus tax.

The Epson PC will be available in two factory configurations: dual floppy disks or single floppy with a 20 megabyte internal hard disk, both with a massive 512K of RAM.

The base configuration comes standard with an 8088 microprocessor, 512K of RAM (expandable to 640K), a 360K, 5¼" floppy disk drive, an IBM AT-type detachable keyboard, a built-in Centronics parallel printer port, an RS232C serial port and will be bundled with MS-DOS.

The other factory-built configuration

features a single floppy disk with a 20 megabyte internal hard disk.

A full line of components and peripherals includes a 12" RGB colour monitor with a corresponding colour/graphics video card; and a monochrome video card for either the floppy or hard disk versions.

The Epson PC can also be configured with all IBM-compatible enhancement cards. Other features include three full-size IBM standard option slots; an 8087 numeric co-processor socket; speaker; and front panel ac power reset and option switches for easy access.

For further information contact **Epson Australia, 17 Rodborough Road, Frenchs Forest, NSW 2086. (02) 452-5222.**

Lower cost LAN

Software Corporation of Australia has begun shipments to its dealers of an innovative network product which it claims will meet most of the networking needs of a majority of users — at a fraction of the usual cost.

The product, EasyLan, carries a recommended retail price of \$275 (plus tax if applicable) and consists of a 10 metre length of cable, a standard RS232 serial connector at each end of the

cable, and two floppy disks.

Installation of EasyLan is achieved simply by plugging the cable into the serial port of each IBM-PC standard computer and booting up with the provided software. Once mounted, the EasyLan software allows users to share disk drives, printers and modems.

Developed by Server Technology of Sunnyvale, California, the new product includes a pass-

word capability to aid security of files. While lacking many of the features of higher-end LANs, EasyLan does accomplish the two tasks which the majority of users need most of the time: transferring disk files from one computer to another, and sharing an expensive letter-quality printer or other peripheral.

Up to 10 personal computers can be linked in a star pattern using EasyLan. Because the

method of connection involves the serial port of the PC, an RS232 serial communications card needs to be available on each PC. Most IBM-PC standard computers already have that capability. In addition, the PC at the hub of the star needs a separate serial port for each PC connected to it. This is easily achieved through the use of a serial cable with inexpensive DB-25 connectors.

New diskettes

Skarbek Trading has released a complete range of computer diskettes including Media Tech disks, which are well established in the US. These disks are suitable for all popular PCs and come as single and double density, one or two sided. For more information contact Skarbek trading on (03)842-7087.

CSIRO Viatel service

The CSIRO now has a database on Viatel carrying information on home building hints, recently available CSIRO scientific informational video programs, CSIRO school project information and CSIRO publications. It can be accessed by the CSIRO Viatel index on screen 232.

Low cost serial/parallel converter

The Model 775 serial/parallel converter from Alfatron comes with an RS232 cable ready for plugging into a serial interface

BRIEFS

on a PC. It converts all serial data to parallel in the Centronics format. Internal shunts are provided to select baud rates, stop bits and parity for the serial side. For further information contact Alfatron on (03)758-9000.

PC-DOS to support extended memory boards

Digital Research Inc has modified Concurrent PC-DOS to take advantage of the extended memory capability now offered on the IBM PC. The boards enable Concurrent PC-DOS operating systems to run multiple large applications simultaneously. As well as the IBM PC, Concurrent PC-DOS runs applications for compatibles such as dBASE, Lotus 1-2-3 and WordStar. For further information contact Arcom Pacific on (07)52-9522.

AMP INVITES YOUNG AUSTRALIANS TO EXPLORE NEW HORIZONS IN POPULAR SCIENCE.

IF YOU ARE UNDER 19, ENTER NOW!

Anouncing AMP's "Beyond 2000" Science Award for 1986. Sponsored by Australia's largest insurer and most substantial investor, this Award is open to all Australians under the age of 19.

AMP's "Beyond 2000" Science Award invites young Australians to create working examples of how science can contribute to daily life.

The Award aims to promote enterprise and ingenuity among young people, and encompasses all categories of popular science.

Entries must demonstrate innovation, practicability and scientific and technological content. Entries may be as simple as a better safety pin or as complex as the creative mind can conceive.

The Award carries a total of \$40,000 in prizes. This includes a First Prize valued at \$18,000, including travel, accommodation and science-related visits within the U.S.A. There will also be prizes at State and Territory levels.

This Award has been established by the AMP Society in order to encourage Australia's young people to use their initiative and ingenuity. It is hoped that by attracting a wide range of new ideas this Award will be instrumental in causing the community at large to address the challenges in our day-to-day living in the period leading up to the next century and beyond.

The AMP Society is pleased to be associated with the Seven Network's popular series "Beyond 2000" and the Australian Science Teachers' Association.

Full details of how to enter are on the Entry Form and Conditions of Entry. These can be obtained from AMP offices and representatives, or from Science Teachers at Secondary Schools.



'BEYOND 2000' SCIENCE AWARD



Australians sharing Australia

For more information, an Entry Form and the Conditions of Entry, send this coupon to:

AMP "Beyond 2000" Science Award
Freepost 111, G.P.O. Box 2527
Sydney 2001

No postage required.

Name: _____

Address: _____

Postcode: _____

Telephone: _____


USED TEST EQUIPMENT

**WE BUY
WE SELL —
YOU WIN!**

**A NEW SERVICE TO
THE AUSTRALIAN
ELECTRONICS
INDUSTRY!**

For further information, contact:

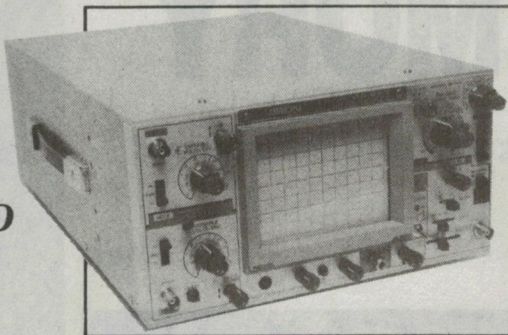**CAPRICORN COMPUTING SERVICES
PTY. LIMITED**
1st Floor, 1 Avon Road
North Ryde, 2113
Ph: (02) 888-3544



Capricorn Computing Services Pty Ltd, a well established broker of computer equipment, offer for the first time in Australia;

A TEST EQUIPMENT MATCHING SERVICE.

Selling — the perfect way to dispose of your surplus equipment and get that extra cash when its time to upgrade.

Buying — the price you pay is substantially lower than the new equipment price. A real alternative to the high cost of Test Equipment purchase and upgrade.

You tell us whether you are a buyer or seller (or both), what equipment you want to sell or purchase and if you have a specific model or your general requirements. We then match you up on our Database records with the equipment that you either want to buy or sell.

We do all the matching — Buyer to Seller Seller to Buyer. You win the rewards in dollars \$aved!!!

★ CRO'S ★ SIGNAL GENERATORS ★ LOGIC
ANALYSERS ★ DATASCOPIES ★ RADIO
EQUIPMENT ★ DEVELOPMENT EQUIPMENT
★ POWER SUPPLIES

Master the Microprocessor

Learn how Microprocessors
really work
... the practical way.

The Purpose of this Course

There is a considerable, expanding and world-wide demand for people with a real knowledge of microprocessors and general computer technology. Such people are needed to design and evaluate systems and to assess and develop the enormous range of possible applications, both present and future, of microprocessors and to understand the installation and servicing of the main types of equipment of which they may form the most vital component (A microcomputer has already been produced to replace the mechanical programmer on a domestic washing machine, for example.) This Course provides the necessary basic information to enable a student to really understand the functioning of microprocessors and their supporting circuitry.

usually referred to as the "hardware". This is backed up by showing how to program a microcomputer (or produce its "software") in the most fundamental form of computer language called "machine code". No previous knowledge of computers is necessary, though a little basic knowledge of electronics plus digital and logic circuits will be found helpful.

A special introductory short course is available to provide this back-ground information, if required by an individual student on the course without extra fee.

Student—Tutor Contact

A qualified Tutor is available to every Student throughout this Course in order to deal with any queries which may arise and to assess certain questionnaires which are issued to Students throughout the period of training.

Certificate

Issued to all Students completing the Course successfully. Course covers main requirements of the City and Guilds Certificates in Computers.

Practical Self Study Course

FREE COLOUR BROCHURE

Post coupon now. The Australian School of Electronics Pty. Ltd., P.O. Box 108, Glen Iris, Victoria, 3146.


Please send your brochure without any obligation to:

Name

Address

ETI 6/86

Postcode

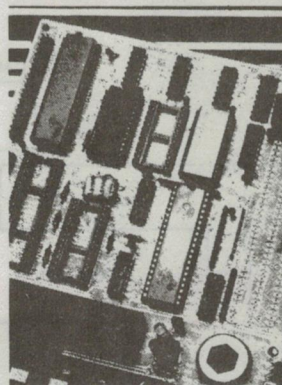

How the Course is organised

The basis for the practical work in the Course is the Microcomputer. This is supplied completely assembled and ready to use. The Course text is carefully arranged in sequence so that each new section follows logically from previous work. Hardware description and programming technique progress together, so that the Student is discouraged from treating them as distinctly separate subjects. Following each section of descriptive text, detailed instructions are given in order to use the Microcomputer to provide a practical demonstration of each new function or technique. This provides a very powerful way of learning precisely how the system operates, and enables any possible ambiguities in the Student's mind to be quickly resolved.

PROCESSOR AND MEMORY

Day one: the computer breakfast; a whirring processor and 1024 bytes of special K!

Phil Cohen

THIS BEGINS a new series that looks at the fundamentals of your computer. It's designed to teach you what actually makes a computer tick. By the end of the series, you should be familiar with all of the concepts you need to write simple programs in assembly language, and have a good knowledge of what goes on inside your computer.

Hardware

The most important parts of the computer are the processor and the various types of memory.

The processor is the central control mechanism of the computer, and everything

that the machine does depends on it. The processor follows the instructions that the programmer has given and passes commands and information to other parts of the machine, to the screen display, the loudspeaker, disk drive, and so on.

Physically, the processor looks unimpressive, it's just a large IC. Other ICs provide the computer's memory and a number of other interesting bits and pieces.

Memory

While it's following a program, there is often the need for the computer to store the intermediate results of a calculation, or

keep track of a game score or other transient facts. For this, the processor uses the 'RAM' part of its memory.

'RAM' stands for read and write memory (or random access memory) and it's the computer's scratchpad. Any information which is stored in RAM is lost when the computer is turned off. Of course, for things like game scores this doesn't matter at all.

There is another type of memory in the computer, called 'ROM' (read only memory). The difference between RAM and ROM is that the information in ROM is not lost when the computer is turned off, in fact, it's not possible to change what's stored in ROM without taking out the ICs that make up the ROM.

When a computer changes the information in its RAM memory, it's said to be 'writing to memory', just as you would write on a blackboard. When it looks at the information in its memory, it is said to be 'reading from memory'. This is the significance of the terms 'read and write memory' and 'read only memory'. The computer can never write to ROM, but it can read from and write to RAM.

Programs

Some types of program are stored in ROM and some in RAM. When you first turn the computer on, without a games cartridge in it (if it is that sort of computer) and with no cassette or disk in it, it will respond in some way by putting information on the screen, even just the name of the computer.

The program that tells the processor what to put on the screen when the computer is first turned on is in its ROM memory. It has to be, of course, because if it was in its


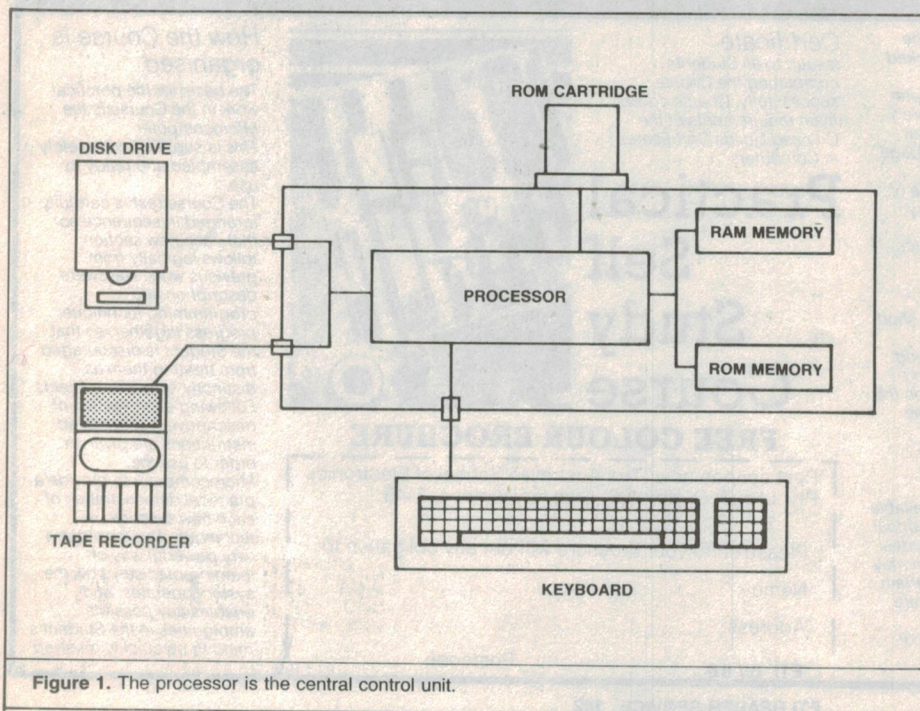
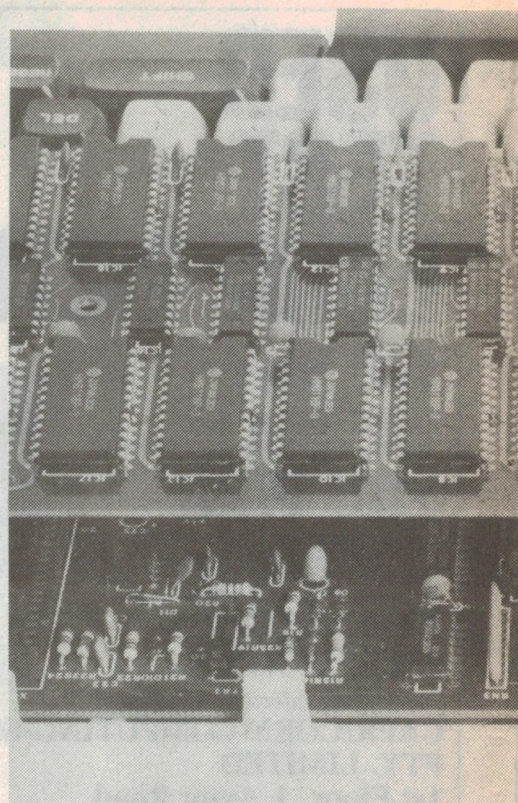


Figure 1. The processor is the central control unit.

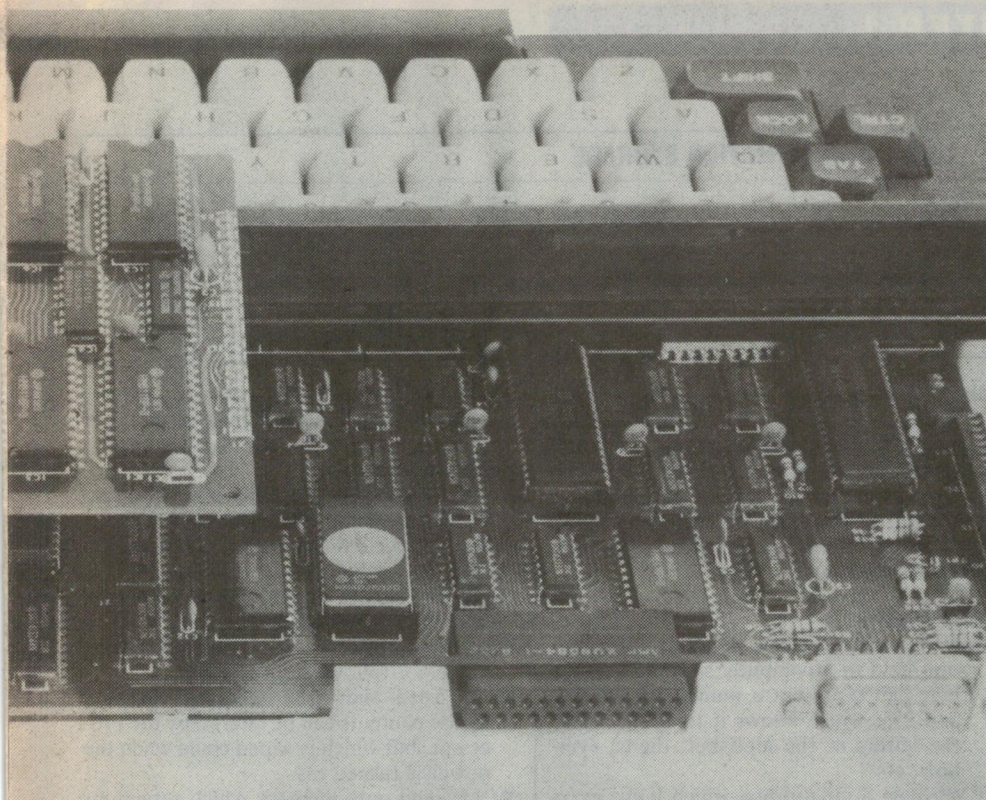

RAM, it would be wiped clean when the machine was turned off!

Programs that are not already in the computer when it is first turned on are stored in a number of different ways. These include a standard cassette tape that the computer stores a series of tones on like Morse code which it can later read as a program; a floppy disk which apart from its shape works in much the same way as tapes; and a cartridge or plug-in module that holds one program.

Programs that are loaded from tape or disk, or typed in from the keyboard are stored temporarily in RAM. When you turn the computer off, any program that you loaded in from tape or disk is lost. Of course, it's still on the tape, and when you want to use the program again all you have to do is to get the computer to load it from the tape into its RAM again.

Game cartridges are a little different. They actually contain ROM on to which the game program (or word processor, or whatever) has been stored. The advantage of cartridges over disk or tape is that you don't have to wait for the program to be loaded into RAM — it's right there on ROM waiting to be read by the processor as soon as the computer is turned on.

Tapes and disks are a bit like RAM in that the information on them can be altered by the computer. If, for example, you type a new program into the computer, you can store it on tape or disk so that it can be used again later. The information on the tape or disk is not forgotten when the computer is turned off.

You can also store other information such as a sequence of letters on tape or disk.

Inside a home computer. It's not as complicated as it looks.

Why do computer makers bother with RAM when tape and disk are better? Because RAM is a lot faster. Table 1 summarises the advantages and disadvantages of the various types of computer memory.

The 'K'

The amount of memory that a particular computer has is measured in 'Ks'. One K is 1024 addresses. Each address can hold one character such as a letter, digit or symbol, one thousand words of a magazine article (at an average five letters per word, plus a space) will take up around 6000 bytes, or approximately 6K of memory.

Notice by the way that 'K' is not the same as 'k'. The 'k' means 1000, while the 'K' means 1024. So one km is 1000 metres, and one kV is 1000 volts, but 1024 bytes is one K.

When measuring the size of memory, it doesn't matter which type of memory you are talking about; the K is used to measure the size of ROM, RAM, and even disk sizes.

For example, a typical computer nowadays will have 20K of built-in ROM (which holds all of the programs the computer needs when it is first turned on), 64K of RAM, and maybe a disk drive which can hold 360K of programs or other information.

Processor power

There are a number of different processors and different versions of the same processors on the market all of which have their

"WHICH RADIO DO I NEED?"

...THE ANSWER IS
IN THE PALM
OF YOUR HAND

Whatever task you have to do the ICOM IC-40 is the one that can handle it.

It's ideally suited for farming, transport, sports, bushwalking & boating. Whatever the communication problem you need to solve this is the radio that's being

proven every day in a million different uses.

Contact your local dealer for a demonstration of the most advanced CRS portable available in Australia.



Please post to:

ICOM AUSTRALIA PTY. LTD.
7 DUKE STREET WINDSOR 3182.
VICTORIA.

Name _____

Address _____

City _____

Postcode _____

or phone ICOM on (03) 51 2284

 **ICOM**
The World System

IC0014

ETI READER SERVICE 183

ETI June 1986 — 71

INSIDE YOUR COMPUTER 1

advantages and disadvantages. Two important measures of the power of a processor are its clock speed and the number of bits of information it can handle at the one time.

Processor speed is usually measured (a little misleadingly) in terms of the frequency of the clock oscillator that it is designed to run with. For example, one processor may be designed to run at 6MHz and another at 8MHz. I called this figure misleading because it is really only of use in comparing different versions of the same processor.

For example, a cheap version of a particular processor may be designed to run at 4MHz, but its military-specification counterpart (identical in every other respect) may run at twice the speed — 8MHz. The 8MHz version will process exactly twice the amount of information per second than the 4MHz version.

But a different type of processor altogether may run at 3MHz, and yet outperform either of the two 'faster' ones. This is because although it performs less instructions per second, the instructions may be far more powerful in themselves, allowing it to process *more* information per second. So speed is only of use in comparing different versions of the same processor.

The second figure that tells you some-

TABLE 1. INFORMATION STORAGE

Memory	Erased when machine is turned off?	Able to be changed by the computer?	Fast?
RAM	yes	yes	yes
Built-in ROM	no	no	yes
ROM cartridge	no	no	yes
Tape, disk (magnetic media)	no	yes	no

thing about processor power is the number of 'bits' it will handle. The 8080 processor, for example, is an 8-bit processor, while the 8086 is a 16-bit processor. I'll explain bits later on in the series, but in much simplified terms this means that the 8086 can handle twice as much information in a single step than the 8080 can.

Glossary

Byte: a measure of the amount of information held in a computer's memory; each byte can represent a number between 0 and 255, which allows it to store any of the letters of the alphabet, digits, symbols, etc.

Cartridge: a plug-in box which holds extra ROM with a program on it.

K: each K represents 1024 bytes of memory, enough for about 160 words.

Magnetic media: a name given collectively to disks, tapes and anything else that uses a magnetic field on a moving material to store information.

Memory: that part of a computer where information is stored outside the processor.

pcb: printed circuit board, on to which the computer is built.

Processor: the central control mechanism of the computer; a large IC.

Program: a series of instructions which the processor follows step by step.

RAM: read and write memory, memory whose contents can be altered by the processor, but which is wiped clean when the power is turned off.

ROM: read only memory which retains its information with the power off, but whose contents cannot be altered by the processor.

Attention! microbee users and admirers

ONLINE - A GREAT MONTHLY INFORMATION PACKAGE

For only \$25.00 per year, you can join the thousands of microbee owners who have found the way of keeping up to date and in tune with their microbee. Subscribers to Online, the microbee journal, are privy to the latest hardware and software releases, are entertained by a myriad of applications and are tutored in the latest languages.

Don't let your microbee rest! Put it through its paces with Online — your monthly upgrade kit in a magazine.



Online

ONLY
\$25
YEARLY

SUBSCRIBE NOW!

YES! Please enter my subscription, as marked, to Online for one year (12 issues) at a cost of \$25.00.

Name: _____

Address: _____

Town/Suburb: _____ State: _____ P/code: _____

METHOD OF PAYMENT: ☐ Money Order/Cheque

☐ Please charge my

Expiry Date: _____ Signature: _____

- Unless otherwise stated, your subscription will commence from the next issue to be published upon receipt of this form.
- Single copy price \$2.95 plus 30 cents p+h per issue within Australia.
- All subscriptions and enquiries should be addressed to:
The Subscription Officer, Online, P.O. Box 41, West Gosford 2250.

Sphere

Warren Wilson,
Altona, Vic 3018


This program uses the hi-res graphic facilities of the Microbee to produce a simple sphere.

It has three options in size: large, medium and small. The large size sphere is large enough to see the effect of simple 3D graphics.

This program could be modified to use the colour facilities of colour Microbees or the simple structure of the sphere could be modified to produce many different sphere-like shapes, for instance footballs or doughnuts.

```
00100 REM GRAPHICS/MATHEMATICAL WARREN WILSON WOSOFT SOFTWARE1985
00110 CLS:POKE 220,25:INVERSE:CURS 16,1:PRINT" BASIC SPHERE BY WARREN WILSON
":NORMAL
00120 INVERSE:CURS 22,5:PRINT" INPUT SIZE OF SPHERE ":NORMAL
00130 CURS 25,6:PRINT"[1] LARGE SPHERE":CURS 25,7:PRINT"[2] MEDIUM SPHERE":CURS
25,8:PRINT"[3] SMALL SPHERE"
00140 CURS 21,10:INPUT"WHICH SPHERE NUMBER 1-3 ?":G
00150 IF G<=0 OR G>4 THEN CURS 21,10:PRINT[A50 32]:GOTO 120
00160 IF G=1 THEN LET N1$="LARGE SPHERE":GO=80:HO=15:G1=80:H1=45:G2=25:H2=45
00170 IF G=2 THEN LET N1$="MEDIUM SPHERE":GO=40:HO=7.5:G1=40:H1=22.5:G2=12.5:H2=
22.5
00180 IF G=3 THEN LET N1$="SMALL SPHERE":GO=20:HO=3.75:G1=20:H1=11.25:G2=6.25:H2
=11.25
00190 HIRES
00200 CURS 0:PRINT N1$
00210 FOR N=1 TO 700
00220 S1=S1+0.009
00230 SO=SIN(S1):CO=COS(S1)
00240 A=INT(GO*SO):B=INT(HO*CO)
00250 REM A=INT(80*SO):B=INT(15*CO)
00260 SET A+220,B+120
00270 C=INT(G1*SO):D=INT(H1*CO)
00280 REM C=INT(80*SO):D=INT(45*CO)
00290 SET C+220,D+120
00300 E=INT(G2*SO):F=INT(H2*CO)
00310 REM E=INT(25*SO):F=INT(45*CO)
00320 SET E+220,F+120
00330 NEXT N
00340 CURS 17,14:INPUT"DO YOU WANT ANOTHER SPHERE Y/N ?":S1$
00350 S1$=KEY:IF S1$="" THEN 350
00360 IF S1$="Y" OR S1$="y" THEN 110 ELSE POKE 220,111:END
```

LARGE SPHERE

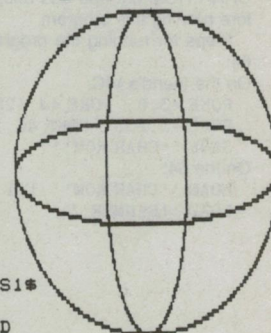

Sight read music

R. McFadyen,
Turramurra, NSW 2074

'Sight Read Music' is intended to be used by instrumentalists and singers.

When a note appears on the bar lines, the note should be played or sung. After a short delay (which is preselected at the start of the program) the note is sounded and named.

The range of notes is selected using the note code for the Microbee (1 to 23). The range can be limited to one note only if needed.

The program is for naturals only; a program for sharps would require the note codes in lines 350 to 410 to be changed to those for sharps. The data in lines 470 to 500 are read two at a time, the first being the vertical position on the screen and the second the corresponding note code.

```
00100CLS
00110 PRINT" Sight Read Music"
00120 INPUT"Select lowest note code ( 1 to 23 ) ":L
00130 INPUT"Select highest note code ( 1 to 23 ) ":H
00140 INPUT"Select delay (1 to 9)":T
00150 IFH<LTHEN100
00160 HIRES:REM draw lines
00170 FORY=112TO144STEP8
00180 PLOT 80,YTO440,Y
00190 NEXTY
00200 PLOT 80,112TO80,144:PLOT 84,112TO84,144:PLOT 440,112TO440,144
00210 PLOT 120,96TO128,88TO128,160TO136,160TO120,120TO128,112TO136,120TO128,128
00220 FORY=96TO160STEP8
00230 PLOT 300,YTO315,Y
00240 NEXTY
00250 FORN=1TO28:REM select note
00260 READY,C
00270 IFC<LTHEN460
00280 IFC>HTHEN460
00290 X=306:REM draw note
00300 PLOT X,YTOX+4,Y:PLOT X+1,Y+1TOX+3,Y+1:PLOT X,Y-1TOX+4,Y-1
00310 PLOT X,Y-2TOX+4,Y-2:PLOT X+1,Y-3TOX+3,Y-3
00320 CURS272:PRINT" "
00330 PLAY0,T*4
00340 CURS272
00350 IFC=10RC=13THENPRINT"A"
00360 IFC=30RC=15THENPRINT"B"
00370 IFC=40RC=16THENPRINT"C"
00380 IFC=60RC=18THENPRINT"D"
00390 IFC=80RC=20THENPRINT"E"
00400 IFC=90RC=21THENPRINT"F"
00410 IFC=110RC=23THENPRINT"G"
00420 PLAYC,8:REM play note, erase note
00430 PLOTI X,Y-1TOX+4,Y-1:PLOTI X,Y-2TOX+4,Y-2:PLOTI X+1,Y-3TOX+3,Y-3
00440 PLOTI X,YTOX+4,Y:PLOTI X+1,Y+1TOX+3,Y+1
00450 FORY=96TO160STEP8:PLOT 300,YTO315,Y:NEXTY
00460 NEXTN
00470 DATA 133,16,105,4,145,21,117,9,149,23,121,11,101,3,125,13,97,1,109,6
00480 DATA 137,18,113,8,141,20,129,15,109,6,137,18,121,11,125,13,149,23
00490 DATA 133,16,117,9,141,20,101,3,129,15,97,1,113,8,105,4
00500 DATA 145,21
00510 RESTORE:GOTO250
```


Banner

Chris Baird
Glendale, NSW

The idea for this program came as a result of looking at all the printouts around high school that had been done by 'Print Shop'. It prints strings up to ten characters long on to the printer. The word can be centered or not, have the letters character used as the pixel or a character of your choice as the pixel.

People with 64s will need to find a friend with a VIC-20 and save the CHAR ROM on tape and reload it before running this program.

Steps for running the program on a 64:

On the friend's VIC:

POKE 43,0 : POKE 44,128
POKE 45,255 : POKE 46,143
SAVE 'CHAR ROM'

On the 64:

LOAD 'CHAR ROM',1,1
LOAD 'BANNER'

```
0 REM BANNER
1 PRINT"Q"
10 INPUT"STRING";A$
20 IFLEN(A$)>10THENPRINT"SORRY, BUT THE STRING IS TOO LONG."GOTO10
25 IFA$=""THENEND
30 INPUT"CENTERED (Y/N)";B$
35 Z$=""
40 IFB$="N"THEN51
50 IFB$="Y"THEN61
60 PRINT"JUST TYPE Y OR N":GOTO30
61 INPUT"CHARACTER PRINTED(Y/N)";C$:C$=RIGHT$(C$,1):AL=0
62 IFC$<"Y"ANDC$<"N"THENPRINT"TYPE Y OR N ONLY":GOTO61
63 IFC$="Y"THENAL=1
64 IFC$="N"THENINPUT"CHARACTER";Z$:Z$=LEFT$(Z$,1)
65 IFB$="N"THEN100
70 A=5-(LEN(A$)/2)
80 FORI=1TOA:Z$=Z$+" ":NEXTI
90 Z$=Z$+A$
91 IFLEN(Z$)=10THEN94
92 Z$=Z$+" ":GOTO91
94 A=Z$
95 GOTO110
100 IFLEN(A$)=10THEN110
105 A$=A$+" ":GOTO100
110 OPEN3,4:OPEN5,4,6:PRINT#6,CHR$(21):CLOSE6
120 FORI=0TO7
130 FORI=1TO10
140 PRINT" "MID$(A$,I,1)
150 A=PEEK(7680)
160 S=32768+(A*8)+11
170 A=PEEK(S)
180 IFAL=1THENZ$=MID$(A$,I,1)
190 FORJJ=7TO0STEP-1
200 J=2+JJ
210 IF(AANDJ)=JTHENPRINT#3,Z$:GOTO220
215 PRINT#3," "
220 NEXTJJ,I:PRINT:NEXTI
230 PRINT:CLOSE3
240 GOTO1
```

Status

C. Groenhout,
Watson, ACT 2602

Status is written simply to show the status of the user port at any time. When RUN the program clears the screen and prints up eight 0s in the top left hand corner of the screen. When any switch from S0 to S7 is depressed a 1 appears in the appropriate position to represent the individual bits.

Status Draw, based around Status, uses the Super Expander to draw on the VIC's screen in high resolution. Pressing S0 will make the line go up, S1 goes down etc with diagonal lines possible. By pressing all four switches at once (S0-S3) the screen clears and the 'cursor' is reset to the centre of the screen.

```
' STATUS '
5 C=.5:PRINT"Q"
10 A=PEEK(37136)
20 FORB=0TO7
30 C=C*2
40 IF(AANDC)=0THENA$="1"+A$:GOTO50
45 A$="0"+A$
50 NEXT
60 PRINT" "A$:A$=" ":C=.5:GOTO10
```

```
' STATUS DRAW '
10 GRAPHIC2
20 X=80:Y=80:POINT2,511,511
30 A=PEEK(37136)
40 IF(AAND1)=0THENY=Y-1:IFY<0THENY=0
50 IF(AAND2)=0THENY=Y+1:IFY>159THENY=159
60 IF(AAND4)=0THENX=X-1:IFX<0THENX=0
70 IF(AAND8)=0THENX=X+1:IFX>159THENX=159
75 IFA=240THEN:SCNCLR:X=80:Y=80
80 POINT2,X*6.4,Y*6.4
90 GOTO30
```

Quado

C. Groenhout,
Watson, ACT 2602

Quado is a simple experiment in quadrophonic drawing in high resolution. The cursor starts in the centre of the screen and by using the keys I, J, K and M the cursor is moved around the top right hand quarter of the screen with the other three quarters following in suit. The result? A picture, in four colours, symmetrical in two axes which you can sell off to any uninformed person for a top secret plan of a new microprocessor! Note: This programme uses the Super Expander.

```
10 GRAPHIC2:X=80:Y=80:POINT2,511,511:POKE650,128
20 GETA$:IFA$=""THEN20
30 IFA$="I"THENY=Y-1:IFY<0THENY=0
40 IFA$="M"THENY=Y+1:IFY>80THENY=80
50 IFA$="J"THENX=X-1:IFX<0THENX=0
60 IFA$="K"THENX=X+1:IFX>160THENX=160
70 IFA$<"I"ANDA$<"J"ANDA$<"K"ANDA$<"M"THEN20
80 REGION2:POINT2,X*6.4,Y*6.4
90 REGION4:POINT2,X*6.4,(511-Y*6.4)+511
100 REGION5:POINT2,511-(X*6.4-511),Y*6.4
110 REGION6:POINT2,511-(X*6.4-511),(511-Y*6.4)+511
1000 GOTO20
```


SOLDERING & DESOLDERING?



GO NO
FURTHER THAN

HAKKO

☆ Easily replaceable, long life nozzle, ☆ Accurate temperature control
☆ Increased thermal capacity — 40W heater
☆ Powerful suction ☆ No clogging ☆ Quick, easy filter replacement
☆ Super quick heat up
☆ Super-accurate control over the entire temperature range between 160°C and 420°C ☆ High productivity for the professional user
☆ Hakko's unique temperature control which is sensorless, zero-cross, on/off switching



Heyden-Spike Co. Pty. Ltd.

Telephone: (02) 938-1566

Telex: AA74709

Fax: (02) 938-1467

ETI READER SERVICE 185

**Be part of
Today!**



When we analyse the recent past and project the immediate future, computers and communications technologies play a vital part, but we must avoid the tendency to look only to the hardware level. The fact that technologists have appropriated words like 'communications', 'information' and 'data' and given them electronic rather than social meanings, should not disguise the fact that in the final analysis, communications involves people and ideas, not electronic bit and bytes.

People and Ideas . . . that's the side of Australia's Communications Revolution we tell about in this informal look at today's world of computers and telecommunications.

At your Newsagent now!

Or simply send \$4.95 plus \$1.00 post and packing to —
Federal Marketing Book Sales, P.O. Box 227, Waterloo
2017 NSW.

SHOPAROUND

ETI-1402: Digital sampler

Now, for a fraction of the cost of the commercial product musicians can build this excellent sampler. The only likely difficulty to procure parts are IC3, ZN429 available from Ferranti Computer Systems, 22 Mandible St, Alexandria, NSW 2015, (02) 698-5544, and IC2 the National AD0820 available from Geoff Wood. Both Jaycar (02)745-3077 and Geoff Wood (02)427-1676 will have the complete kit, possibly All Electronic Components as well. Boards will be available from Rod Irving (03)543-7877, All Electronic Components (03)662-3506 and RCS Radio (02)587-3491.

ETI-173: Electrostatic hazard detector

Having this project in your workshop will save you heaps of trouble with your ICs or transistors by beeping whenever electrostatic hazard threatens. The complete kit will be available from Geoff Wood Electronics (02)427-1676 (nb: the new phone number following the GWE move) and All Electronic Components (03)662-3506. Printed circuit boards will be available from Force Electronics (08)212-2672 and from All Electronic Components.

ETI-345: Demister timer

This project is used to automatically turn off a rear window demister after 10 or 20 minutes. All Electronic Components, (03)662-3506, will stock the complete kit, as well as the pc boards. Force Electronics, (08)212-2672 will also stock pc boards. The only parts that might be difficult to obtain are the 16A relay, which will be obtainable from RS Components, (02)669-3666; and the XR 2240 timer, which will be available from Jaycar, (02)747-2022.

Artwork

For those constructors willing and able to make their own pc boards and/or front panels, we can supply same-size film transparencies of the artwork, positives or negatives as you require. From the list given

below, select what you want and address your request/order to:

'ETI-xxx Artwork'

ETI Magazine

PO Box 227

Waterloo, NSW 2017

When ordering, make sure you specify positives or negatives according to the process you use. Your cheque or money order should be payable to 'ETI Artwork Sales'. Prices for the artwork for this month's projects are as follows:

ETI-1402 front panel \$8.00

side panel \$3.00

pc board \$5.00

ETI-173 front panel \$4.13

pc board \$4.60

ETI-345 pc board \$3.15

You might also care to know that almost every pc board (and most front panels) ever published by ETI may be obtained from:

All Electronic Components

118 Lonsdale St

Melbourne, Vic 3000

RCS Radio

651 Forest Rd

Bexley, NSW 2207

For pc boards produced in recent years, the following suppliers either keep stocks on hand or can supply to order:

Acetronics

112 Robertson Rd

Bass Hill, NSW 2197

(02)645-1241

Jaetronics

58 Appian Drive

St Albans, Vic 3021

Jaycar

117 York St

Sydney, NSW 2000

Jemal Products

PO Box 168

Victoria Park, WA 6100

Mini Tech

PO Box 9194

Auckland, NZ

Rod Irving Electronics

425 High St

Northcote, Vic 3070

BOOKS OF SPECIAL INTEREST . . .

computer hardware and techniques

ALMOST EVERYBODY'S PERSONAL COMPUTER BOOK

Written for the computing beginner to break the enormous barrier of jargon and mystique that seems to surround computers. With a highly readable approach, the author introduces the basic concepts and develops them into a general discussion on personal computers including choosing and caring for a PC. Also offers an introduction to BASIC programming. 160pp.

H0144Z ~~\$9.95~~ \$5.95

SECRETS OF THE COMMODORE 64

A beginner's guide to the C64 with masses of useful information and programming tips as well as describing how to get the best from the powerful sound and graphics facilities. Includes two useful chapters on machine code. 109pp.

J0297B ~~\$9.95~~ \$5.95

AN INTRODUCTION TO MSX BASIC

For those wanting to learn to program, Microsoft Extended (MSX) Basic offers a powerful and flexible version of the most popular computing language. This comprehensive introduction starts with the basics and progresses by stages to more advanced programming techniques and includes coverage of advanced multicolour, sprite graphics, and the programmable sound generator. 88pp.

K0047P \$6.95

INSTANT PROGRAMMING ON YOUR SEGA SC3000 COMPUTER

Spiral-bound for easy use, this is THE Sega SC3000 beginner's book! In carefully explained, easy to follow steps, it covers the function of each key and all of the commands needed for super fast mastery of BASIC programming. This is a book for do-ers: The second part of the book teaches the real art of programming with plenty of examples and subroutines. 84pp.

K0051P \$12.95

THE BEST VIC/COMMODORE SOFTWARE

Trying to find the most suitable software for personal computers can be frustrating. The editors of Consumer Guide have compiled comprehensive reviews of VIC 20 and Commodore 64 programs based on ratings by user groups; further evaluation is given by the editors and Commodore software experts Jim and Ellen Strasma. Each review describes the program's purpose and features, detailing both the good points and bad. Each program has been rated for ease of use, clarity of written and on-screen instructions, and overall performance. The program's price, publisher, format and hardware requirements are also included. The reviews are presented in sets by topic: Word Processing, Business, Home, Education, Networking, Strategy Games, Arcade Games and Programming Aids. Spiral bound, 192pp.

K0052G ~~\$9.50~~ \$4.95

THE BEST APPLE SOFTWARE

Trying to find the most suitable software for personal computers can be frustrating. The editors of Consumer Guide have compiled comprehensive reviews of Apple II, II Plus and IIe programs based on ratings by user groups; further evaluation is given by the editors and Apple software expert Roe Adams. Each review describes the program's purpose and features, detailing both the good points and bad. Each program has been rated for ease of use, clarity of written and on-screen instructions, and overall performance. The program's price, publisher, format and hardware requirements are also included. The reviews are presented in sets by topic: Word Processing, Business, Home, Education, Networking, Strategy Games, Arcade Games and Programming Aids. Spiral bound, 160pp.

K0060G ~~\$9.50~~ \$5.95

SPOTLIGHT ON COMPUTER AWARENESS

An introduction to speaking confidently about how computers work, their applications, their history (from abacus to IBM) and employment prospects in computer related fields. Includes a comprehensive glossary. 84pp.

H0145P ~~\$9.95~~ \$4.95

AN INTRODUCTION TO 6502 MACHINE CODE

Starts with a general background to microprocessing and then details all of the legal 6502 instructions. Also covers the use of opcodes and gives machine specific listings and sample programs. 107pp.

K0178B ~~\$9.95~~ \$7.55

THE USER'S GUIDE TO COMMODORE 64 & VIC 20

The editors of Consumer Guide have compiled a thorough introduction to the Commodore 64 and Vic 20 computers, software and peripherals. With colour illustrations and a clearly written text, this reference will guide the newcomer through all phases of learning how to use the computer: From setting the system up, learning what each key does, expanding the system with peripherals, to buying new software. Specific exercises are included for each of the keys. Spiral bound, 80pp.

H0065G ~~\$9.50~~ \$5.95

DISCOVERING KNOWLEDGEMAN

According to prestigious Byte magazine, KnowledgeMan may be the most powerful relational DBMS currently available for microprocessors- and this is a powerful introduction! After a general overview, data management and spreadsheet capabilities are examined in eight sets of detailed lessons structured to give maximum learning benefits. 342pp.

K0086P ~~\$34.95~~ \$29.95

amateur radio dx, communications

25 SIMPLE AMATEUR BAND AERIALS

Describes how to build 25 amateur band aerials that are simple and inexpensive to construct and perform well. Projects range from the simple dipole up to a mini-rhombic. 63pp.


N0286B ~~\$9.95~~ \$5.95

THE WORLD IN MY EARS

This is THE basic manual for anyone with an active interest in shortwave listening written by Aurthur Cushen M.B.E., world-reknown authority and broadcaster. In the first section, the book covers the historical development of shortwave broadcasting and the listening hobby that grew up with it. The second section covers the practical aspects: how to start out, how to erect antennas, all about time zones, DX clubs, reporting, news sessions, etc. 204pp.

N0420C ~~\$10.95~~ \$7.95

Can't find it?

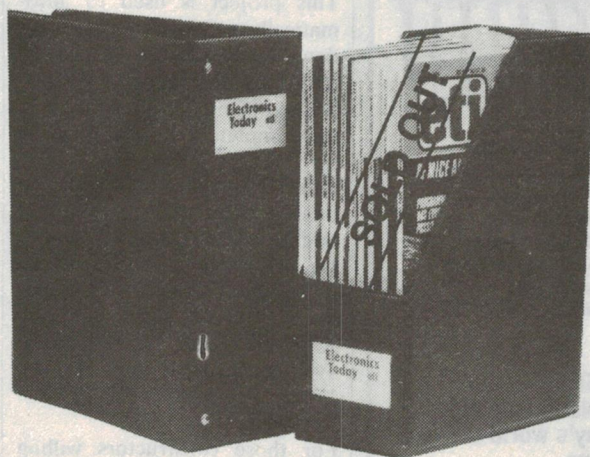

SAVE with SIX!
6 Holders — only \$37.50
6 Binders — only \$39.95

MAGAZINE BINDERS \$8.00
Ready to use binders with easy, clip-in fastener, covered in soft, decorator brown vinyl. Holds 12 issues of Electronics Today.

MAGAZINE HOLDERS \$8.00
Big, easy to assemble holders, covered in soft, decorator brown vinyl. Holds 12 issues (at least) of Electronics Today.

So easy to order —
Simply return the Freepost coupon opposite
Please allow \$2.90 per binder for postage and packing

File it!

... AT NEW LOW PRICES

AUDIO ENTHUSIAST'S HANDBOOK

Covers the record/playback curve, stylus compliance, acoustic feedback, stereo tape track standards, compensating sideways drag, amplifier power ratings and more. \$2.75 Retail, 96pp.

G0383B

Reduced to only \$2.00

CHOOSING AND USING YOUR HI-FI

Provides basic information on the technical specifications of hi-fi equipment. Offers advice on what to look for in equipment in order to obtain real high-fidelity sound and reproduction. \$4.95 Retail, 88pp.

G0385B

ONLY \$3.95

THE 6809 COMPANION

This is not a beginner's introduction, but a thorough reference and discussion of the features of the 6809 microprocessor. An excellent reference! \$6.95rrp, 88pp.

J0154B

Be quick at this price \$2.00

THE ART OF PROGRAMMING THE 1K ZX-81



The features of the ZX-81 are explained in some detail as background to programming. Here include the random number generator, graphics facilities and timer. PEEK and POKE are also explained. The well-written section on programming should make anyone with a 1K ZX-81 a whiz! \$6.75 Full Price. 86pp.

K0226B

A Rediculous \$2.00

All telephone enquiries to
Fulfilment Australia Pty. Ltd.,
(02) 816-2300

Prices subject to change without notice.

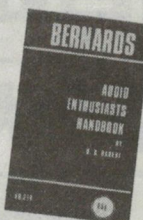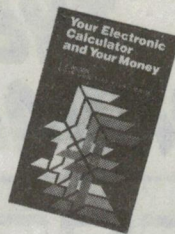

MINI-MATRIX BOARD PROJECTS

This selection of 20 useful projects to build is an excellent introduction to constructing electronic projects. Those without any experience in electronics will find it easy to read and simple to follow. \$6.75 RRP, 102pp.

D0062B

Priced to clear \$2.00

YOUR CALCULATOR AND YOUR MONEY

If you are interested in money and do even the simplest calculations, this book is a 'must.' It shows how to get the most practical use out of this efficient and powerful tool. The contents cover everything from simple arithmetic to compound interest, and depreciation. \$4.75 RRP, 174pp.

M0246B

\$2.00

FUN & GAMES WITH YOUR ELECTRONIC CALCULATOR

Calculators might be a powerful and time saving tool, but they can also be an endless source of amusement and an excellent source of relaxation, as this book shows. What do 55 snakes in a 14 foot square pit do? (You'll have to read page 6 to find out.) \$2.50 RRP, 63pp.

M0370B

\$2.00

THE BASIC BOOK OF HAM RADIO

This easy to read American Publication tells how the Amateur Radio Service works, how to obtain a Novice Licence, what to buy to get on the air and where the action is — awards, contests, public service, satellite communications, radio clubs and other ham activities. \$5.75 RRP, 128pp.

N0287R

Only \$3.95

YOUR MAIL ORDER COUPON

ELECTRONICS TODAY INTERNATIONAL

BOOK SALES

PLEASE ENCLOSE
\$3.25 per book
for postage, handling
and insurance

For airmail to Papua
New Guinea, New Zealand
Oceania and
Southeast Asia,
add \$6.00 to these charges.

BOOK TITLE	BOOK NUMBER	QTY	PRICE TOTAL

Please tick box to indicate method of payment:

Cheque*/Money Order ☐

*Please make payable to the
Federal Publishing Company Pty. Ltd.

Put your cheque or money order in an envelope with this order and send it to: Federal Direct, Freepost No. 4, P.O. Box 227, Waterloo, NSW 2017. No postage stamp required in Australia.

Mastercard ☐ American Express ☐ Bankcard ☐ ☐ Tick

☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐ Credit Card No.

(Unsigned orders cannot be accepted)

Card Expiry Date..... Signature.....

Allow up to 6 weeks for delivery

Total price of books \$
Add postge and handling \$
(\$3.25 per book)

PLUS Binders @ \$10.90 \$
(Inc P+P)

TOTAL \$

NAME:

ADDRESS:

..... POSTCODE:

TELEPHONE:

THE 1986 SECONDARY SCHOOLS

ELECTRONICS



COMPETITION



GUIDANCE FOR SCHOOLS ENTERING THE ETI ELECTRONICS COMPETITION

Peter Phillips

The aim of this article is to give those teachers and students participating in the ETI schools competition some help and ideas. It is about how to make the most out of very little with some advice on projects and purchasing.

Equipment

As money and equipment for electronics in high schools is in short supply existing equipment will need to be adapted. It may be possible to excite the P&C organisation into allowing funds to be used to buy some more suitable gear or to at least purchase a range of components and hardware. A recommended shopping list is included to give support to those approaching the P&C organisation for some funds.

The most important requirement in electronics is a supply of soldering irons. All high schools have a stock of 12 volt power supplies, and 12 volt soldering irons costing around \$10 each could be used in conjunction with these. Although suitable only for small soldering jobs, these irons offer safety and cost effectiveness. Perhaps one temperature controlled soldering station could be bought for use by the teacher. By using low voltage soldering irons the risk of the iron burning through the 240 volt lead is overcome.

The next concern is whether to use printed circuit boards. If pc boards are to be avoided, consideration could be given to either pre-etched multipurpose pcb or veroboard. Veroboard can be cut up easily into small sections for student use and is

easily adapted for a variety of designs. It has the disadvantages of requiring wire links between strips, fiddly soldering and requiring track cutting.

If the intended undertaking is likely to contain only a few items, you may like to design a 'blob' board. This consists of a pcb with a number of 10mm (or so) squares separated from each other. Students surface mount the components and the board can then be cleared afterwards for others to use.

Printed circuit board manufacture is possible, providing the necessary chemicals can be purchased. Several options are available here, the simplest being to draw the design on the board with a 'dalo' pen (pc resist pen) and to then etch it. If a sophisticated design is envisaged, a good reference is 'Making your own pc board' which appeared in ETI April 1985.

Because it is unlikely a room can be dedicated to an electronics laboratory it may be necessary to set up a number of portable 'stations'. A wooden board with the necessary items attached to it could be used and made to a size that allows its storage in a cupboard. The board might contain a few basic tools, solder and soldering iron and some sort of pcb holder

made from a bulldog clip bolted at a suitable height above the board.

Measuring equipment such as a voltmeter should be normally part of the school's stock. If teacher expertise is available a basic meter movement could be converted into an ohmmeter or an ammeter or multirange voltmeter. Alternatively, cheap multimeters could be purchased, although capabilities of the really cheap ones will be limited.

Although the items mentioned only provide a fairly crude set-up, teachers are no doubt aware of the difficulty of doing advanced work with a class whose knowledge of the field is minimal. Any undertaking in either the competition or just as an interest group will most likely be low key, perhaps with an emphasis on mechanics as well. If a highly motivated group of skilled children are participating then the basic items discussed may need to be augmented.

Some ideas for projects

As a TAFE teacher of industrial electronics, I have had contact with kids attending link courses, as well as in purchasing and setting up for electronics courses. A point worth mentioning is that an interested teacher may like to contact the local TAFE college for ideas. Not all colleges run electronics courses, but those that do would no doubt be only too pleased to show the set-up they have and to discuss ideas. In my experience a lot can be done with limited equipment providing the teacher is well organised and prepared.

Typical popular projects are door chimes, flashing light indicators, continuity testers or projects based on the 555 timer. These projects are generally built on veroboard and run from a 9 volt battery. Other ideas that spring to mind are a burglar alarm system, a basic electronic music instrument that uses a number of 555 oscillators tuned to give a scale, weather monitoring equipment such as wind direction, temperature and rainfall indicators. One TAFE college I know of actually set up a model train which provided lots of reasons for some attached electronics.

The ETI Simple Projects book is also an invaluable source. It has been sent to schools participating in the competition, but is also available from newsagents.

Another possibility is interfacing with a computer. The actual electronics need only be simple, in the form of an interface

between, for example, some lights and the computer's outputs. Naturally the interface deals with TTL (5 volt logic) and that may need to be the province of the teacher.

Small dc electric motors are cheap and lots of imaginative possibilities arise. The use of simple optocoupling devices, perhaps to count items passing a point, or to detect the presence of an object can be incorporated. At a recent exhibition, a TAFE college set up a tube that had a number of steel balls rolling from one end to the other. Once all the balls had passed one way, the tube was tilted with a motor and all the balls then flowed the other way, controlled with a simple electromechanical gate. The balls were counted with an opto device and the number displayed on a fabricated display using incandescent lights.

Another possibility is some form of robot. There is no need to have it remote or computer controlled, trailing wires are sufficient.

Other projects might include actual test equipment or equipment to enhance other school activities, (eg, an electronic stop watch for sport involving a conventional but large clock face and a motor to drive the hands; an electronic scoring system using large digits is also a possibility).

In summary, ideas for projects are limitless. By using simple schemes, success is more likely.

Where to buy

It is difficult to generalise on where to buy throughout Australia. One point worth stressing at the outset is the power of bulk buying. Most retailers offer some form of discounting for



wholesale purchasing, although this will imply a minimum number per item and often a minimum overall value. The Dick Smith chain offers bulk purchasing through DS Distributors (not Dick Smith, but DS Distributors) from its centre in Sydney. Information on this can be obtained from any Dick Smith catalogue.

Rod Irving Electronics in Melbourne and Altronics in Perth, offer a similar deal, as does George Brown (Protronics in WA and SA). Note that George Brown in Sydney offers a 30 day account specially for high schools, alleviating the need for cash transactions. The account will be sent to the principal, whose permission in the first place will have been sought.

Government stores do not generally stock much in the way of electronic items. However, examination of the government contracts may show deals that are cost effective. Care is required in selecting a firm from which to purchase. Some firms offer high quality, relatively expensive components that represent good value if quality is important. A firm that deals in this type of good is RS Components. Its catalogue is a model and the range offered very extensive. It also provides good literature backup, but costs are often more than other outlets'.

GREAT PRIZES FOR YOUR SCHOOL

\$2000 worth of electronic equipment from Dick Smith Electronics to the winning school group.

25 soldering irons from Scope and **25 solder packs from Multi Core Solders** to the first 25 schools to register in the competition and go on to complete it.

15 jumbo components bags from Dick Smith Electronics:

Congratulations to the first 15 schools which registered including Kogarah Marist High, NSW, Tarooma High, Tasmania and Mawson High, South Australia.

Throughout the year ETI will invite other electronics suppliers to join in and offer other great prizes.

HOW TO ENTER

Groups representing their schools should submit the attached registration form which itself brings no obligation. Entry forms and suggested project designs will be forwarded to the groups on receipt of the registration form. Entrants are required to build an electronic device to their own or one of our designs and write a report on its operation, construction (and design) and the group's involvement. The device and report must be lodged with us by 15 September, 1986. State, Territory and New Zealand finalists will be announced on 19 September, 1986. The competition winner will be announced 16 September, 1986.

REGISTRATION FORM

COMPLETE AND SEND TO "SECONDARY SCHOOLS COMPETITION", ELECTRONICS TODAY INTERNATIONAL, PO BOX 227, WATERLOO, NSW 2017.

SCHOOL

ADDRESS

GROUP LEADER'S NAME

SCIENCE TEACHER'S NAME

DOES YOUR SCHOOL ALREADY HAVE AN ELECTRONICS GROUP OR COURSE?

Often, convenience to a store is important. After all, spending money by driving or telephoning all over the place to save a few cents is pointless.

The best advice is to try for bulk purchases if possible. No tax is payable and components and hardware can often be had for as low as half the cost of retail prices. The temperature controlled soldering iron station available from DS Distributors is much less than the advertised cost from the retail outlets, providing a number are bought. If a wholesale shopping list costing around \$200 was presented to the P&C association, its acceptance could be aided with the information that this amount represents around \$400 worth of retail components but is contingent on purchasing a minimum value of components.

Other good sources are disposals stores, car wreckers and the like. I have often purchased remnants from industry, such as pcb cutoffs, end of production throwaways and so on. A phone call to large manufacturers often brings to light incredible bargains. Typical of this was a purchase I once made from STC at Liverpool (NSW). By buying a number of superseded plug-in printed circuit cards for \$1 each, I obtained 50 diodes, 15 transistors, 100 resistors, 30 capacitors and 2 relays from each card. The desoldering exercise could well be undertaken by students and lots of usable components obtained.

Recommended shopping list

- Resistors, 100 each value, in the decades of x1, x10, x100, x1k, x10k, x100k: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8 and 8.2.
- Soldering irons and solder.
- Small long nose pliers, side cutters and screwdrivers.
- Desoldering wick or a desoldering tool.
- One or more multimeters.
- Printed circuit board and chemicals for preparation and etching.
- Storage cabinet for the resistors.
- Wire, connectors, plastic sleeving.
- Miscellaneous components, eg, capacitors, transistors, integrated circuits to suit planned projects.

Purchasing outlets

The following firms are representative of those that supply the sort of components you will need. Not all the firms are found in all states, and many others are not listed due to the lack of awareness of their existence by the author. This particularly applies to firms outside NSW. Those enterprises not listed may well offer deals superior to the following.

- George Brown:** (Protronics in SA and WA.) This firm deals in wholesale purchasing in a wide range of components.
- Dick Smith:** The retail outlets are well known and offer most parts required by hobbyists. The wholesale division called DS Distributors is only situated in Sydney.
- Rod Irving Electronics:** Based in Melbourne.
- Pre-Pak Electronics:** Offers a mail order service.
- Jaycar Electronics:** Stocks a wide range of kits and components. Has an agency in Brisbane.
- Ritronics:** Minimum account order of \$50, based in Clayton, Victoria.
- Emona Instruments:** Specialises in educational equipment rather than components. Head office in Sydney, agencies all states. May have low price test equipment suitable for project building.
- Circuit Components:** Based in Bexley, (Sydney), this firm specialises in printed circuit board chemicals, drafting aids and photosensitive products.
- Altronics:** Based in Perth, offers a wide range of components, similar to Dick Smith.
- RS Components:** Deals in mail order components, the outlets in Australia are from the parent company in England.



TELECOMMUNICATIONS AUSTRALIAN STYLE ADAPTOR CABLE
 • Australian socket to plug/socket
 • Length 10 metres
 Cat. Y16015 Normally \$15.95
SPECIAL, ONLY \$12.75



TELEPHONE ADAPTOR
 • Australian plug to U.S. socket
 • Length 10cm
 • Cream colour cable
 Cat. Y16026 Normally \$6.95
SPECIAL, ONLY \$5.55



TELEPHONE CURL CORD
 • U.S. plug to U.S. plug
 • Replacement hand set cord
 • Length 4.5 metres
 • Colours: cream, dark brown
 Cat. Y16022 Normally \$7.95
SPECIAL, ONLY \$6.35



TELEPHONE EXTENSION CABLE
 • U.S. plug to U.S. socket
 • Length 10 metres
 Cat. Y16024 Normally \$8.95
SPECIAL, ONLY \$7.15




TELEPHONE EXTENSION CABLE
 • U.S. plug to 2 U.S. sockets
 • Length 10 metres
 Cat. Y16028 Normally \$10.95
SPECIAL, ONLY \$8.75



TELECOMMUNICATIONS AUSTRALIAN TO U.S. ADAPTOR CABLE
 • Australian socket to U.S. plug
 • Length 5 metres
 Cat. Y16017 Normally \$7.95
SPECIAL, ONLY \$6.35



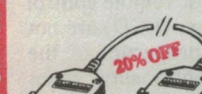INLINE SWITCHING BOX
 • 25 pin "D" plug to 25 pin "D" socket (RS232)
 • DIP switches allow easy switching of internal wiring.
 Cat. P Normally \$32.95
SPECIAL, ONLY \$26.35



COMPUTER LEAD
 • 25 pin "D" plug to 25 pin "D" plug (RS232) DIP switches in each plug allow many combinations of internal wiring, making this a truly universal lead.
 • Mylar shielding against RF interference.
 • Length 2 metres.
 Cat. P19031 Normally \$59.95
SPECIAL, ONLY \$47.95



IC SPECIALS!

	1-9	10+	100+
4116	\$1.80	\$1.70	\$1.60
4164	\$2.95	\$2.75	\$2.50
2716	\$5.90	\$5.50	\$5.50
2732	\$6.25	\$5.95	\$5.50
2764	\$6.25	\$5.95	\$5.50
27128	\$6.95	\$6.50	\$6.25
6116	\$2.95	\$2.75	\$2.50
41256	\$8.95	\$8.50	\$8.00
6284	\$6.50	\$5.50	\$5.25
27256	\$11.50	\$10.50	\$10.00

WORLD MODEM CHIP
 Cat. U21614 Normally \$49.50
Save \$20, SPECIAL \$29.50




RITRON MULTI PURPOSE MODEM
 The RITRON Multi Purpose Modem has all the features you require...
 • CCITT V21 300 Baud Full duplex
 • CCITT V23 1200/75
 • Bell 103 300 Full duplex
 • Bell 202 1200 Half duplex
 • Auto answer, auto disconnect.
 Telecom Approval No. C84/37/1134
 Cat. X19103 Normally \$399
SPECIAL \$299
 (Limited stock, so be quick!)



DELUXE 5 1/4" DISK STORAGE UNIT
 Features...
 • Diskette fan display system elevates the disks for easy identification and access.
 • Lockable lid (2 keys supplied)
 • Clear smoked plastic lid
 • High impact plastic base
 • 45 diskette capacity
 Cat. C16050 Normally \$49.95
SUPER SPECIAL, \$24.95



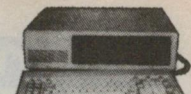COMPUTER PAPER
 Quality paper at a low price! 2,500 sheets of 11 x 9 1/2", 60 gsm bond paper.
 Cat. C21001 Normally \$44.95
SPECIAL \$37.95



IBM* COMPATIBLES
 from \$899*
 Incredible deals to suit everyone including special package deals!
 *256K RAM, single drive, graphics, disk controller and printer cards.
 IBM is a registered trademark.

256K RAM: Colour Graphics, Disk Controller Card, 1 parallel port, 2 disk drives and 3 months warranty. only \$1,395

640K RAM: Colour graphics, Multifunction Card, Disk Controller Card, 2 serial and 1 parallel ports, 2 disk drives and 3 months warranty. only \$1,495

256K PACKAGE DEAL: Includes Colour Graphics Card, Multifunction Card, Disk Controller Card, 2 serial and 1 parallel ports. A 120 C.P.S. printer and a monochrome monitor and 3 months warranty! only \$1,950

640K PACKAGE DEAL: Includes Colour Graphics Card, Multifunction Card, Disk Controller Card, 2 serial and 1 parallel ports. A 120 C.P.S. printer, a monochrome monitor and 3 months warranty! only \$2,050
 *IBM is a registered trademark.



RS232 MINI PATCH BOX
 • Interface RS232 devices
 • With male to female 25 pin inputs
 • 25 leads with tinned end supplied
 • Complete with instructions
 Cat. X15654 Normally \$25.95
SPECIAL, ONLY \$20.75



RS232 GENDER CHANGERS
 Saves modifying or replacing non-mating RS232 cables by changing from male to female to male. All 25 pins wired straight through
 Male to male: Cat. X15650
 Female to female: Cat. X15652
 Normally \$19.95
SPECIAL, ONLY \$15.95



TELECOMMUNICATION PLUG TO 2 SOCKETS.
 Ideal for modem connections.
 Cat. Y16014 Normally \$12.95
SPECIAL, ONLY \$10.35



RS232 DATA SWITCH WITH TESTER
 • 25 pin RS232 "D" connectors 2 in, 1 out or 1 in, 2 out.
 • Ideal for 2 computers to one peripheral or 1 computer to 2 peripherals.
 • No power required.
 • Six dual coloured LED indicators showing certain flow status.
 T.D. Transmit Data
 R.D. Receive Data
 R.T.S. Request To Send
 C.T.S. Clear To Send
 D.S.R. Data Set Ready
 D.T.R. Data Terminal Ready
 • Housed in heavy duty metal cabinet.
 • Size: 200(W)x68(H)x150(D)mm
 Cat. X19110 Normally \$149
SPECIAL, ONLY \$129

CENTRONICS DATA SWITCH
 • 36 pin gold plated female Centronics connectors.
 • All other specs as for RS232 Data Switch with Tester.
 Cat. X19115 Normally \$169
SPECIAL, ONLY \$149



IBM COMPATIBLE CARDS
 NEW MOTHER BOARDS!
 XT compatible mother boards, 8 slots, room for 256K RAM
 Cat. X18020 \$295

GAMES ADAPTOR CARD
 Features 2 joystick ports.
 Cat. X18019 \$49

MULTIFUNCTION CARD
 (384K RAM) Parallel, serial and game port. Plus battery backup clock.
 Cat. X18013 \$329

DISK CONTROLLER CARD
 Controls 2 slimline drives
 Cat. X18005 \$89

HIGH RESOLUTION MONOCHROME GRAPHICS CARD
 Give your IBM real graphics capability.
 Cat. X18007 \$249

512K RAM CARD
 Including RAM Cat. X18015 \$299
 Excluding RAM Cat. X18016 \$129



APPLE* COMPATIBLE CARDS
 Printer Card Cat. X17029 \$89
 Drive Card Cat. X17019 \$95
 80 Column Card Cat. X17025 \$109
 Speech Card Cat. X17009 \$69
 Music Card Cat. X17011 \$99
 Super Serial Cat. X17035 \$129
 RGB Card Cat. X17039 \$79



JOYSTICK FOR IBM
 Features Selectable "Spring centering" or "free floating". Electrical trim adjustments on both axis. 360 degree cursor control
 Cat. C14205 Normally \$39.95
SPECIAL, ONLY \$34.95



APPLE JOYSTICKS
 Ideal for games or word processing. Fits most 6502 "compatible" computers.
 Cat. C14200 Normally \$34.95
SPECIAL, ONLY \$29.95



20 M/BYTE HARD DISK DRIVE FOR IBM* AND COMPATIBLES
 Includes disk controller card.
 Cat. X20010 \$1,250
 *IBM is a registered trademark.



APPLE* COMPATIBLE SLIMLINE DISK DRIVES
 Japanese Chiron mechanism, compatible with 2E and 2 plus.
 Cat. X19910 Only \$249
 Japanese Chiron mechanism, Cat. X19901 Normally \$225
NOW \$175
 (*Apple is a registered trademark.)



MITSUBISHI DISK DRIVES
MF353 (3 1/2" DRIVE)
 Double sided, double density, 1 M/Byte unformatted, 80 track per side.
 Cat. C11953 \$280
MF351
 3 1/2" Standard size disk drive. Single sided, double density.
 Cat. C11921 \$225

M2896-63
 Slimline 8" Disk Drive, Double sided Density No AC power required. 3ms track to track, 1.5 Mbytes unformatted, 77 track side 10s/su 10 bit soft error rate.
 Cat. C11916 \$550
 Case & Power Supply to suit Cat. X11022 \$159

M4854
 Slimline 5 1/4" disk drive. Double sided, double density, 96 track/inch, 9621 bit/inch, 1.6Mbyte unformatted 3ms track to track access, 77 track/side.
 Cat. C11904 \$350
 Case & Power Supply to suit Cat. X11011 \$109

M4853
 Slimline 5 1/4" disk drive. Double sided, double density, 1 Mbyte unformatted, 3ms track to track, 80 track/side, 5922 bits/inch.
 Cat. C11903 \$260

M4851
 Slimline 5 1/4" disk drive. Double sided, double density 500K unformatted, 40 track/side. Steel band drive system.
 Cat. C11901 \$219
 Case & Power Supply to suit Cat. X11011 \$109

M4855
 Slimline 5 1/4" disk drive, double sided, double density, 96 track/inch. 2.0 Mbytes unformatted.
 Cat. C11905 \$385



5 1/4" FLOPPY DISK SPECIALS!
 All prices 10 disk boxes!

	1-9	10+
XIDEX S/S D/D	\$29.95	\$29.95
Cat. C12401		
D/S D/D	\$38.95	\$36.95
Cat. C12410		
High Density Cat. C12520	\$125	
VERBATIM DATALIFE S/S D/D	\$27.95	\$26.95
Cat. C12501		
D/S D/D	\$34.95	\$32.95
Cat. C12504		
VERBATIM VALULIFE S/S D/D	\$24.95	\$22.95
Cat. C12421		
D/S D/D	\$29.95	\$25.95
Cat. C12425		

3 1/2" DISK SPECIALS
 Verbatim S/S Cat. C12610 \$69.95
 Verbatim S/S Cat. C12612 \$89.95
 Xidex S/S Cat. C12600 \$65.95
 Xidex D/S Cat. C12602 \$89.95

NEED HIGH DENSITY DISKS FOR YOUR IBM AT?
 "Buy your High Density disks at below recommended retail prices from Rod Irving Electronics and SAVE!!"
 R.R.P. \$113 Our Price \$99.95



CIS 5 1/4" D/S DISKS
 100% certified and error free guaranteed! Where else can you get 100% guaranteed D/S D/D disks for just \$24.95?!!
 Cat. C12440 Only \$24.95
 "Less 10% for 10 or more!!"



SUPERB KAITEC 180 C.P.S. PRINTER
 Epson FX80 compatible, standard 80 column dot matrix, Near Letter Quality mode, and 3K buffer!
 Cat. C20020 Normally \$525
SPECIAL, ONLY \$479



PHOENIX 5
 Suits Apple, Commodore, even your VCR!
 • Pal and R.G.B
 • Normal Resolution
 • 13" CRT Dot Pitch 0.65mm
 • Horiz. Resol. 320 TV lines
 • Vert. Resol. 560 TV lines
 • Display Characters 1,000 Ch (40x25)
 • 16 Colours (Pal)
 • Green tint display
 Cat. X14522 Normally \$499
SPECIAL ONLY \$379



RITRON 2 MONITORS
 Stylish, swivel base monitor, available in amber or green.
 Green Cat. X14506 Normally \$215
 Amber Cat. X14508 Normally \$219
SPECIAL, ONLY \$199



ROD IRVING ELECTRONICS
 425 High Street, NORTH-COTE, 3070 VICTORIA, AUSTRALIA
 Phone (03) 489 8866
 48 A Beckett St, MELBOURNE, 3000 VICTORIA, AUSTRALIA
 Ph. (03) 663 6151
 Mail Order and correspondence: P.O. Box 620, CLAYTON 3168
 TELEX: AA 151938



MAIL ORDER HOTLINE
 (03) 543 7877
 (2 lines)

POSTAGE RATES

\$1-\$9.99	\$2.00
\$10-\$24.99	\$3.00
\$25-\$49.99	\$4.00
\$50-\$99.99	\$5.00
\$100-\$199	\$7.50
\$200-\$499	\$10.00
\$500 plus	\$12.50

 This is for basic postage only. Come Road freight, bulky and fragile items will be charged at different rates.
 Certified Post for orders over \$100 included "free!"
 Registered Post for orders over \$200 included "free!"
 All sales tax exempt orders and wholesale inquiries to RITRONIC'S WHOLESALE, 56 Renner Rd., Clayton Phone (03) 543 2166
 Errors and Omissions Excepted.

LIGHT AND ELECTRONICS

Peter Phillips

IT IS FAIRLY common knowledge that electricity produces light just as light can generate electricity. However, generating electricity in this way has, to date, not been developed much beyond the use of solar cells. Even in the most cost effective cases, other means of generating electricity are more attractive, limiting the use of solar energy to low power applications such as from powering calculators to trickle charging batteries. But the use of light in conjunction with electricity is far more common, in ways the average user may not even be aware of.

Opto-electronics is the term used to categorise the theory behind those devices that use light in combination with electricity. As usual, our coverage is brief but informative; enough to whet your appetite for more, not too much to confuse the issue.

The facts of light

Around the turn of the century, arguments raged as to the nature of light. Was light composed of 'particles', or was it a form of wave energy? Evidence abounded to support both theories, ultimately resulting in a 'yes' verdict for both forms. The wave theory suggests that light is an electromagnetic vibration, a rapid succession of pulses, similar to a radio transmission but at a much higher frequency. The particle theory, developed by Einstein, assumes that light is a stream of small particles, now known as photons. The particle theory ushered in quantum physics, and provided insight to the atom, thus introducing the world to the atomic age. This theory identifies the photon as a quantum of energy, proportional to the frequency of the wave. Both these theories are inconsistent with each other but they are nevertheless both applied: light is considered a wave to explain certain phenomena and considered as

particles where the wave theory falls down. Confused? So are many scientists, and one can only speculate where it will all end.

By using both theories, all the phenomena of light can be explained. For our purposes, it is sufficient to recognise that light is a form of energy, with a wavelength depending on the colour of the light. A wavelength is the distance between two equal points of the wave, as shown in Figure 1. A relationship exists between the number of cycles occurring each second to the speed the wave travels. The velocity of light, as all school students know, is around 300,000 kilometres per second. Wavelength is determined by dividing the velocity with the frequency.

It is common to define each colour by its wavelength rather than its frequency, giving rise to terms such as the Angstrom. Figure 2 shows how the spectrum is portrayed as a series of very short wavelengths of electromagnetic energy, from red as the longest to violet the shortest. Thus, red light has the lowest frequency and becomes infrared once its frequency falls below that which the eye can perceive. Ultraviolet light is at the other end of the spectrum and green somewhere in the middle. As a further illustration, Figure 2b shows the entire frequency spectrum, depicting the relative position of each subgroup of uses. Light occupies frequencies around one thousand million million cycles per second (10^{15} Hz); sound extends up to only 20,000 Hz.

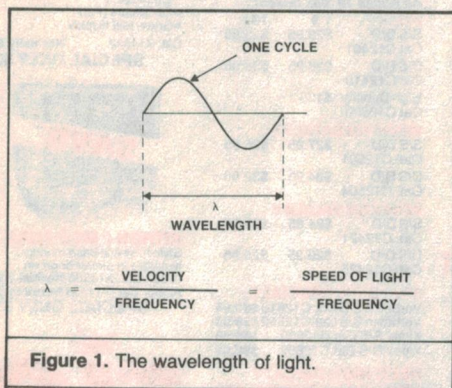


Figure 1. The wavelength of light.

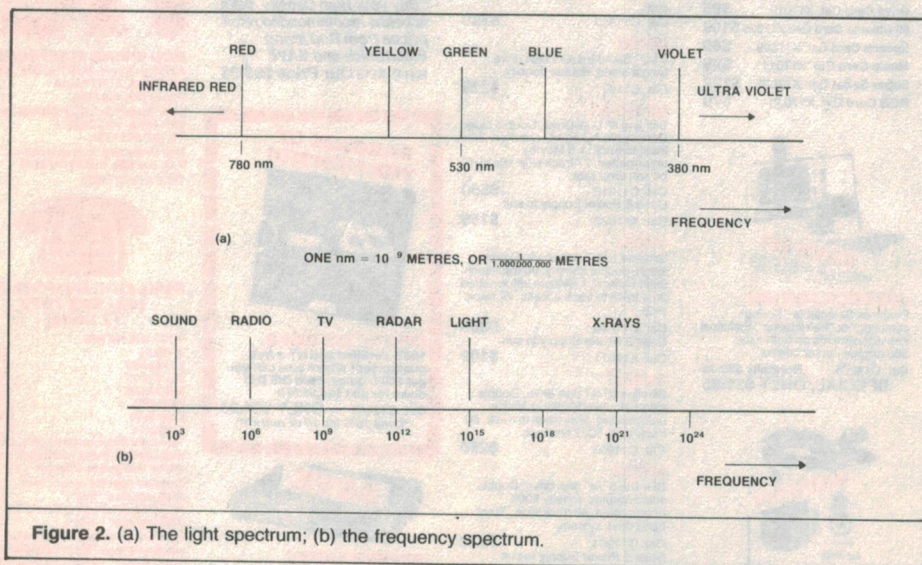


Figure 2. (a) The light spectrum; (b) the frequency spectrum.

An overview

Opto-electronic devices can be grouped into two categories: those that produce light and those that react to light. The light emitting diode (LED) is the most common light producing device and many applications for these exist. LEDs often form the basis for displays, as light sources in conjunction with other light operated devices, and are currently used in most domestic remote control units. Liquid crystal displays (LCD) are not light producers, but the properties of the chemicals within the assembly allow areas to appear dark or light according to control voltages applied to sections of the display.

Another common display that produces light is the cathode ray tube (CRT). In the

**Electronics
Today**


**POST
FREE**

No stamp required
if posted
in Australia

FREEPOST No. 4
The Federal Publishing Company Pty Ltd
P.O. Box 227,
Waterloo, NSW 2017

SAVE OVER \$5.00 – SUBSCRIBE FOR 2 YEARS

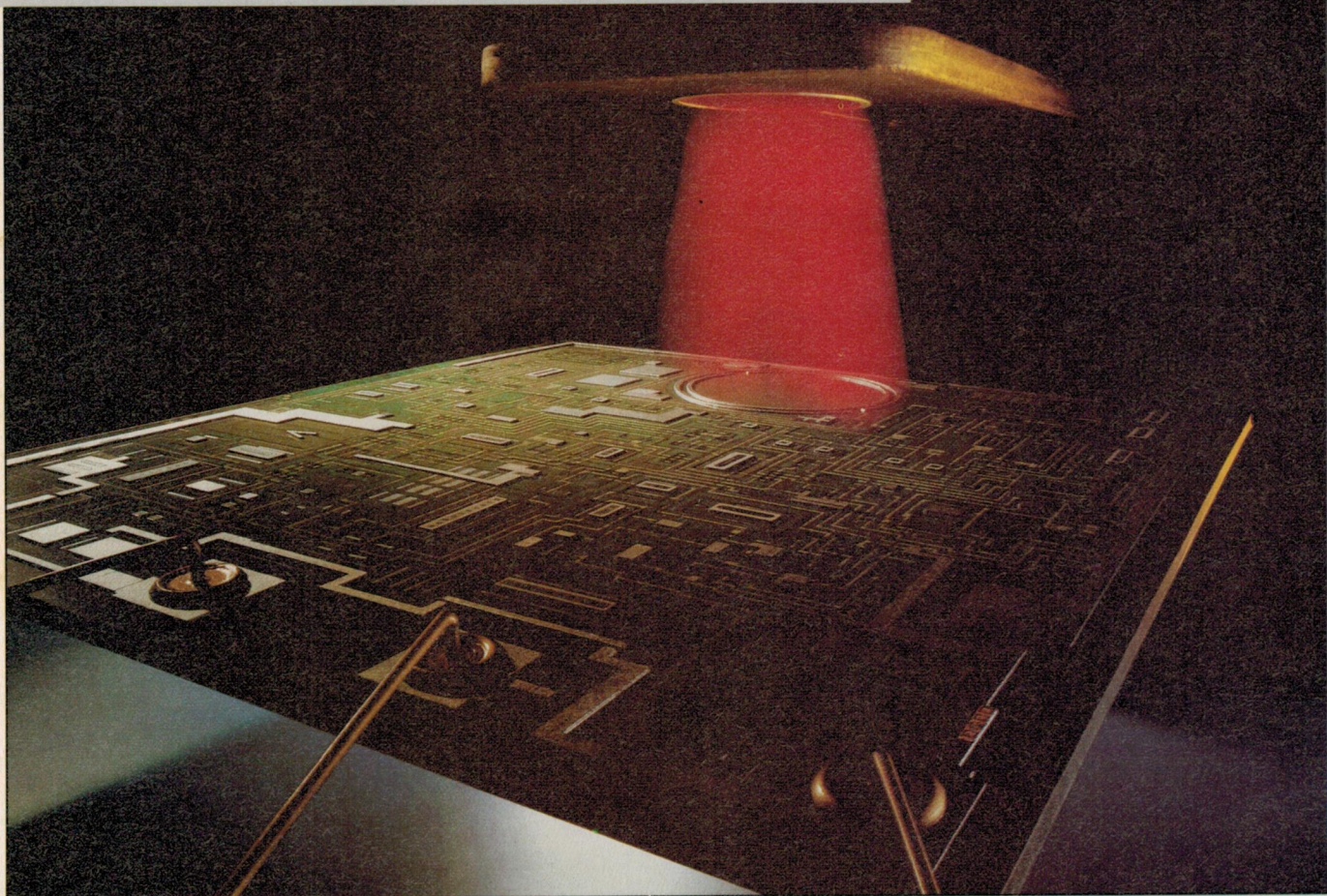The combination of light and electricity is a marriage of two abstract forms of energy. Both operate at the highest speeds known in nature, and together produce effects and functions as exciting as any technology can offer. The field of opto-electronics is probably still in its infancy and may well constitute a future technology.



Photograph courtesy of VSI Electronics Australia.

CRT, an electron beam is used to excite a phosphor-coated screen. When an area is bombarded with electrons, that section will glow a different colour according to the various phosphors.

Devices that react to light vary from those that produce a voltage when struck by light to devices whose electrical properties alter as a result of incident illumination. Solar cells, otherwise known as photovoltaic cells are the most common examples of a device that produces electrical energy from light. Devices whose electrical properties alter as a result of exposure to a light source include light dependent resistors (LDRs), photodiodes, phototransistors, even photo-FETs. These components are

used to allow a circuit to respond in some way to a light source, for example pulsed light often used to transmit information.

The use of fibre-optics is another area of great interest to those wishing to transmit information. This technology uses optical fibres to conduct light in much the same way as wire conducts an electric current. A light source at one end is acted upon to pulse the light at high speeds in such a way that information in the form of a digital pulse train is produced. Sensors at the other end or at a number of points along the way respond to the light, and circuitry to amplify and decode the information is used to regain the original information. Lasers are becoming more widely used, with applications ranging

from exotic light shows to surgery, warfare and data transmitting uses. Compact disc players use a laser in conjunction with a photosensitive detector so there is no physical contact with the disc as information on the disc is read.

Having summarised the topic, it now remains to examine these devices and to show their applications. Opto components are often very cheap, and many otherwise impossible tasks can be performed easily by the combination of light producing and light sensitive devices.

Light sources

The invention of the electric light in the latter half of the 19th century forced the re-►

Fluke. First Family of DMMs.



When accuracy, performance and value are important, professionals the world over look to Fluke — the first family of DMMs.

Reliable Fluke-quality 3½- or 4½-digit DMMs fit every need — from design engineering to industrial troubleshooting.

There's the low-cost 70 Series — the most DMM you can get for the money. The tough 20 Series — totally sealed and built to survive the dirtiest, grimeiest, roughest jobs. The reliable 8020B Series — made to withstand the rigors of the field service environment. The precise 8060A Series — the most powerful and complete test and measurement system available in a hand-held package. And, of course, the versatile Bench/Portables that carry on the Fluke tradition for precision and durability in lab-quality bench instruments.

Fluke comes in first again with the world's largest selection of quality accessories to help extend the capabilities of your DMM even further.

There's no need to look anywhere else. Uncompromising Fluke design and leading edge technology are the reasons why attempts at imitation will never fool the millions of professionals that accept nothing less than a Fluke.

FROM THE WORLD LEADER
IN DIGITAL MULTIMETERS.



ELMEASCO **Instruments Pty. Ltd.**

N.S.W. 15 McDonald St, Mortlake. Tel: (02) 736 2888
VIC. 12 Maroondah Hwy, Ringwood. Tel: (03) 879 2322
QLD. 243 Milton Rd, Milton. Tel: (07) 369 8688
S.A. 241 Churchill Rd, Prospect. Tel: (08) 344 9000
W.A. 46-48 Kings Pk Rd, West Perth. Tel: (09) 481 1500

Talk to your local distributor about Fluke

• **A.C.T.** Actec Pty Ltd (062) 80 6576 • George Brown 80 4355 • **N.S.W.** Ames Agency 699 4524 • George Brown (02) 519 5855 Newcastle 69 6399 • Bryan Catt Industries 526 2222 • Collier Tools 763 1888 • D.G.E. Systems (049) 69 1625 • Davred Electronics 267 1385 • W.F. Dixon (049) 61 5628 • Macelec (042) 29 1455 Ebson 707 2111 • Selectro Parts 708 3244 • Geoff Woods 810 6845 • **N. TERRITORY** Thew & McCann (089) 84 4999
• **QUEENSLAND** L.E. Boughen 369 1277 • Colourview Wholesale 275 3188 • Fred Hoe & Sons 277 4311 • Nortek (077) 79 8600 • St Lucia Electronics 52 7466 • Selectro Parts (Qld) 394 2422 • **S. AUSTRALIA** Prototronics 212 3111 • Trio Electrix 212 6235 • Redarc Electronics 278 7488 • A.W.M. Wholesale • **TASMANIA** George Harvey (03) 31 6533, (002) 34 2233 • **VICTORIA** A.W.M. Electrical Wholesale • Radio Parts 329 7888 • G.B. Telespares 328 3371 • Browntronic 419 3986 • R.K.B. Agency 82 7704 • A.J. Ferguson 347 6688 • SIRS Sales (052) 78 1251 • Mektronics 690 4593 • **W. AUSTRALIA** Atkins Carlisle 321 0101 • Dobbie Instruments 276 8888 • Cairns Instrument Services 325 3144 • Willis Trading 470 1118

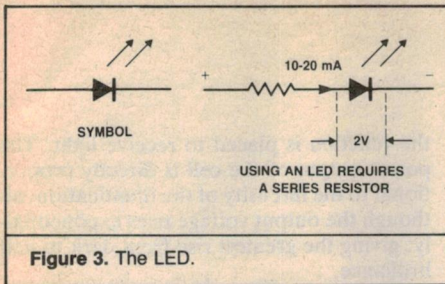


Figure 3. The LED.

placement of arc lamps that had been used previously. From an electronics standpoint, another eighty or so years had to elapse before the discovery of a light source in a solid state device. Certainly there were other methods of producing light: neon indicators, fluorescent tubes, phosphorescent indicators, but none so successful as the LED.

Light emitting diodes are semiconductor diodes emitting electromagnetic radiation when operated in the forward direction. The wavelength of the emitted radiation depends on the semiconductor material used and its doping. GaAsP LEDs (gallium arsenide phosphide LEDs) emit red light, GaP LEDs (gallium phosphide LEDs) produce green or yellow light, and GaAs diodes (gallium arsenide IRED) emit in the infrared region of the spectrum. The basis of the LED, as any other diode, is a pn junction. However, the energy given off by the junction under current-carrying conditions in a conventional silicon or germanium diode is largely in the form of heat. By using the various materials mentioned, a diode still results, but one that dissipates the energy in the form of light.

Figure 3 shows some of the various types of LEDs available. Apart from the conventional 5mm red LEDs so commonly employed, the range extends over LEDs of various shapes and sizes: dual LEDs, high brightness types, focused LEDs, bezel mounted varieties, and so on.

It is important to know some basic electrical characteristics of these easy to use devices. The current through the diode must be limited to around 10 to 20mA, depending on the size of the LED. The voltage drop across the device is approximately 2

volts, and the reverse breakover voltage is a very low value, about 3 to 5 volts. Thus, LEDs are generally used in dc circuits and require special consideration where ac is involved. Very little heat is generated allowing high packing densities, and their life is generally in the order of 100,000 hours.

Most TTL digital chips can drive an LED directly, allowing their use as state indicators. Dual LEDs, incorporating a green and a red LED in the one package are ideal to display up to three states: off, green and red. Flashing LEDs which require 5 volts for operation contain an IC within the package. These make excellent warning indicators such as a simple deterrent on a car dashboard. High intensity or prefocused LEDs are used as optical data transmitters, in conjunction with a light sensitive detector. Infrared LEDs (IREDs) are found in most remote control units. Because they emit energy just below the visible spectrum, many manufacturers include a conventional LED to indicate that the unit is transmitting.

Displays

Displays incorporating LEDs or LCD modules are as common as mud, and offer features that permit communication between a device and the user. LCD displays are more complex than the LED types, but operate with extremely low power consumption. A disadvantage of LCD displays is the need for an external light source. However, under bright light conditions, LED types become harder to read making the LCD device the better choice. LCD displays can include a wide range of characters, even pictures, with colour being incorporated as required. Solid state screens are usually LCD, and many car manufacturers are including dashboard instrumentation based on specially designed LCD panels.

Because of its relative simplicity, the LED display is best suited to the hobbyist. In general, seven segments are employed,

some including a decimal point, as shown in Figure 4. The segments are usually labelled from a to g, and special decoder/driver digital ICs are used to allow the display to show numbers and a limited range of letters. Reference to most texts on digital electronics will provide information on how to use these devices. One point to note is the polarity of the power supply to the display. Some varieties connect all the anodes to a common point, others the cathodes. The common anode types would require the positive supply to this pin; the device driving the individual segments would need to provide a path to the negative terminal. The opposite polarity would be used for a common cathode type.

Bar graph indicators are often incorporated in audio equipment, and can be used wherever a level of some type needs to be indicated. A bar graph indicator, integral to the driving electronics, is available in the National Semiconductor IC type 3916. This device contains ten LEDs, arranged in a line, and requires a minimum of external components to allow the display to provide an indication of a quantity being measured. The input signal to the unit needs to be a voltage proportional to the variable being monitored. Thus, a solid state petrol gauge, oil pressure indicator, thermometer, voltmeter and so on become simple but effective realities.

The CRT

Cathode ray tubes are, without doubt, the most common means of displaying complex visual information. Prior to computers, the usual applications were in TV sets or cathode ray oscilloscopes. The principle of operation of a CRT is simplicity itself. Figure 5 shows the basics required by a CRT that is to display information. A highly evacuated glass envelope, suitably shaped is arranged to have a source of electrons at one end and a phosphorous-coated screen at the other. The 'electron gun' is merely an

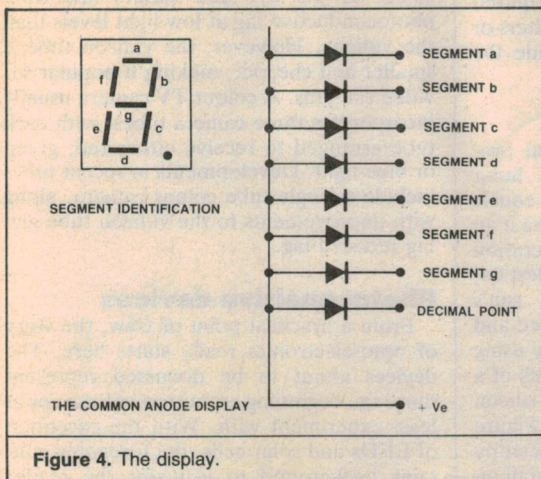


Figure 4. The display.

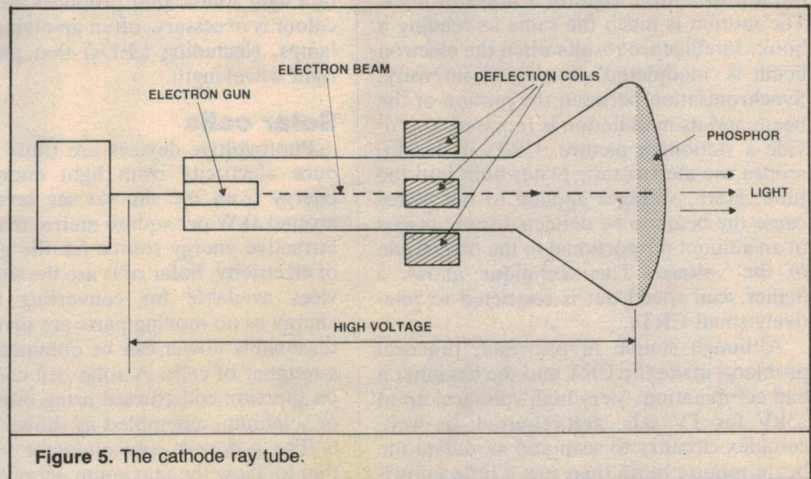


Figure 5. The cathode ray tube.

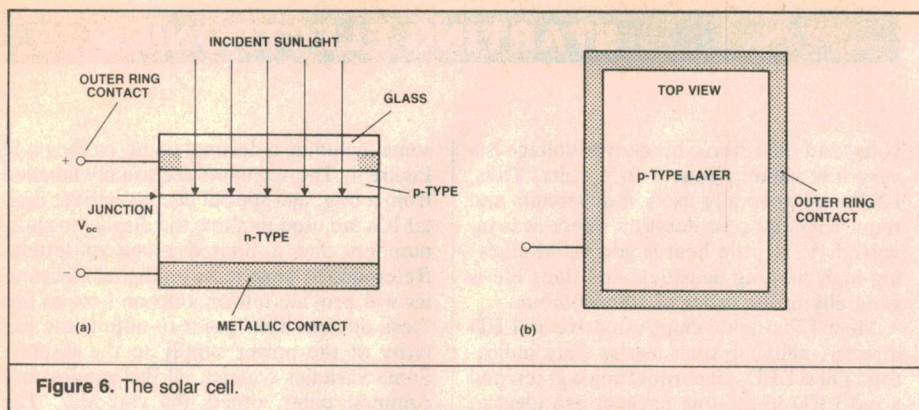


Figure 6. The solar cell.

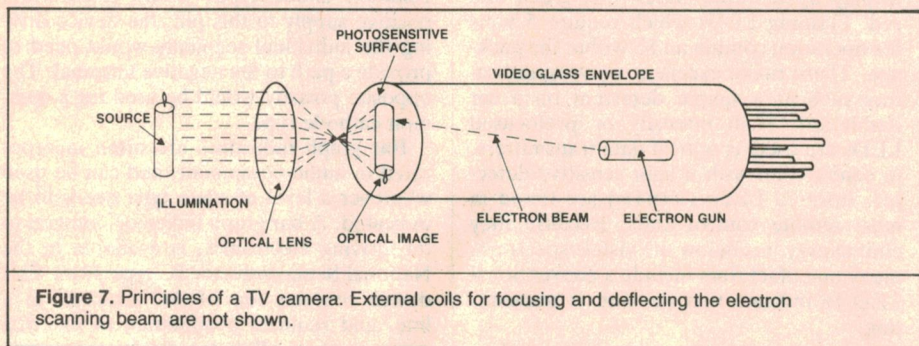


Figure 7. Principles of a TV camera. External coils for focusing and deflecting the electron scanning beam are not shown.

assembly containing a specially coated tube that is heated by a filament. Other electrodes within the gun focus the electron beam so that a high positive voltage present at the phosphor-coated end can attract the beam. The point of collision between the electrons and the phosphor results in the emission of light, the intensity of which is proportional to the strength of the electron beam.

Because a single point of light is relatively useless, a means of moving the beam over the entire face of the tube has to be provided. This can be done either by electrostatic or electromagnetic means. A TV set or a computer monitor uses an assembly called a yoke consisting of four coils arranged to allow the beam to be attracted vertically or horizontally. By applying suitable currents to the coils, the beam can be made to sweep the entire tube, usually from top left to bottom right in a series of lines. The motion is much the same as reading a book. Intelligence results when the electron beam is 'modulated' to vary its intensity. Synchronisation between the motion of the beam and its modulation is required to provide a stationary picture. CRTs in oscilloscopes use electrostatic plates built into the tube. Here, voltages applied to the plates cause the beam to be deflected from its axis at an amount proportional to the magnitude of the voltage. This technique allows a higher scan speed but is restricted to relatively small CRTs.

Although simple in principle, practical problems make the CRT and the beginner a bad combination. Very high voltages, up to 25kV for TV sets, are required; as well, complex circuitry to scan and modulate the beam require more than just a little knowl-

edge. However, a dissertation on optoelectronic devices would be incomplete without reference to this, the last living example of the valve.

Light sensitive devices

Using light to control an electrical current requires the use of components that have a characteristic which alters when exposed to light. Such devices are classified as being either photovoltaic, photosensitive or photoemissive. The most common group is the photosensitive types, and these form the basis of most opto-electronic applications. All these devices are most sensitive to a particular colour or wavelength, and are usually given specifications for this colour. As white light (such as that from the sun), comprises all colours, many devices operate effectively if such a light source is provided. If maximum sensitivity is required, the use of a light source that produces the required colour is necessary, often involving filters or lamps, (including LEDs) that provide the right wavelength.

Solar cells

Photovoltaic devices are those that produce electricity from light energy. Solar energy from the sun (at sea level) equals around 1kW per square metre, making it an attractive energy source for the generation of electricity. Solar cells are the simplest devices available for converting the sun's energy as no moving parts are involved and reasonable power can be obtained by using a number of cells. A solar cell consists of a pn junction constructed using either silicon or selenium, assembled as shown in Figure 6. The p doped semiconductor sufficiently thin to allow the maximum energy to fall on

the junction is placed to receive light. The power output of the cell is directly proportional to the intensity of the illumination, although the output voltage rises exponentially, giving the greatest rise from dark to half brilliance.

Because the response of a selenium solar cell is very similar to the eye, having its maximum output somewhere in the centre of the visible spectrum, these cells are used in exposure meters or for light measurement. Silicon cells have their highest output in the infrared region. Their most typical uses are in powering remote low power equipment, trickle charging batteries and providing energy for calculators and similar devices.

Video camera tubes

A phototube is an example of a photoemissive device. Although relatively obsolete, the phototube deserves a mention as it was the precursor to the video camera tube. From a constructional point of view, an element called the cathode is coated with a material that will emit electrons when struck by a light source. A second element (the anode) is placed to attract the electrons when a positive potential exists between it and the cathode. The resulting current is proportional to the light intensity, and a common application was to use a phototube as the active device in reproducing the sound from a movie film.

Early camera tubes used the photoemissive principle in a device called the image orthicon tube. From this developed the vidicon and plumbicon tubes, both of which use a plate whose conductivity varies with incident light. An electron beam is 'scanned' across the surface of the plate to allow a complete frame to be produced line by line. Figure 7 illustrates the general principle. Such tubes are vastly more complex than the simple phototube which, nevertheless, owes its origins to this device. The plumbicon tube has a spectral response closer to the eye and suffers less from photoconductive lag at low light levels than the vidicon. However, the vidicon tube is smaller and cheaper, making it popular for video cameras. A colour TV camera usually incorporates three camera tubes, with each tube arranged to receive either red, green or blue light. Developments in recent tubes include a single tube colour camera, along with improvements to the vidicon tube giving reduced lag.

Photosensitive devices

From a practical point of view, the story of opto-electronics really starts here. The devices about to be discussed represent those the beginning enthusiast can use, or at least experiment with. With the exception of LEDs and solar cells, the foregoing contains background to acquaint the reader

with devices outside basic electronics applications. Not so the components that follow. Using relatively simple circuitry, it becomes possible to build such items as a turns counter, a light activated switch, a remote control system and so on. A very popular device to control ac loads, including motors, lighting, heaters etc, is a solid state relay with an optocoupler input.

The basis of many opto devices is the pn junction alluded to in this and previous articles within the series. One device that does not rely on the pn junction is the light sensitive resistor. The LDR is a passive photoelectric component consisting of a layer of either cadmium sulphide or cadmium selenide, arranged between two connecting grids. Figure 8 shows the symbol, construction and a simple application.

The resistance of the LDR falls from a very high value (around 10M ohms) to only tens of ohms when illuminated. The response curve of a CdS device to colour is fairly similar to that of the eye, with a peak sensitivity in the centre of the spectrum. A problem with the LDR is its speed of operation. A reduction in light is detected quite slowly but a faster response can be measured when the incident light level is increased. Because the device is passive, its terminals are not polarised meaning the LDR can be used in ac or dc circuits.

The photodiode

A pn junction comprises two oppositely doped sections of semiconductor placed next to each other which allow the passage of a current when the p doped section has a positive voltage compared to the n doped section. Reversing the polarity prevents the flow of current, and in this way a semiconductor diode results. It is generally assumed that when the junction is subjected

to the reverse voltage no current flows. However, if measured with sensitive instruments, a small current, called the reverse leakage current, can be detected. The value of this current will increase with temperature and (you guessed it) with incident light.

The photodiode takes advantage of this interesting phenomenon and is arranged with its junction placed near a lens to focus the light on to this area. A circuit using a photodiode measures the reverse current caused by the light when the diode is operated with a reverse bias. The current is almost directly proportional to the intensity of the light, suggesting the photodiode be used in light measurement applications. Because the currents are small, some form of amplifier is usually required.

The photodiode is characterised by its small size, allowing it to be used in applications where a large number of individual light sources has to be detected, such as a card reader in a computer. Another advantage of these components is their speed of operation, a feature that often dictates their use despite the need for amplification of the signal. Figure 9 shows the basic construction and symbol.

Phototransistors

A light sensitive transistor is, in effect, a combination of a photodiode and a transistor within the one package resulting in the simplest photodiode-amplifier arrangement. A lens is usually incorporated on the top of the transistor, with three leads extending from the package, identified in the usual manner. Because of the extra gain, the response to light variations is slower than for the photodiode; the package is also larger. These devices, like the photodiode, have a spectral response most sensitive to colours around the red region and making

them suitable for use with filament lamps and red LEDs.

Although all three leads are available for use, most applications only use the collector and emitter leads, with the base lead left open circuit. Often a circuit using a light sensitive transistor is very simple, involving perhaps several other conventional transistors, or maybe an operational amplifier. Sometimes because of their sensitivity, the light source can be routed to the lens by means of optical fibres. This allows the electronics to be relatively remote from the optical action, an advantage where heat and vibration may be likely to cause problems to the phototransistor.

A variation on the basic phototransistor is the photo-darlington device. This package contains, in effect, two photosensitive transistors, coupled as shown in Figure 10. Very high current gains can be achieved, although speed of response falls accordingly. The use of these devices allows the detection of very low light levels, although careful design of the support circuitry is required to minimise the effects of leakage currents within the device.

Another component that is sometimes encountered is the light sensitive SCR. This device uses a photodiode within the SCR package to allow light to trigger the SCR. The classic application for the LASCR is to turn on outdoor lighting when the ambient light falls below a certain level. These devices are mainly low power types, but offer the characteristic of acting like a self-locking relay whereby, once triggered, the SCR remains on until deactivated by some other means.

Opto-electronic modules

The combination of a light source and a light sensitive device forms an optocoupler. ▶


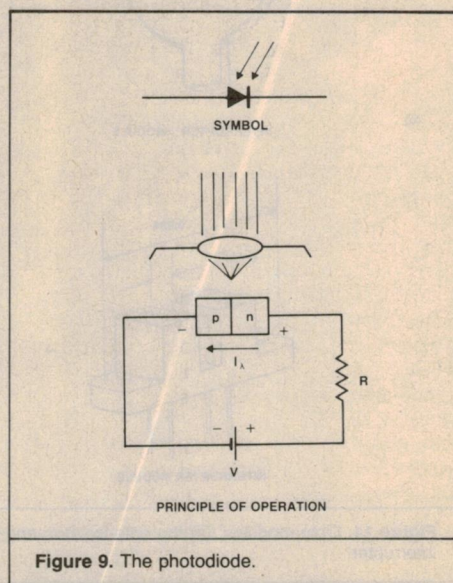
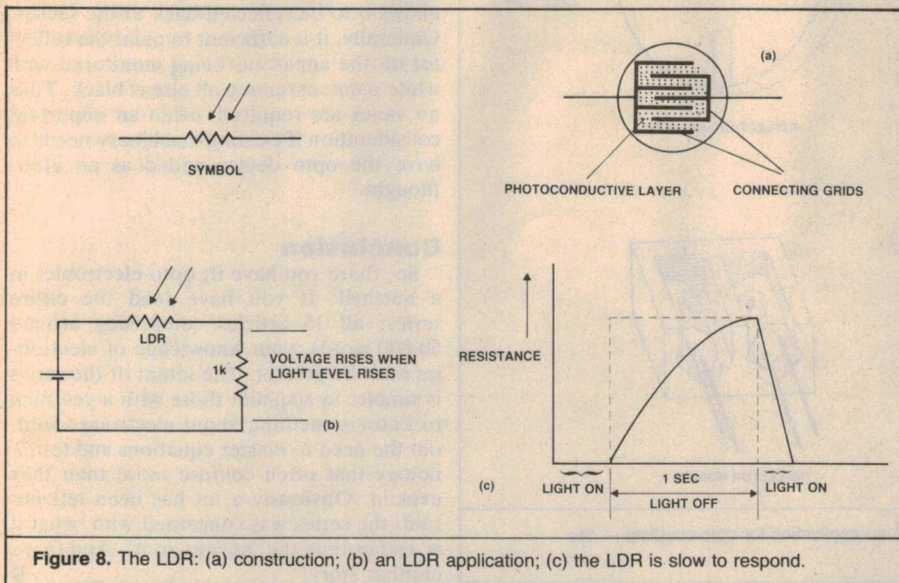


Figure 8. The LDR: (a) construction; (b) an LDR application; (c) the LDR is slow to respond.

Figure 9. The photodiode.

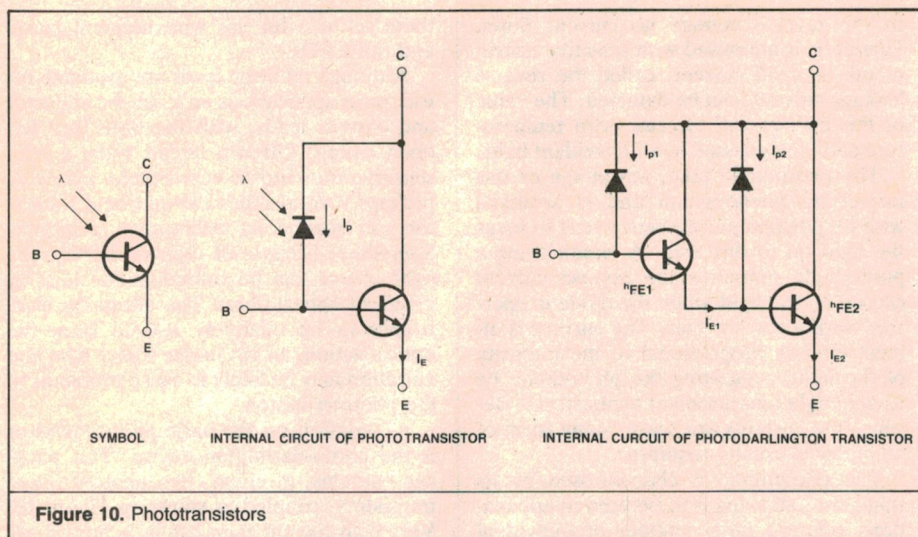


If provision is made to interrupt the path of the light an opto-interrupter results. Figure 11 shows some of the devices commonly available. A photocoupler, also known as an opto-isolator, contains in a totally sealed DIL package, an IRED and a phototransistor. The two components are electrically isolated, with an isolation voltage rating measured in kilovolts. Their main use is in interfacing between two circuits that must be electrically independent, such as a low voltage controller acting as a mains operated power device. The control signals are fed to the IRED and the output signal is from the transistor. Coupling between the two is provided by a transparent dielectric housed within the package. The controller needs to provide a current of around 10mA to the IRED, at a voltage of 1 to 2 volts and, as the switching speed of the combination is measured in microseconds, frequencies of many kilohertz can be passed through the unit.

Interrupter modules are very useful components, as the mounting of the devices within the package ensures optimum positioning of the two and means the user need only be concerned with the circuit requirements. As Figure 11 shows, there are two basic module types: the interrupter and the reflector. The first positions the sensor apart from the light source with a gap that can allow a vane to block the light. A good application is in counting the turns of a shaft, or if time is included, as a rev counter. Because the sensor is usually a transistor, support circuitry is simple, usually something to convert the signal to a digital format and the rest of the processing is via a digitally based circuit. These devices are often used instead of a mechanical limit switch, providing increased reliability.

The reflector types use a light beam that is sourced from the package at an angle that allows it to be reflected back to the sensor. Generally, it is sufficient to paint the reflector on the apparatus being monitored with white paint, assuming all else is black. Thus no vanes are required, often an important consideration if existing machinery needs to have the opto device added as an afterthought.


Conclusion

So, there you have it; opto-electronics in a nutshell. If you have read the entire series, all 15 articles comprising around 50,000 words, your knowledge of electronics must be greater. The intent of the series is simple; to acquaint those with a yearning to know something about electronics without the need to master equations and terminology that often confuse more than they explain. Obviously a lot has been left unsaid; the series was concerned with 'what it is' rather than the 'how to do it'. And that's another story!

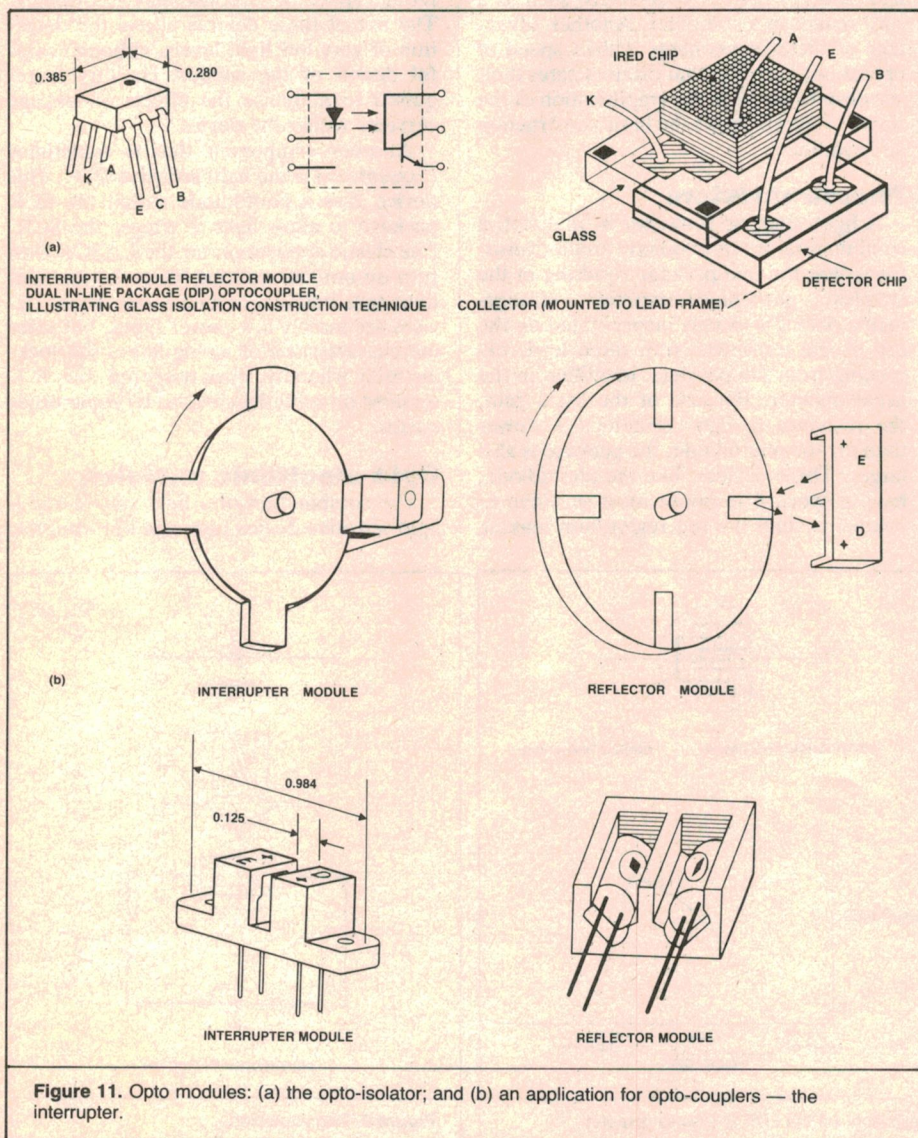

WHY DRIVE A MANUAL?

(WHEN YOU CAN AFFORD AN AUTOMATIC)

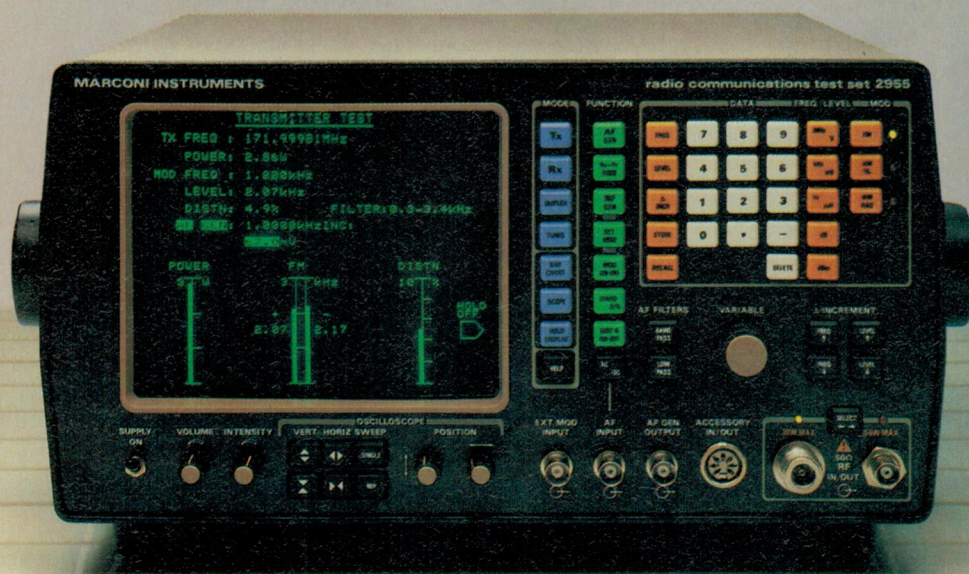

It's fast. And it's easy. Take our transmitter test.

Connect your transceiver. Press the TX key. Key your transmitter. In 3 seconds you can read transmitter frequency, power, modulation performance and distortion. That's what we call automatic! (Of course you could use GPIB and give your finger a rest.)

This unique level of simplicity and speed is available across transmitter, receiver, and full duplex tests up to 1000 MHz. In AM, FM, and PM – on mobiles, portables, and base stations.

Then there's the screen facility. This presents test results in both digital and bar chart format. You can freeze it – or store it. Use peak hold

to capture peak deviation. Or print the result out on the optional micro printer.

And as you'd expect it includes a tone generator/decoder for both sequential and single tone systems. To make it even easier to use, you can store your 37 most commonly used front panel settings for the next ten years.

The new 2955 makes other radio test sets seem overpriced and slow. Let us give you a demonstration. Just ring us.

marconi instruments 

Marconi Instruments
2 Giffnock Avenue
North Ryde N.S.W. 2113
N.S.W. Phone (02) 887 6117
VIC. Phone (03) 813 2977

THE INCREDIBLE NEW 2955 MOBILE RADIO TEST SET FROM MARCONI

Subscribe NOW to Electronics Today

IMPROVE YOUR LIFESTYLE BY MAXIMISING YOUR LISTENING AND VIEWING PLEASURE!


By subscribing to Electronics Today you will be kept up to date with feature-packed articles, the latest news and everything that Electronics enthusiasts, like you, need to know. There are always new techniques, new products and helpful stories to improve your knowledge.

WIN!!!!

This superb Sony Hi-Fi and Video combination could be yours!

Worth over \$10,000!!

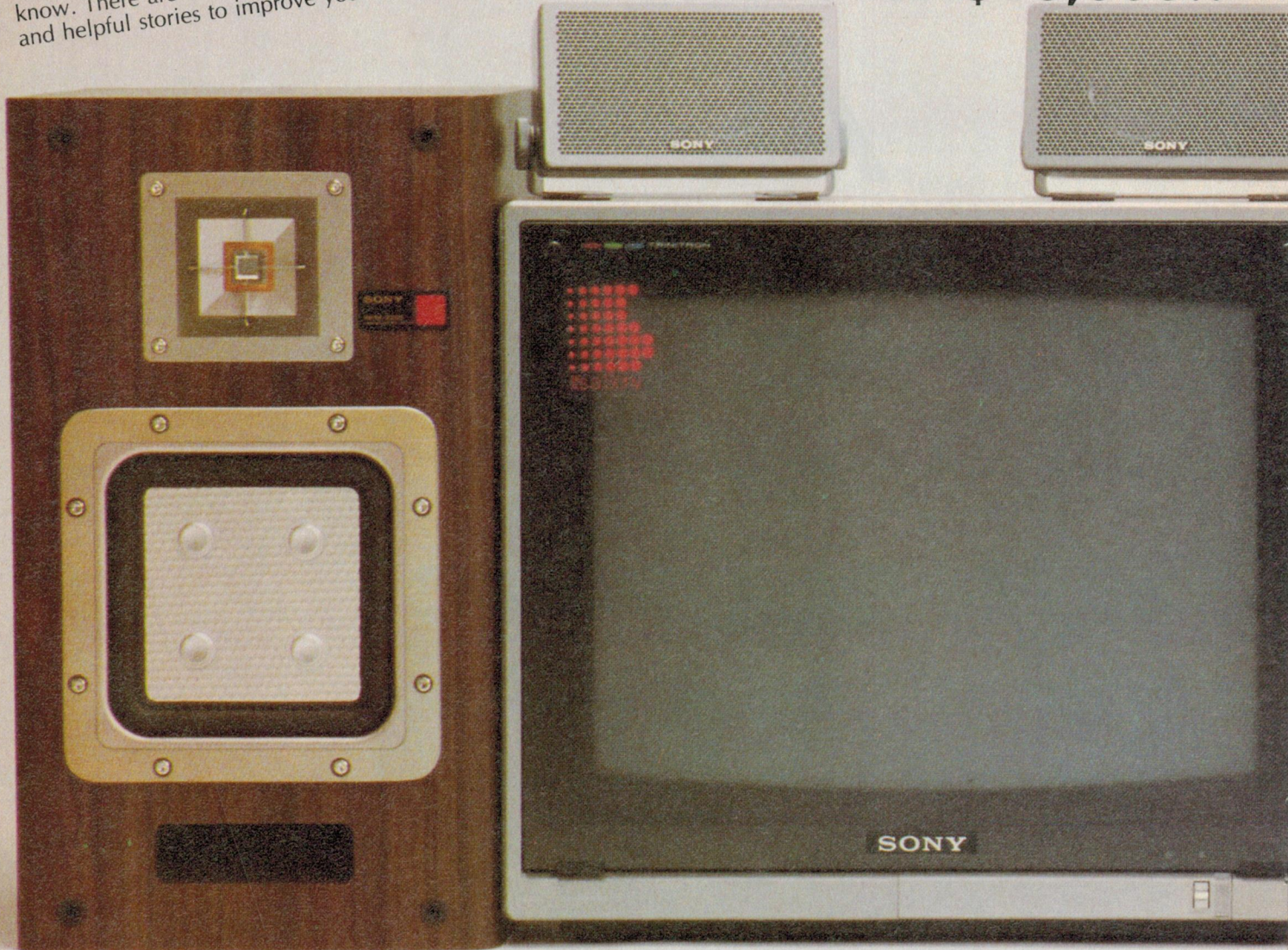Subscribe for 2 years and enjoy a special saving of almost \$6!



This ultimate in sight and sound reproduction you've only ever dreamed of before could be yours if you decide to subscribe to Electronics Today magazine. By subscribing to Electronics Today, you may very shortly be relaxing in front of your own Sony system, enjoying the superb listening pleasure that can only come from Compact Disc technology, and while basking in richer listening pleasure you could be watching, filming, or recording your selection using your new Sony Video-8 video system, both systems designed to be fully integrated with each other. This magnificent Sony Component System represents true, leading edge, technology. The 100 watt RMS per channel integrated stereo amplifier will give you plenty of power and can reproduce the

most demanding in CD fidelity. The discrete three head design stereo cassette deck will improve the faithfulness of your recorded sound. Improved frequency response will be evident as your AM/FM precision quartz tuner eliminates interference. With 20 key direct music selection and infra red remote control, the Digital Compact Disc player satisfies your most demanding requirements in fidelity and convenience. The digital compatible APM speaker system has been specially designed to cater for near perfect CD reproduction. A 20" high resolution Profeel monitor, including speakers, represents the best in video display monitors while the complete Video-8 system combines quality with portability. To complete the system a tuner/timer for the PAK 88 is included.

and win **YOUR FREE GIFT** — JUST FOR SUBSCRIBING!

This super-versatile Swiss Army Knife has seven different features — from a wire stripper to a can opener — and is that indispensable tool you'll find hard to do without.

The Swiss Army Knife features include a large blade, small blade, can opener, screw driver, cap lifter, wire stripper and key ring. You will receive 12 issues of Electronics Today (one every month) for \$35.40 or better still subscribe for 24 months and save \$5.90 — that's equal to 2 issues for free!

CLAIM YOUR
SPECIAL FREE
GIFT ...



NOW!

(Magazine and gift sent separately.)



WIN THE HI-FI/VIDEO SYSTEM OF
YOUR DREAMS!

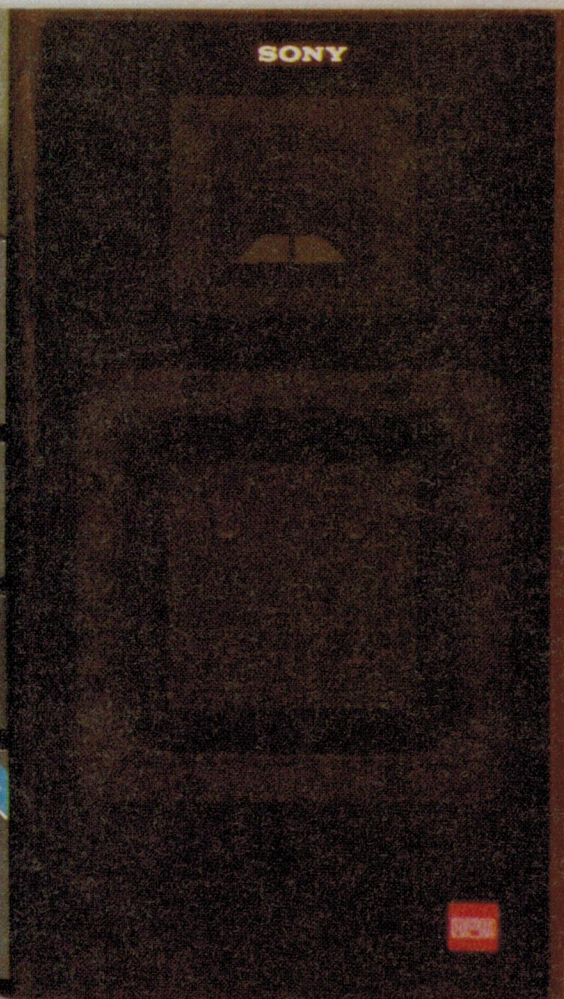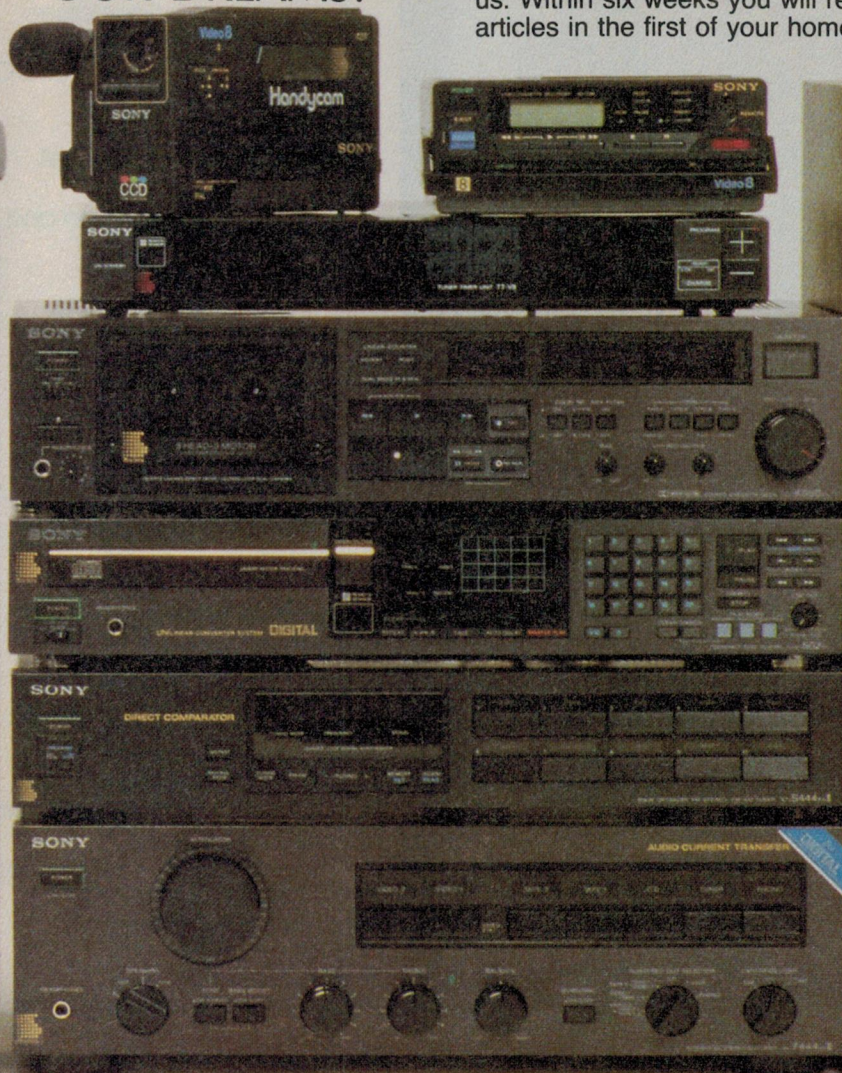Simply complete the subscription card in this magazine and send it FREE to us. Within six weeks you will receive your Swiss Army Knife and be enjoying articles in the first of your home-delivered ELECTRONICS TODAY magazine.



SONY

SHARE THE VISION

YOU MUST ACT NOW

YOUR NO-RISK GUARANTEE

If, for any reason you are not completely delighted with ELECTRONICS TODAY . . . simply let us know, and we'll gladly refund the unused portion of your subscription.

NSW Permit No TC86/532 issued under the Lotteries and Art Unions Act, 1901
VIC Raffles and Bingo permits Board Permit No 86/270 issued on 13/3/86
ACT Permit No TP86/162 issued under Lotteries Ordinance.
(Offer valid until 31 August, 1986.)

The exciting prize draw is also open to all subscribers who renew before the closing date. If the prize is not claimed within 12 months, a second draw will be run.

Let Arlec land you the best price in town!



TRANSFORMERS: General purpose, specific application, P.C.B. mount, ferrite core and encapsulated.

POWER SUPPLIES: Specialised and switch mode.

PLUG PACK ADAPTORS: AC, DC and regulated outputs.

BATTERY CHARGERS: Specialised Nicad, Gel Cell and lead acid.

P.C.B. ASSEMBLY: Insertion and wave soldering Arlec or customer components.

WHAT ELSE? Light dimmers, speed controllers, electronic timers and component housing.

DESIGN: Computer assisted development facilities. Conforming to Australian standards with Electricity Authority and Telecom approval.

MANUFACTURER: Electronic assembly line features:

- laser guided insertion
- wave soldering machines
- Modern Press Shop:
- computer controlled turret press and guillotines.

Local and Off Shore:

- Arlec has factories in Australia and Hong Kong.

40 YEARS IN THE BUSINESS: Arlec is the name you can trust for:

- customer satisfaction
- quality control
- after sales service
- guarantee on all work done.

ARLEC

QUALITY PRODUCTS

VICTORIA:	
NEW SOUTH WALES:	(03) 895 0222
QUEENSLAND:	(02) 789 6733
SOUTH AUST:	(07) 852 1131
WESTERN AUST:	(08) 297 0766
CANBERRA:	(09) 445 3611
HOBART:	(062) 80 5519
LAUNCESTON:	(002) 34 2233
TOWNSVILLE:	(003) 31 6533
DARWIN:	(077) 79 4288
WAGGA WAGGA:	(089) 84 4227
NEWCASTLE:	(069) 21 2735
	(049) 25 896

ETI READER SERVICE 188


CLEARING THE LAB SHELVES

— with the Marconi 2955 communications service monitor

Peter D. Williams

Peter Williams is Director of Associated Calibration Laboratories in Melbourne.

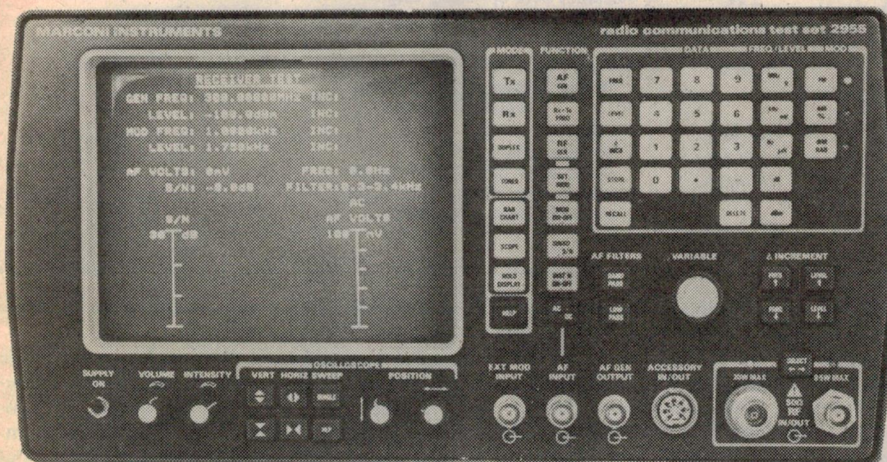Is test equipment too complicated, too expensive? This new test set says no to both questions but what would Guglielmo say to his company's latest creation? It checks a transceiver in less than three seconds!



MARCONI HAS NOT always been first with the latest technological advance and has been criticised in the past for unimaginative and complacent engineers and marketers. However, in the last few years, sweeping changes in direction and close attention to costs have changed all this.

All this is by way of introduction to one of Marconi's latest efforts in test equipment design — a multi purpose radio service test unit.

The Marconi 2955 is a specialised instrument for use in the test, diagnosis and repair of communication equipment over the frequency range of 0.4 to 1000MHz.

During production, communications equipment is subjected to exacting tests of its frequency accuracy, frequency stability, modulation, distortion, sensitivity, unwanted or spurious outputs from transmitter, power output of transmitter, and encoding and decoding tones.

One would expect these specifications to be checked as part of any radio repair process also, and until a few years ago this required shelves full of test gear. For example, to measure frequency you needed a counter; to generate an rf signal you needed a signal generator; to measure distortion, a distortion meter; power output, a power

meter, etc. All in all six or seven separate, expensive instruments, time consuming to interconnect and evaluate, possibly leading to skimmed work and a tarnished reputation for the repair shop and service industry generally.

From this situation developed the concept of the 'service monitor', which would combine these test functions and add in the feature of portability. In Australia we have had, with varying degrees of success, this type of equipment from Ailtech-Singer, Cushman, IFR, Motorola, Systron Donner, Wavetek, to name a few, and all designed to do more tests while packed into a single instrument.

So what's so special about the Marconi 2955? It's the fresh start approach.

Different but how?

After doing it's homework, Marconi obviously concluded that technicians wanted less complexity, fewer knobs and less time to learn how to drive it.

What you see on the screen of the Marconi box is transmitter frequency, power output, deviation frequency and modulating frequency with its level. All this information is held on the screen until it is erased with vertical bar charts displaying the dynamic measurements in real time — no meters, no range settings as the box uses auto ranging on all scales.

If you wish to check the receiver of your transceiver, a quick push of the Rx = Tx pushbutton automatically places the 2955 on the same frequency that was transmitted to it and injects the receiver frequency to the radio under test.

If your radio operates on duplex, where receive and transmit frequencies differ, or even cross band transceivers, any of these offsets may be entered into any one of the 38 non-volatile storage areas. Complete in-

LABORATORY REPORT: MODEL 2955 SERIAL No. 119507/107

In the case of modulation and power indications, most test sets have accuracies ranging from 5% to 20% so a radio that has a nominal 10W output could indicate anywhere from 8W to 12W and still be within the specification of the test set. It is important for any test department to not only calibrate its equipment so that it is within specification, but to know what the tolerances are so that allowance can be made for the readings. It is pleasing to see such a comprehensive range of specifications supplied with the 2955 to enable these allowances to be made.

The Marconi is of first class construction. Modular layout makes servicing, if and when required, a breeze.

To further indicate the tightening and upgrading of specifications, which we believe are required in today's environment, we have shown Marconi's claimed specifications with our results and related these to average current workshop specifications represented by other multipurpose instruments and a representative figure expected of laboratory type instruments.

Lab Results & Manufacturer's Specs	Present W/shop Specs (average)	Lab Equip Specs (average)
rf SIGNAL GENERATOR SECTION		
Frequency Range 400kHz — 1.0GHz		
Output Level		
Measured: ± 2 dB	± 3 dB	± 1.5 dB
Spec: ± 2 dB		
Residual FM		
Measured: < 30 Hz	< 100 Hz	< 15 Hz
Spec: < 30 Hz		
Harmonics		
Measured: 1.5MHz -38 dBc; 1.5-250MHz -35 dBc; 250-1000MHz -20 dBc	< 25 dBc	< 25 dBc
Spec: -20 dBc; -30 dBc; -20 dBc		
Spurious (worst case)		
Measured: < -60 dBc	< -60 dBc	< -80 dBc
Spec: < -45 dBc 0.4-88MHz < -60 dBc to 1000MHz		
MODULATION SECTION		
AM accuracy @ 50% indication		
Measured: better than 3%	$\pm 10\%$	$\pm 5\%$
Spec: $\pm 10\%$		
FM accuracy @ 5kHz deviation		
Measured: better than 3%	$\pm 10\%$	$\pm 5\%$
MASTER OSCILLATOR		
Oven oscillator 10MHz		
Measured: ± 1 part in 10^8 over 1 hour after warm up		± 2 parts in 10^7 over 24 hours
Spec: stability < 1 part 10^9 over 1 second		

rf FREQ METER SECTION

Accuracy: same as internal standard $\pm 3\%$

Error resolution:

1Hz/10Hz to 100MHz
10Hz/100MHz to 1GHz

Sensitivity
BNC input

Measured: nominal 30mV

12dB SINAD

Spec: 50mV

N type input

Measured: nominal 224mV

12dB SINAD

Spec: 500mV

rf POWER METER

Accuracy

Measured: better than 5% $\pm 13\%$ $\pm 1.5\%$

@ 476MHz and

155MHz 10W

Spec: $\pm 10\%$

MODULATION METER

AM/FM on receive

Accuracy over operating range

Measured: better than 5% $\pm 10\%$ $\pm 1\%$

Spec: $\pm 8.5\%$ 50Hz-10kHz

AM/FM on generate

Accuracy over operating range

Measured: better than 5%

Spec: $\pm 10\%$ 50Hz to 5kHz

SINAD METER

Accuracy over operating range

Measured: better than ± 1 dB ± 1 dB

Spec: ± 1 dB

DISTORTION METER

Accuracy over operating range

Measured: better than 3%

Spec: $\pm 5\%$

AF LEVEL METER

Accuracy over operating range

Measured: better than 5%

Spec: $\pm 5\%$

PM/AM/FM ACCURACY

Measured: better than 8% over operating range

Spec: $\pm 10\%$

Voltage measured 3%

Spec: $\pm 5\%$ 10mV/Div to 20V/div

Sweep rates 100 μ s/div to 5s/div

locked to internal standard

strument stores of frequency and modulation parameters can be set up at will; a decided convenience for those checking systems using common channels — police, fire, government and the like.

Functions and features

As befits a pedigreed, self respecting and processor-controlled test box, all the desired functions listed earlier can be initiated: rf power meter, rf frequency counter, modulation meter, rf signal generator, audio signal generator, audio frequency counter, voltmeter, audio distortion meter, SINAD meter, digital oscilloscope, and tones encoder/decoder.

Pushbuttons for function and data entries are colour coded.

The CRT display provides prompts during data entry, guidance during sequences and shows measurement results by means of five auto ranging bar charts. A relatively crude example of bar charts is the loudness

displays on audio gear. The display on the 2955 enables technicians to make precise adjustments to levels. Previously, digital equipment was at a disadvantage for this sort of work as you could not easily see the effect of adjustments approaching or receding from a desired figure as you do with analog meters. The 2955 gives the best of both worlds.

The digital storage scope has an 800kHz sampling rate with a 50kHz bandwidth so you can see the transmitter's or receiver's audio. Repetitive sweep, single sweep and freeze facilities are available. This freeze enables you to observe readings at leisure, especially if you have just keyed in a high-power transmitter and don't want to overload the rf.

Frequency counters can simultaneously show rf and AF frequency readings with either 1Hz or 10Hz resolution for rf and 0.1Hz for AF. Accuracy of the readings is that of the internal frequency standard; if

you are after better accuracy an external standard can be used.

The signal generator can be set up by the keyboard, keying in a transmitter as described earlier or from any of the user programmed sequences. Modulation can be internal or external for AM, FM or phase and is protected against reverse power overloads. Independent tuning for duplex measurements enables cross band operation from say VHF to UHF or vice versa.

Modulation monitoring both on the built-in oscilloscope and from the speaker is possible. Some might question the inability of the monitor to show or provide spectrum analysis. The low receive sensitivity could be criticised too, because an ability to do off air tests of remote transmitters aids in diagnosis. The short answer to these criticisms is that the 2955 was deliberately designed to give automatic frequency tuning with inputs of about 50mV. Obviously greater sensitivity would trigger unwanted responses

and, as the box is billed as service test set, it is expected that equipment under test would be on the bench. Spectrum analysis is best left to the specialised instruments designed for the task.

Radio frequency power can be measured from microwatts to 30W continuously or up to 100W for short periods. Again, the auto ranging bar chart will show the power as well as display it digitally on the screen. The bar charts allow easy tuning of final output stages. The fact that power can be shown down to a milliwatt or better, means that you can use the instrument to show injection levels to oscillators, mixers and the like.

The audio frequency generator operates from 20Hz to 20kHz with a fixed 1kHz tone for distortion measurements. All these internal tones can be used to modulate the rf generator for AM, FM and phase modulation.

Tone encoding/decoding facilities make it a breeze to simulate audible as well as sub-audible tones.

Selective calling systems using four international standards plus any user defined systems are available. In addition, you can send and receive a sequence of up to 10 out of 15 allocated tone frequencies, which can be generated in single step, tone burst or a continuous cycle. For transmitter testing, each received tone is compared with standard frequency allocations held in memory. The read out will give the percentage frequency error.


The built-in self-test facility may be called up to enable faults to be identified to a major module level or to group of components. In fact, every time the instrument is turned on, the self-test circuitry goes through three major checks. Failure of any of these tests causes an error message to be displayed and sub tests are initiated so that you can isolate the problem with fault tracing.

Other features include a 'freeze' facility which can hold a displayed value so modulation limiting circuits can be adjusted; auto ranging measurement scales for checking transmitters; an on-screen warning and audible alarm for rf power overload; and a HOLD display key to enable you to freeze all readings once they have stabilised.

A carrier wave form can be seen at the IF socket at the rear. With duplex testing there is no restriction on total frequency offset between receiver and transmitter thus allowing even cross band testing.

A split screen enables you to see transmitter information on the left and receiver information on the right. It can all be copied on to a printer with customer names, serial number, date, etc, for record keeping.

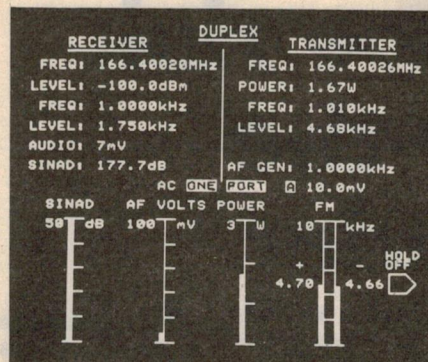Standard default settings are -100dBm and 1.75kHz deviation at 1kHz modulating frequency for the signal generator.



Duplex testing. Screen display can show major parameters for the transmitter and receiver functions of any VHF or UHF radio. Receive and transmit frequencies can be up to 999.6MHz in difference. Note displayed frequency error for a nominal 166.4MHz signal. HOLD OFF message shows that information is 'frozen' on screen even when radio is not activated. Information may be erased at leisure. Note that some receiver functions are not displayed. If duplex is used, similar information for only receiver or transmitter can be shown. Also note the fast acting bar indicators. The power chart can resolve to 1μW up to 300μW.

Without doing anything else except keying the transmitter into the Marconi to get the receiver frequency, you can get a system check of the radio. Selecting other keys will give you SINAD, distortion or S/N (signal-to-noise). The tuning knob can give you fine control of deviation, tones, etc.

The 2955 has a big seven-inch screen which makes it ideal for displaying a built-in instruction manual. Even during the setting up of a test sequence, help is close at hand by pressing the button labelled HELP! What you see displayed are options, terminology and how to achieve the next step in the sequence. Having sorted yourself out, pressing the same button restores you to the real world of the information display.

This screen is not a conventional phosphor CRT but includes an internal mesh which at normal viewing distances improves sharpness of the lettering.

Two sockets N and BNC are available on the front panel for high and low power inputs. The low signal output is protected against 50 watts reverse, flashing an uncomplimentary signal on the screen and sounding an alarm!

Performance

Radio frequency power measurement down to better than a milliwatt can enable you to check low rf levels in predriver stages or local oscillators. Although the accuracy of ±20% at low levels isn't lab stuff, remember that rf power meter manufacturers such as Bird don't claim much better than that. Communication power accuracy is around the ±10% for higher powers.

Frequency accuracy using the crystal

oven as standard issue is better than five parts in 10-8. To get this degree of accuracy in other instruments you have to have it optioned up.

Signal generator output needs to have dependable figures. The accuracy approaches that of laboratory instruments and exemplifies the nature of present day requirements. Users of communication equipment are getting the benefit of business and government institutions demanding more exacting technical requirements for equipment.

The lowest reference frequency generated is 400kHz with resolution of 50Hz. If anything below this is wanted, then you have a problem.

"Off air" checks with antenna are not possible unless you are right under/alongside the transmitter. But how much off air testing would you want to do anyway?

The digital oscilloscope is not entirely adequate for 'fine line' analysis, and the lack of spectrum monitor/analyser means you really need a proper spectrum analyser if you want to see limits of spurious outputs with any accuracy.

The audio generator has no usable output below 20Hz. Some users may want to modulate/sweep an oscillator to get response curves of an Rx front end etc.

Apart from unplugging the coax, it is not possible to remove the rf carrier for noise tests.

Output for reference from the internal frequency standard is not available and there is no obvious external adjustment to put the internal frequency standard on frequency, although a 1MHz reference standard can be applied to a BNC socket on the rear panel.

On the ergonomics side, pushbuttons for incrementing up or down must be pressed repeatedly to effect continual change in level or frequency rather than simply pressed while the level steps automatically until released. As it is, a pushbutton can be pressed, click heard but no action, unless pressed dead on centre.

Conclusion

The Marconi has been correctly billed as a mobile communication test and service unit. With it you can do all the tests required to evaluate any radio. If some older tests such as quietening are not shown then I suggest that a procedure could be devised.

At \$13,600 or thereabouts plus sales tax this unit represents excellent value for the tasks it can perform and at a level of accuracy found in R&D departments, if at all, only a few years ago.

With accessories to handle cellular radio coming up, dc supplies for portable operation, the 2955 must be seriously considered by anyone involved in servicing communication systems. To my mind, it is digital technology usefully employed.

Interference risk from over-the-horizon radar

Shortwave listeners are familiar with the Russian over-the-horizon radar, informally known as the Russian Woodpecker, and are aware that as it moves up and down shortwave frequencies, it causes considerable interference.

A similar system of over-the-horizon radar is in use in the US for surveillance, and Australia is setting up a similar project in Central Australia. According to Doctor Desmond Ball in a recent Radio Australia interview, funds have been allocated to complete the project.

Traditional radar uses very high frequencies and is based on the line-of-sight which enables excellent definition of an aircraft or whatever object is being surveyed as the signal bounces off the object. But the range of area

under radar supervision is very much restricted. The over-the-horizon radar uses much lower frequencies in the shortwave bands and is functional between 3 and 30MHz. The radar beam is bounced off the ionosphere and depending on power the signal could skip twice across the world 3000 to 5000km.

Over-the-horizon radar suffers in precision object location and identification. Australian authorities believe that as the southern hemisphere has better propagation and there is less air-

craft traffic, identification of unannounced objects is more readily detected. It is on these two assumptions that Australia feels its system is more advanced than the two presently in operation.

The first over-the-horizon radar introduced by the Russians caused protests from shortwave listeners and broadcasters when it was activated from its location at Gomel near Kiev in the Ukraine. The second station, located in the Caucasus, is focused down to the south-east covering China, and the third in Siberia on the Amur River at Nikolaevsk covers the northern region of the globe. The early Russian stations used tremendous



— Arthur Cushen

power, up to 20 or 40 megawatts.

In recent years the Russians have reduced power and become less troublesome, but it is not certain whether that was due to the international protests.

Doctor Ball assured his listeners that the Australian over-the-horizon radar would not cause the same degree of interference due to the much lower power being used (around 50kW).

DOC news

The first of three transmitting stations for the new ABC short-wave radio service which will blanket the Northern Territory officially began on 20 February, 1986.

John Brown, acting for Communications Minister Michael Duffy, announced the commencement of operations at the Alice Springs high-powered (50,000 W) transmitting station. The other two stations, at Tennant Creek and Katherine, are scheduled to begin transmissions later in the year. Each of the three will have an approximate broadcasting range of 450 km in all directions, and, in combination, will effectively provide radio coverage of the whole of the Northern Territory.

The Alice Springs station (call sign VL8A) will broadcast on frequencies of 4.835 MHz (daytime) and 2.310 MHz (night and early morning). Call signs and frequencies for the other stations will be: Tennant Creek, VL8T, using 4.910 MHz (day-

time) and 2.325 MHz (night and morning); and Katherine, VL8K, using 5.025 MHz (daytime) and 2.485 MHz (night and morning).

Proposals to have commercial entrepreneurs paid an annual fee for rebroadcasting ABC television programs to small, remote communities have proved unacceptable on cost grounds.

Minister Duffy said the government had decided money would be better spent on the regular capital works program under which ABC transmitters and translators were being extended to larger communities round the country. The minister said his department would continue to encourage small communities in remote Australia to invest in self-help broadcasting reception schemes enabling them to get radio and television services much sooner than the government could provide them, given its wider responsibilities across the nation.

SBS's multicultural television

service officially began broadcasting in Hobart and Perth on 16 March 1986.

Originally the SBS was to begin transmissions in both cities by the end of January 1986. However, due to delays in the delivery of transmitters and the installation of time delay equipment to provide Perth with programs in local time, the opening had to be put back to March. Test transmissions were broadcast approximately a fortnight in advance of the official opening to enable installation of UHF antennas.

The DOC launched extensive UHF education programs in both cities, with a pamphlet on UHF reception delivered to every household and a hands-on information stand being set up to handle inquiries from the public.

Over four million Australians in regional areas will receive an extra ABC radio service if draft plans issued last November are successful. The intention is to in-

troduce the service over the next five years, but this is dependent on clearance of television channels from what is known as Band 2 and studio construction in many parts of Australia.

A discussion paper on the subject has been published, entitled *A Second Regional Radio Network for the Australian Broadcasting Corporation*.

The SRRN scheme would involve the establishment of 16 new regional radio studios and upgrading of all existing ones.

Communications Minister Duffy announced that three ABC radio services (Regional Radio 1, Radio 2 and Stereo FM) will shortly be available via the satellite.

The new Secretary to the Department of Communications, Mr Charles Halton, CBE, officially took over from the retiring Secretary, Mr Bob Lansdown, CBE on 1 February, 1986.

SIEMENS

RFI PROTECTION COMPONENTS

Five ranges of components to counter problems of electrical interference . . . outside the lab.

Because there is no one solution to radio frequency interference (RFI), Siemens makes 5 main ranges of interference suppression components. From these, additional equipment can be customised to cope with your RFI problems.

As you know, outside interference often only raises its ugly head outside the lab. So consider this basic Siemens range that can counter most causes . . . and see an end to customer complaints, warranty costs, service expenses and legal battles.




1. Surge Voltage Protectors . . . ideal for very large energy spikes such as are induced into wiring by nearby lightning strikes to the ground.

2. Varistors . . . for lower energy spikes. Also useful as secondary back-up behind gas arrestors; and can be used directly across mains wiring to remove spikes riding on the 50 Hz waveform.

3. RFI Filters . . . used on the mains outlet to keep out the most notorious interference; and also to prevent your equipment interfering with others.

4. Ceramic Capacitors . . . to be scattered over circuits and across all the input/outlet lines on data communication points.

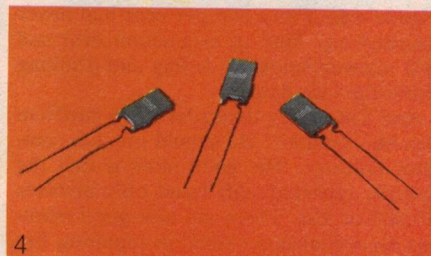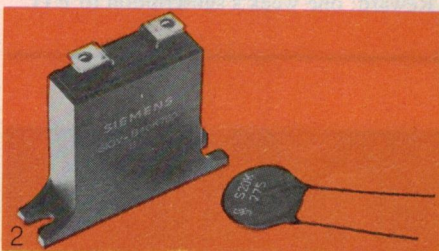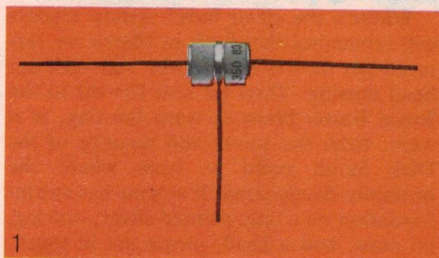5. Specialised Components . . . including X capacitors, Y capacitors, current compensated chokes and micro chokes.



Special Siemens advantages

- ☐ Because Siemens parts are already used by major local manufacturers, substantial stocks are in ready supply.
- ☐ Siemens staff are skilled in all the available protection technologies; so can offer real help to designers who encounter tricky problems.

Call us now, for quick supply or helpful consultation.

Siemens Ltd.

544 Church St., Richmond, Vic. 3121.

Sales Offices

Melbourne:

(03) 420 7318

Sydney:

(02) 436 8730

Distributors:

Victoria: Promark Electronics (Vic.)

(03) 878 1255

New South Wales: Nexus Electronics Pty. Ltd.

(02) 439 5800

New South Wales:

Promark Electronics Pty. Ltd.

(02) 439 6477

Queensland: ECO Electronics

(07) 376 5677

South Australia: R.G. Pank Pty. Ltd.

(08) 51 2411

South Australia: Protronics Pty. Ltd.

(08) 212 3111

Western Australia: Reserve Electronics

(09) 328 9755

INGENIOUS ELECTRONIC ENGINEERING

Computer terrorism

A Melbourne academic, Gary Cooper of RMIT, has just completed a study of the nation's computer industry and its attitude to security. He polled the EDP managers of the 700 largest computer companies. Some figures quoted in *Pacific Computer Weekly* magazine: 50% of managers believed they were vulnerable to sabotage; 25% admitted to significant problems with staff threatening to cause machine downtime or sabotage; 7% admitted to discovering a fraud by staff using the machine.

Of those who had discovered problems like this in their installations a quarter said they had not done anything about it and two thirds had not taken legal action.

The same survey found that 14% of managers said they had experienced disasters like floods, 10% had experienced a fire, yet six did not know where their nearest fire brigade was. Forty five per cent had never practised any kind of evacuation drill and 10% allowed smoking, eating and drinking within the installation.

And The Actor thinks he had a problem with Mr Gaddafi?! He should join the computer industry. The good news is that the typically reported staff fraud only involves \$10,000 or less. There are also good openings for technicians skilled in repairing fire damaged computers.

Another piece of paper floating across the desk this week catered, not for the hopelessly laid back, but for the ridiculously paranoid. Netmap, a North Sydney based computer company that would like to get a little bigger has opened a hotline that will advise you on how to overcome your security problems. With an assurance from Michael Hilsden that "doors, locks and passwords are no longer effective barriers to computer intrusion" ringing in your ears, you will be advised to buy an encryptor. This is a device that completely scrambles the signal on the line so no one can understand what you're saying. There are good openings for technicians skilled in installing encryption systems.

Ain't it good to back a winner?

Missing persons bureau

Where's the silver lady? Astute readers will remember that back in March we featured her on the front cover with half her head missing. Then we sent her off to the Royal Easter Show to wave the flag, as it were, from the safety and security of the Dick Smith stand — from where she promptly disappeared. If anyone has any information on a lady painted silver, one leg, no arms, half a head, please get in touch. Reward: one week's subscription to ETI.

Comet Halley



Spotted: One weekend at Braidwood by the ETI Staff.

SCOPE TOOLS


From Truscott

NEW INFINITELY ADJUSTABLE 200° - 470° C

Illuminated Temp. readout monitors actual tip temperature.

Zero Voltage switching for maximum component safety.

Select the tip temp. required.

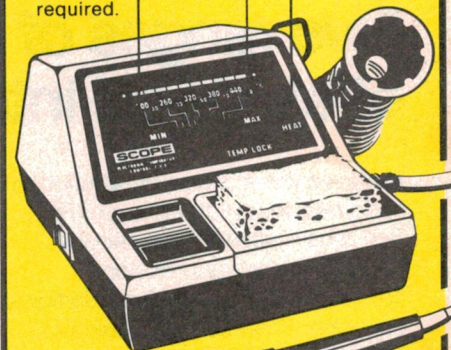

CODE ETC60L

60 Watts of back-up power - 30W Pencil optional.

Burnproof & flexible lead.


Ceramic encapsulated element for lowest earth leakage

SOLDER REMOVER METAL BODY - SELF CLEANING

CODE SR



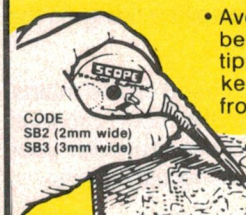SOLDER BLOTTER 2 M IN WIND BACK DISPENSER



• Avoid burnt fingers because metal tipped container keeps fingers away from iron tip

• Dispenser locates tape positively

CODE SB2 (2mm wide) SB3 (3mm wide)

IAN J. TRUSCOTT ELECTRONICS

30 Lacey Street,
(Cnr. Windsor Street)
CROYDON, 3136
Telephone: (03) 723 3860





There's just one Australian up there.

STC, alone among Australian companies, was chosen to build vital electronics for the AUSSAT satellites. This is in recognition of our many achievements in communications,** and a tribute to our known ability to manufacture technological components to the "fail-safe" standards demanded in space.

As communications systems evolve at an

amazing rate, STC maintains its status at the leading edge. Today, the many STC products and services, all designed within the last two years, continue to speed and simplify the ways in which people and businesses communicate. STC. The first Australian company into space.

The only Australian company into space. Proudly part of the AUSSAT Programme.

STC

An Australian Company of ITT

THE LEADING EDGE.

**STC electronics are also built into satellites for the Indonesian and Mexican governments as well as the vital U.S. communications satellites WESTAR and GALAXY.

Get all of Yamaha's latest audio equipment for only 33 cents.



Fill in this coupon and you'll get Yamaha's free catalogue featuring the latest and complete range of compact disc players, cassette decks, turntables, cartridges, integrated amps, separate amps, tuners, receivers, graphic equalizers, headphones and system components. With each component comes something you wouldn't expect. **5 YEAR WARRANTY.**

Name _____

Address _____

Postcode _____

Yamaha Consumer Electronics Division, 17-33
Market Street, South Melbourne, Victoria 3205.

*Limited warranty.

